

★ LTI systems described by linear, constant coeff, DE's.

- Last time we classified systems and limited ourselves to a class of systems for the remainder.

Linear - Time-Invariant (LTI) Systems.

- Today we will see how LCCDE's provide the natural framework for studying LTI systems from an external perspective.

★ Internal v/s External descriptions.

- Consider a first-order system with input/output relationship

$$\text{causal } x(t) \rightarrow \boxed{} \rightarrow y(t) = e^{-at} \int_0^t b e^{at} x(t) dt$$

This is an external description of the system.

- external system descriptions tell us nothing about the details inside the block.
- external descriptions are not unique to a system, multiple internal descriptions could lead to the same external one.

E.g.

$$y' + \underbrace{\frac{R_1 + R_2}{R_1 R_2 C}}_a y = \underbrace{\frac{1}{R_1 C}}_b x$$

b above

$$y' + \underbrace{\frac{R_1 + R_2}{L}}_a y = \underbrace{\frac{R_2}{L}}_b x$$

b above

From an external perspective, for different component values with same a, b the two systems appear identical.

Both are described by a 1st order LCCDE.

Note: # energy storage elements = # internal states in circuits.

Question: If LTI systems are just LCCDE why have a whole other course?

Answers: - for non homogeneous DE you were likely only taught 1st & 2nd order with a couple of standard inputs.

- Method of undetermined coefficients
- Method of variation of parameters.

But we are interested in systems with arbitrary order and input

You may or may not have learned these in DAAPEg.


⇒ This requires use of convolution or Laplace to solve for causal inputs.

For non-causal inputs we need Bilateral Laplace or Fourier techniques.

Exactly which depends on periodic or not.

* Internal descriptions

Lets look at a 2nd order example.

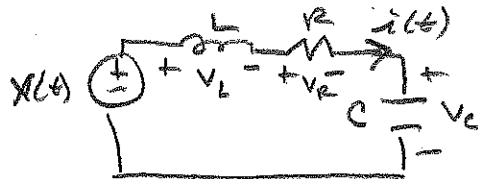

- 2 energy storage elements
so 2 states

1. current through inductor

2. Voltage across capacitor.

Analysis: (1) KVL: $V_L + V_R + V_C = X$

(2) Relationship between V_L and i is $V_L = L \frac{di}{dt}$

(3) put (2) → (1) solve for $\frac{di}{dt} = -\frac{R}{L} i - \frac{1}{L} V_C + \frac{1}{L} X$ (5)

State Equation

↑
derivative of state var

↖
terms of other states

↑
and input.

(4) Relationship between V_C & i : $i = C \frac{dV_C}{dt}$ or $\frac{dV_C}{dt} = \frac{1}{C} i$

another state equation

- Let's combine the state equation (3) & (4) into matrix-vector form.

$$\begin{bmatrix} \frac{di}{dt} \\ \frac{dv_c}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R}{L} & -\frac{1}{L} \\ \frac{1}{C} & 0 \end{bmatrix} \begin{bmatrix} i \\ v_c \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} x$$

↑ derivatives of states ↑
i & v_c.

- Let $\bar{z}(t) = \begin{bmatrix} i(t) \\ v_c(t) \end{bmatrix}$ be the state vector
a collection of signals (states)
 $z_1 = i \quad z_2 = v_c$

Then $\frac{d\bar{z}}{dt} = A\bar{z} + Bx$ • This is a 2D linear state equation.

$\uparrow$ $\uparrow$
 2x2 matrix vector

★ This state equation is an internal description of the system because z_1 & z_2 correspond to physically interpretable states.

Solving it gives us the time evolution of the states, $\bar{z}(t)$

- Now suppose we wanted to treat the output as the resistor voltage V_R

$$y = V_R = Ri = R z_1(t) \quad \text{is a simple (non-dynamic) function of states.}$$

We call this the output equation.

- In summary an internal description is a state equation and output equation where the states have a physical correspondence to the system.

$$\begin{aligned} \dot{\bar{z}} &= A\bar{z} + Bx \\ y &= C\bar{z} + Dx \end{aligned}$$

for matrix A, C and vector B, D constants.

Note: How to solve these directly in this form is outside the scope of the course.

★ external description.

- Going back to our circuit analysis we had

$$(3) \quad \frac{di}{dt} = -\frac{R}{L} i - \frac{1}{L} V_C + \frac{1}{L} x$$

$$(4) \quad \frac{dV_C}{dt} = \frac{1}{C} i$$

- Suppose we are interested in the cap voltage as the output, $y = V_C$

Then if we take the derivative of (4) and substitute it and (4) into (3) we get.

$$y'' + \frac{R}{L} y' + \frac{1}{LC} y = \frac{1}{LC} x$$

A 2nd order LCCDE in y . This is an external description.

- compare this to the internal description

$$\begin{bmatrix} \dot{i} \\ \dot{V}_C \end{bmatrix} = \begin{bmatrix} -\frac{R}{L} & -\frac{1}{L} \\ \frac{1}{C} & 0 \end{bmatrix} \begin{bmatrix} i \\ V_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} x$$

with output equation

$$y = V_C$$

- we loose the evolution of the state i (con)
- we would have to rederive & resolve the external LCCDE for each new output (con)
- But, you already know how to solve the external case (for some "standard" inputs) (pro)

Summary: - internal descriptions are more detailed but (conceptually) harder to solve
 - external descriptions are easier to solve but loose detail.

- we will focus on external descriptions.
- They agree (almost, see stability lecture) most of time.