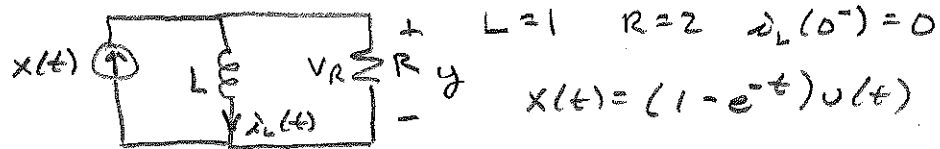


★ Application: Circuit Analysis using Laplace.

Now that we can solve LCDE using Laplace it is obvious that it could be applied to circuits.

Example:



KCL: $i_L + \frac{v_R}{R} = x$ and $v_L = v_R = L i_L'$

$$\frac{1}{R} i_L' + i_L = x \quad \text{or} \quad i_L' + \frac{R}{L} i_L = \frac{R}{L} x$$

substituting values $i_L' + 2 i_L = 2x \quad i_L(0^-)=0$

Take Laplace $s I_L(s) + 2 I_L(s) = 2 X(s)$

Solve for I_L $I_L(s) = \frac{2}{s+2} X(s)$

substitute $X(s) = \frac{1}{s} - \frac{1}{s+1} \Rightarrow I_L(s) = \frac{2}{s(s+2)} - \frac{2}{(s+1)(s+2)}$


$Y(s) = L s I_L(s) = \frac{2}{s+2} - \frac{2s}{(s+1)(s+2)}$ The solution in Laplace Domain.

→ We can save some effort by applying the Laplace transform first.


Resistor: $v(t) = R i(t) \xleftrightarrow{\mathcal{L}} v(s) = R I(s)$

Capacitor: $i(t) = C v'(t) \xleftrightarrow{\mathcal{L}} I(s) = C s V(s) - C v(0^-)$
or equivalently
 $v(s) = \frac{1}{Cs} I(s) + \frac{1}{s} v(0^-)$

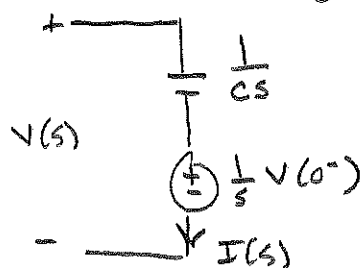These are equivalent to the circuits ← Impedance





Use with KVL

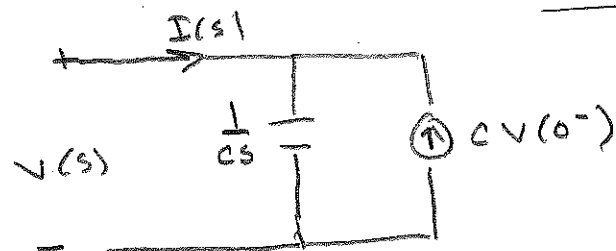


Use with KCL

- Inductor. $v(t) = L i'(t)$

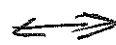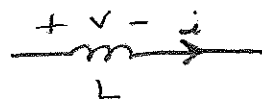


$$V(s) = \underbrace{Ls I(s)}_{\text{Impedance}} - L i(0^-)$$

Equivalent circuits.

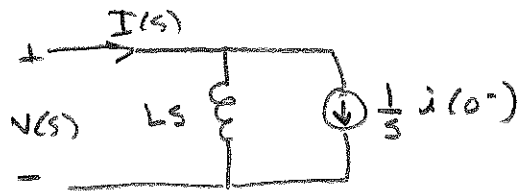

Use with KCL
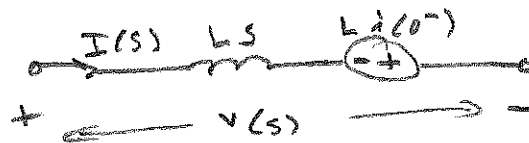
$$\text{or } I(s) = \frac{1}{Ls} V(s) + \frac{1}{s} i(0^-)$$




Use with KVL

Let's redo our example:



- The best model to use is Model I since KCL looks like a good Approach.

OR

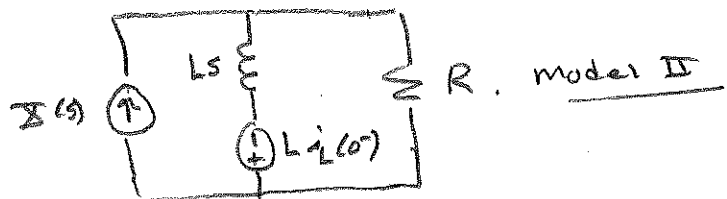

- KCL with Model I

$$X(s) = \frac{Y(s)}{Ls} + \frac{1}{s} i(0^-) + \frac{Y(s)}{R}$$

multiply through by $Rs \Rightarrow Rs X(s) = \frac{R}{L} Y(s) + \frac{R}{L} i(0^-) + s Y(s)$

$$\text{rearranging } (s + \frac{R}{L}) Y(s) = Rs X(s) + \frac{R}{L} i(0^-)$$

$$Y(s) = \frac{Rs}{s + \frac{R}{L}} X(s) + \frac{R}{L} i(0^-)$$

substitute values.

$$Y(s) = \frac{2s}{(s+2)} X(s)$$


$$\text{Substitute } X(s) = \frac{1}{s} - \frac{1}{s+1}$$

$$Y(s) = \frac{2}{s+2} - \frac{2s}{(s+1)(s+2)}$$

The same result,

- Note: This approach is used heavily in AC Circuits where zero-state is usually the case and $x(t)$ are sinusoids.

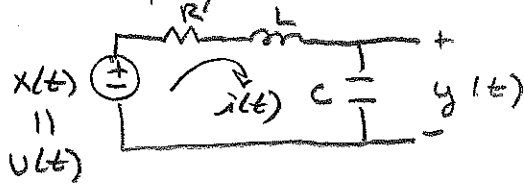
- Lets try another example. series RLC step response with i.c.



$$R = 2 \quad L = \frac{1}{4} \quad C = \frac{1}{3}$$

$$i_L(0^-) = 0 \quad y(0^-) = 2$$

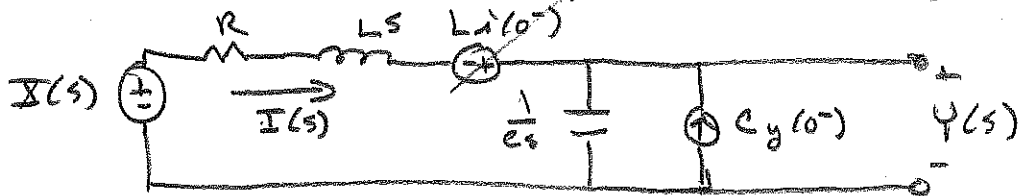Transform the circuit. (what are other choices?)



• KVL: $X(s) = RI(s) + LsI(s) + Y(s)$ (1)

• KCL: $I(s) = \frac{1}{\frac{1}{Cs}} Y(s) - Cy(0^-) = CsY(s) - Cy(0^-)$ (2)

• substituting (2) $\rightarrow$ (1)

$$X(s) = RCsY(s) - RCy(0^-) + LCs^2Y(s) - LCsy(0^-) + Y(s)$$

• collecting terms

$$LCs^2Y(s) + RCsY(s) + Y(s) = X(s) + RCy(0^-) + LCsy(0^-)$$

• divide through by LC

$$s^2Y(s) + \frac{R}{L}sY(s) + \frac{1}{LC}Y(s) = \frac{1}{LC}X(s) + \frac{R}{L}y(0^-) + sy(0^-)$$

or

$$(s^2 + \frac{R}{L}s + \frac{1}{LC})Y(s) = \frac{1}{LC}X(s) + (s + \frac{R}{L})y(0^-)$$

• Substituting values

$$(s^2 + 8s + 12)Y(s) = 12X(s) + 2(s + 8)$$

$$\text{or } Y(s) = \underbrace{\frac{12}{s^2 + 8s + 12} X(s)}_{\text{Zero-state response}} + \underbrace{\frac{2(s + 8)}{s^2 + 8s + 12}}_{\text{Zero-input response}}$$

• when $x(t) = u(t)$

$$X(s) = \frac{1}{s}$$

- Example cont.

Applying input, and $s^2 + 8s + 12$
($s+2$)($s+6$)

$$Y(s) = \frac{12}{s(s+2)(s+6)} + \frac{2(s+8)}{(s+2)(s+6)}$$

- To find $y(t)$ we need to take $\mathcal{L}^{-1}$ of $Y(s)$

• First Term: $\frac{12}{s(s+2)(s+6)} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+6}$

Let's use the "cover up" method to find A, B, C.

$$A = \left. \frac{12(s)}{s(s+2)(s+6)} \right|_{s=0} = \frac{12}{12} = 1$$

$$B = \left. \frac{12(s+2)}{s(s+2)(s+6)} \right|_{s=-2} = \frac{12}{-2(4)} = \frac{12}{-8} = -\frac{3}{2}$$

$$C = \left. \frac{12(s+6)}{s(s+2)(s+6)} \right|_{s=-6} = \frac{12}{-6(-4)} = \frac{12}{24} = \frac{1}{2}$$

• Second Term: $\frac{2(s+8)}{(s+2)(s+6)} = \frac{D}{s+2} + \frac{E}{s+6}$

$$D = \left. \frac{2(s+8)(s+6)}{(s+2)(s+6)} \right|_{s=-2} = \frac{2(6)}{4} = 3$$

$$E = \left. \frac{2(s+8)(s+6)}{(s+2)(s+6)} \right|_{s=-6} = \frac{2(2)}{-4} = -1$$

$$\text{Thus } Y(s) = \frac{1}{s} + \frac{3 - 3/2}{s+2} + \frac{-1 + 1/2}{s+6} = \frac{1}{s} + \frac{3/2}{s+2} + \frac{-1/2}{s+6}$$

using Table:

$$y(t) = \left(1 + \frac{3}{2} e^{-2t} - \frac{1}{2} e^{-6t} \right) u(t)$$

★ Summary: This approach makes Circuit Analysis easier when in zero, state conditions, particular for steady-state analysis.