

problem - 1

$$+ \quad - \quad \downarrow \quad \lambda_0 = \alpha_1 v_{in} + \alpha_2 v_{in}^2$$

$$\alpha_1 = \left(\frac{\partial \lambda_0}{\partial v_{in}} \right)_{v_{in}=0}$$

$$\alpha_2 = \frac{\partial^2 \lambda_0}{\partial v_{in}^2} \times \frac{1}{2}$$

1) THD \rightarrow HD₂

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$

$$\frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) = g_m \rightarrow \alpha_1$$

$$\frac{\partial^2 I_D}{\partial V_{GS}^2} = \mu_n C_{ox} \frac{W}{L} \rightarrow \alpha_2 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L}$$

$$\therefore HD_2 = \frac{1}{2} \frac{\alpha_2}{\alpha_1} V_{peak} = \frac{1}{2} \frac{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})}$$

$$= \frac{1}{4 (V_{GS} - V_{th})}$$

$$2) \left. \begin{aligned} S_{out} &= (g_m V_{in})^2 R_L \\ N_{out} &= (4KT \frac{r}{2} g_m) \cdot R_L \end{aligned} \right\} \frac{S_{out}}{N_{out}} = \frac{g_m}{4KT \frac{r}{2}} V_{in}^2$$

$$3) W/L \uparrow \times \sqrt{2} \rightarrow g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \uparrow \times \sqrt{2}$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \uparrow \times \sqrt{2}$$

$$\therefore (V_{GS} - V_{th}) \downarrow \times \frac{1}{\sqrt{2}}$$

- g_m increased by a factor of $\sqrt{2} \Rightarrow (S/N)_{out} \uparrow \times \sqrt{2}$
- $(V_{GS} - V_{th})$ decreased by a factor of $\sqrt{2} \Rightarrow HD_2 \uparrow \times \sqrt{2}$
- Noise power $\Rightarrow N_{out} \uparrow \times \sqrt{2}$

②

Note: N_{out} increases by a factor of $\sqrt{2}$.
 But signal power also increases by a factor of 2.
 \Rightarrow overall S/N increases by a factor of $\sqrt{2}$.

4) $(V_{GS} - V_{th}) \uparrow \times 2 \rightarrow (W/L) \downarrow \times \frac{1}{4}$

(why: To maintain same current)

$\rightarrow g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \downarrow \times \frac{1}{2}$

- g_m decreases by a factor of 2.

\rightarrow Noise power will be decreased by a factor of 2.

\rightarrow signal power will be decreased by a factor of 4.

$\therefore (S/N)_{out} \downarrow \times \frac{1}{2}$

- $HD_2 \downarrow \times \frac{1}{2}$

NOTE:

From 3) and 4), you can reason that
 Under constant bias current,

① To achieve better NF \rightarrow Increase W/L

② To achieve better linearity \rightarrow Increase $(V_{GS} - V_{th})$.

~~small current density~~
~~per width~~

A few more remarks

① Increasing W/L with constant I_{bias} means

"small current density" for low-noise operation
 per width

② Increasing $(V_{GS} - V_{th})$ with constant I_{bias} means

"large current density" for high-linearity operation.
 per width

~~large current density~~
~~per width~~

$$\begin{aligned}
 5) \quad I_D \uparrow \times 2 &\rightarrow g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \uparrow \times \underline{\underline{\sqrt{2}}} \\
 &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \uparrow \times \underline{\underline{\sqrt{2}}} \\
 &\therefore (V_{GS} - V_{th}) \uparrow \times \underline{\underline{\sqrt{2}}}
 \end{aligned}$$

$$\Rightarrow \left. \begin{array}{l} (V_{out}) \uparrow \times \sqrt{2} \\ (S_{out}) \uparrow \times 2 \end{array} \right\} (S/N)_{out} \uparrow \times \underline{\underline{\sqrt{2}}}$$

$$\Rightarrow HD_2 = \frac{1}{4(V_{GS} - V_{th})} \downarrow \times \underline{\underline{\sqrt{2}}}$$

NOTE:

To achieve better NF and linearity at the same time, bias current needs to be increased


\Rightarrow Trade-off between power and NF, linearity

$$6) \quad THD = HD_2 = \frac{V_{in, max}}{4(V_{GS} - V_{th})} = 0.01$$

$$\therefore V_{in, max} = 0.04 (V_{GS} - V_{th})$$

$$\Rightarrow 4\% \text{ of } (V_{GS} - V_{th})$$

problem-2

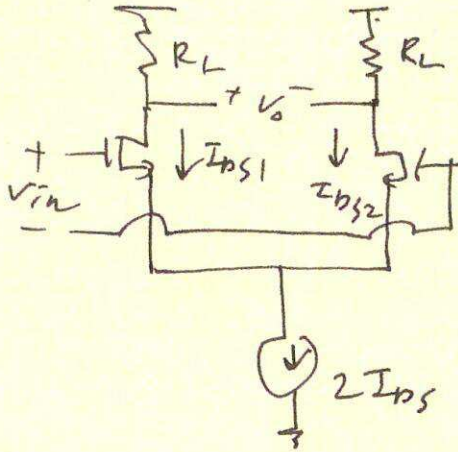

$$i_o = I_{DS1} - I_{DS2}$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{th})^2 - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS2} - V_{th})^2$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left\{ \underbrace{(V_{GS1} - V_{GS2})}_{\text{AC-component} = V_{in}} \underbrace{(V_{GS1} + V_{GS2} - 2V_{th})}_{\text{DC-component}} \right\}$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{GS2}) \left(\sqrt{\frac{2I_{DS1}}{\mu_n C_{ox} \frac{W}{L}}} + \sqrt{\frac{2I_{DS2}}{\mu_n C_{ox} \frac{W}{L}}} \right)$$

$$= \sqrt{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} (V_{GS1} - V_{GS2}) \left(\sqrt{I_{DS1}} + \sqrt{I_{DS2}} \right) \quad \text{--- (1)}$$

$$= I_{DS1} - I_{DS2} = \left(\sqrt{I_{DS1}} + \sqrt{I_{DS2}} \right) \left(\sqrt{I_{DS1}} - \sqrt{I_{DS2}} \right)$$

$$\therefore \sqrt{I_{DS1}} - \sqrt{I_{DS2}} = \sqrt{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} (V_{GS1} - V_{GS2}) \quad \text{--- (2)}$$

From ②,

$$I_{D1} + I_{D2} - 2\sqrt{I_{D1} \cdot I_{D2}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{GS2})^2$$

$$\therefore 2\sqrt{I_{D1} \cdot I_{D2}} = 2I_{D5} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{GS2})^2 \quad - (3)$$

apply

From ①,

$$\begin{aligned} (I_{D1} - I_{D2})^2 &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{GS2})^2 (2I_{D5} + 2\sqrt{I_{D1} \cdot I_{D2}}) \\ &= 2I_{D5} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{GS2})^2 \\ &= \frac{1}{4} \left(\mu_n C_{ox} \frac{W}{L} \right)^2 (V_{GS1} - V_{GS2})^4 \end{aligned}$$

$$\therefore I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{GS2}) \sqrt{\frac{8I_D}{\mu_n C_{ox} \frac{W}{L}} - (V_{GS1} - V_{GS2})^2} \quad - (4)$$

From ④, $I_{D1} - I_{D2} = i_o$
 $V_{GS1} - V_{GS2} = v_{in}$

$$\therefore i_o = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{in} \sqrt{\frac{8I_D}{\mu_n C_{ox} \frac{W}{L}} - v_{in}^2} \quad - (5)$$

$$\begin{aligned} \therefore \text{overall } G_m &= \left(\frac{\partial i_o}{\partial v_{in}} \right)_{v_{in}=0} \\ &= \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{8I_D}{\mu_n C_{ox} \frac{W}{L}} - 2v_{in}^2}{\sqrt{\frac{8I_D}{\mu_n C_{ox} \frac{W}{L}} - v_{in}^2}} \right)_{v_{in}=0} \\ &= \sqrt{\mu_n C_{ox} \frac{W}{L} \cdot 2I_D} \end{aligned}$$

From (5),

$$i_o = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{in} \sqrt{\frac{8 I_D}{\mu_n C_{ox} \frac{W}{L}} - V_{in}^2}$$

$$V_{GS} = \frac{V_{GS1} + V_{GS2}}{2} \leftarrow \text{DC-Bias of NMOS voltage}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2 \quad \text{applying}$$

$$\Rightarrow i_o = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{in} \sqrt{4(V_{GS} - V_{th})^2 - V_{in}^2}$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) V_{in} \sqrt{1 - \frac{V_{in}^2}{4(V_{GS} - V_{th})^2}}$$

(if) $V_{in} \ll 2(V_{GS} - V_{th})$

$\downarrow \sqrt{1-x} \approx 1 - \frac{x}{2}$

$$\approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) V_{in} \left(1 - \frac{V_{in}^2}{8(V_{GS} - V_{th})^2} \right)$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \left(V_{in} - \frac{1}{8(V_{GS} - V_{th})^2} V_{in}^3 \right)$$

$$\Rightarrow \alpha_1 = g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})$$

$$\alpha_2 = 0$$

$$|\alpha_3| = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \frac{1}{8(V_{GS} - V_{th})^2}$$

$$1) THD = HD_3 = \frac{1}{4} \frac{|\alpha_3|}{\alpha_1} V_{peak}^2$$

$$= \frac{1}{4} \cdot \frac{1}{8(V_{GS} - V_{th})^2} = \frac{1}{32(V_{GS} - V_{th})^2}$$

$$2) S_{out} = g_m (G_m \cdot V_{in})^2 R_L$$

$$N_{out} = 4KT \frac{r}{\alpha} G_m \times 2 \times R_L$$

Because of 2 transistors.

$$(S/N)_{out} = \frac{G_m}{8KT \frac{r}{\alpha}} V_{in}^2$$

because of two transistors.

$$3) W/L \uparrow \times 2 \rightarrow G_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \uparrow \times \sqrt{2}$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \uparrow \times \sqrt{2}$$

$$\Rightarrow N_{out} \uparrow \times \sqrt{2}$$

$$\therefore (V_{GS} - V_{th}) \downarrow \frac{1}{\sqrt{2}}$$

$$\Rightarrow (S/N)_{out} \uparrow \times \sqrt{2}$$

$$\Rightarrow HD_3 \uparrow \times 2$$

compare this result with that of single-ended case.

To maintain same bias current.

$$4) (V_{GS} - V_{th}) \uparrow \times 2 \rightarrow W/L \downarrow \times \frac{1}{4}$$

$$\rightarrow G_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \downarrow \frac{1}{2}$$

$$\Rightarrow N_{out} \downarrow \times \frac{1}{2}$$

$$\Rightarrow (S/N)_{out} \downarrow \times \frac{1}{2}$$

$$\Rightarrow HD_3 \downarrow \times \frac{1}{4}$$

compare this result with that of single-ended case.

$$\begin{aligned}
 5) I_D \uparrow \times 2 &\rightarrow g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \uparrow \times \sqrt{2} \\
 &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \uparrow \times \sqrt{2} \\
 &\therefore (V_{GS} - V_{th}) \uparrow \times \sqrt{2}
 \end{aligned}$$

$$\Rightarrow N_{out} \uparrow \times \sqrt{2}$$

$$\Rightarrow (S/N)_{out} \uparrow \times \sqrt{2}$$

$$\Rightarrow HD_3 \downarrow \times \frac{1}{2}$$

$$\begin{aligned}
 6) THD = HD_3 &= \frac{1}{4} \frac{|a_3|}{a_1} \times V_{in, max}^2 \\
 &= \frac{V_{in, max}^2}{32 (V_{GS} - V_{th})^2} = 0.01
 \end{aligned}$$

$$\begin{aligned}
 \therefore V_{in, max} &= \sqrt{0.01 \times 32} \cdot (V_{GS} - V_{th}) \\
 &\approx 0.57 (V_{GS} - V_{th}) \\
 &\Rightarrow 57\% \text{ of } (V_{GS} - V_{th})
 \end{aligned}$$

↑
Compare this with single-ended case

NOTE:

Differential topology can achieve much better linearity over wide input range compared with single-ended topology.