

Therefore equivalent input noise voltage to create this noise current is

$$\overline{V_{n_{eq}}} \cdot \frac{\frac{g_m}{s C_{gs}}}{R_s + R_g + \frac{1}{s C_{gs}} + \left(1 + \frac{g_m}{s C_{gs}}\right) \cdot S L_s} = \hat{i}_{no} \Big|_{\text{due to } \hat{i}_{nd}}$$

$$\Rightarrow \overline{V_{n_{eq}}} = \frac{\left(\frac{\hat{i}_{in2}}{\hat{i}_{in1} // S L_s + \hat{i}_{in2}} \cdot \overline{\hat{i}_{nd}} \right)}{\left(\frac{\frac{g_m}{s C_{gs}}}{R_s + R_g + \frac{1}{s C_{gs}} + \left(1 + \frac{g_m}{s C_{gs}}\right) \cdot S L_s} \right)}$$



if $|\hat{i}_{in1}| \gg \omega L_s$

$$\Rightarrow = \frac{\frac{1 + s C_{gs} R_s}{g_m S L_s + 1 + s C_{gs} R_s} \cdot \overline{\hat{i}_{nd}}}{\frac{g_m}{s C_{gs}}}$$

$$\downarrow \text{if } |1 + j \omega C_{gs} \cdot R_s| \gg g_m \cdot \omega L_s$$

$$\approx \frac{1}{g_m} \left(1 + s C_{gs} \left(R_s + \frac{g_m L_s}{C_{gs}} \right) \right) \overline{\hat{i}_{nd}}$$

\therefore Input referred noise voltage, $\overline{V_{n_{in}}}$

$$\overline{V_{n_{in}}} = \overline{V_{n_g}} + \overline{V_{n_{eq}}}$$

$$\approx \overline{V_{n_g}} + \overline{\hat{i}_{nd}} \cdot \frac{1}{g_m} \left(1 + s C_{gs} \left(R_s + \frac{g_m L_s}{C_{gs}} \right) \right)$$