

3) correlation admittance

$$Y_c = \frac{\overline{V_{neg}}^* \overline{i_{neg}}}{\overline{V_{neg}}^2}$$

$$\approx j\omega C_{gs} \leftarrow \text{same as without } L_s \text{ (see lecture note, page-65)}$$

4) Uncorrelated noise current

$$\overline{i_{nu}} = \overline{i_{neg}} - Y_c \overline{V_{neg}}$$

$$= -j\omega C_{gs} \overline{V_{ng}} \leftarrow \text{see lecture note, page-65}$$

correlated noise current

$$\overline{i_{nc}} = \overline{i_{neg}} - \overline{i_{nu}}$$

4) Optimum admittance

$$Y_{opt} = \omega C_{gs} \sqrt{\frac{g_m R_g}{r}} - j\omega C_{gs} \leftarrow \text{see lecture note page-66}$$

5) F_{min}

$$F_{min} = 1 + 2\omega C_{gs} \sqrt{r \frac{R_g}{g_m}} \leftarrow \text{see lecture note page-67.}$$

Think about why these results are same as in the case of without source inductor