

---


# ECE 5220 RFIC HW -3

(Due: 03/19/2012, Hand in by the end of class time,  
10:45AM)

---

**Homework will not be acceptable after the class.**

## Problem-1: Single-ended amplifier

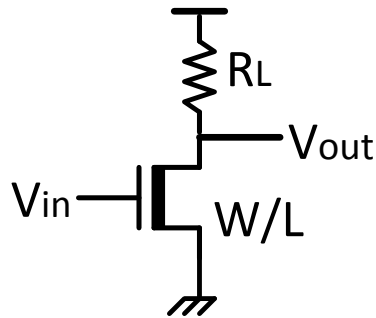


\* From this question, you can think about sizing of a transistor and trade-offs between linearity, noise figure and power consumption.

Assume that DC bias current is determined by square-law characteristic, i.e.,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2.$$

- 1) Calculate THD when  $V_{in} = \cos \omega t$ .
- 2) Calculate output SNR (assumption: the only noise source is drain thermal current noise).
- 3) If we increase  $W/L$  twice while maintaining same bias current  $I_D$ , how much increase (or decrease) in THD, noise power and SNR?
- 4) If we increase overdriving voltage ( $V_{GS} - V_{th}$ ) twice while maintaining same bias current  $I_D$ , how much increase (or decrease) in THD, noise power and SNR?
- 5) If we maintain  $W/L$  same and increase  $I_D$  twice, how much increase (or decrease) in THD, noise power and SNR?
- 6) Express maximum  $V_{in}$  (in terms of the overdriving voltage) which allows less than 1% of THD.

## Problem-2: Differential amplifier

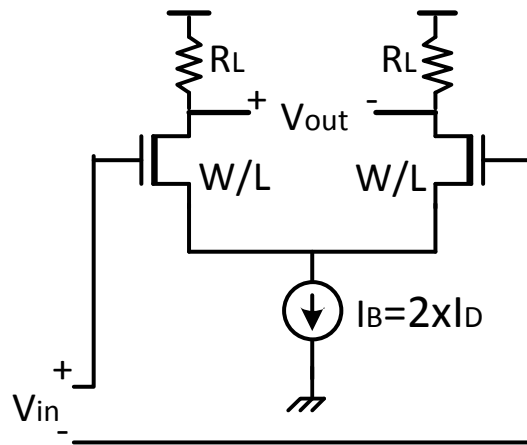

\* Think about which topology between single-ended and differential is better for each of noise and linearity perspective.

Assume that DC bias current for each transistor is determined by square-law characteristic, i.e.,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2, \\ V_{in} \ll V_{GS} - V_{th}$$

- 1) Calculate THD when  $V_{in} = \cos \omega t$   
(use approximation of  $\sqrt{1-x} \approx 1 - \frac{x}{2}$  if  $x \ll 1$ )
- 2) Calculate output SNR (assumption: the only noise source is drain thermal current noise).
- 3) If we increase W/L twice while maintaining same bias current  $I_B$ , how much increase (or decrease) in THD, noise power and SNR?
- 4) If we increase overdriving voltage ( $V_{GS} - V_{th}$ ) twice while maintaining same bias current  $I_B$ , how much increase (or decrease) in THD, noise power and SNR?
- 5) If we maintain W/L same and increase  $I_B$  twice, how much increase (or decrease) in THD, noise power and SNR?
- 6) Express maximum  $V_{in}$  (in terms of the overdriving voltage) which allows less than 1% of THD.