


ECE4220 Class Project #3

Due Date: Dec. 4th (by class time)
Full Credit: 100-pt

Instructor: Dr. Kwang-Jin Koh
ECE Dept. Virginia Tech

Email: kkoh@vt.edu

Common-Mode Feedback Design (1)

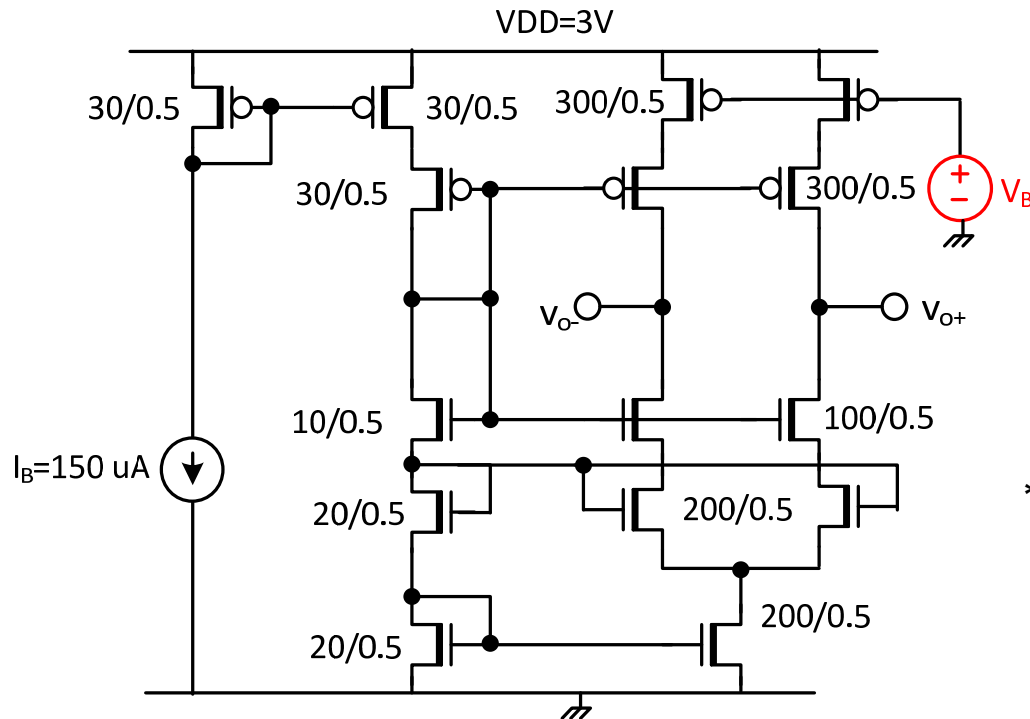


Configure a cascode differential amplifier schematic as shown. Use ideal current source for I_B (note: in real design, I_B will be generated by a bandgap reference typically).

- Q-1) Sweep V_B and find the range of V_B where all the transistors can operate in saturation mode (5 pt).


*You should observe how sensitive of node bias points to V_B .

Common-Mode Feedback Design (2)

 

- Q-2) Set V_B to a specific value within the range you determine in Q-1. Then apply common-mode input DC, $V_{i,DC}$, and sweep it. What's the common-mode input DC range where all the transistors can operate in saturation mode (5pt).

Common-Mode Feedback Design (3)

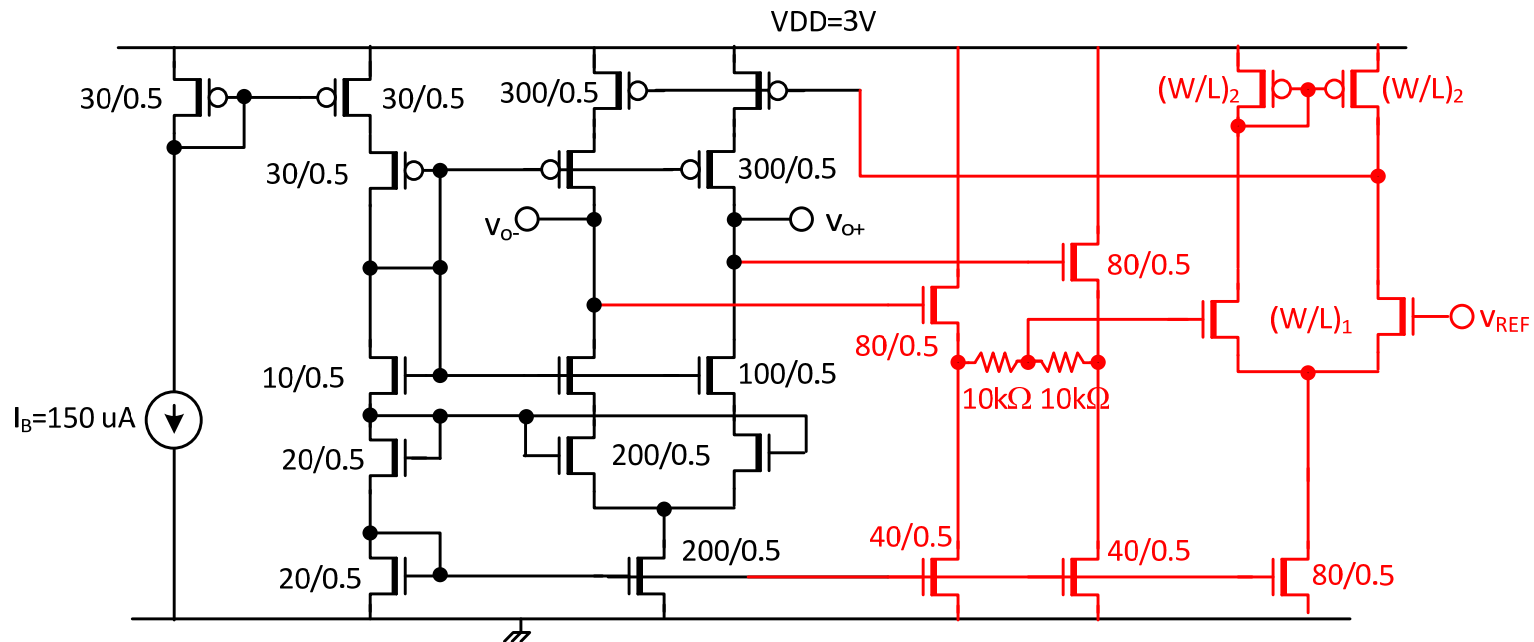


- Q-3) Now, let's design common-mode DC feedback circuits. Set the size of $(W/L)_1$ and $(W/L)_2$ and determine range of V_{REF} so that all transistors can operate in saturation mode (10 pt).

The schematic shows a 10-bit SAR ADC. It features a 3V supply (VDD=3V) and a bias current source $I_B = 150 \mu A$. The circuit includes a network of PMOS and NMOS transistors with various (W/L) ratios (e.g., 30/0.5, 300/0.5, 100/0.5, 200/0.5, 80/0.5, 40/0.5). A feedback loop is formed by a DAC core consisting of a resistor ladder (two $10k\Omega$ resistors) and a DAC output node connected to the input of the SAR logic. The SAR logic includes a comparator and a digital-to-analog converter (DAC) for the feedback. The output of the ADC is V_{O+} , and the reference voltage is V_{REF} . The input signal is $V_{i,DC}$.


- 5

Uncompensated 2-stage OP-Amp (1)

 

- ❑ Q-5) Let's design 2-stage op-amp, and set $C_L=1\text{ pF}$. Calculate and simulate voltage gain ($A_v = \frac{V_o}{V_i}$) (5 pt).
- ❑ Q-6) Calculate dominant pole frequency (ω_{p1}), second pole frequency (ω_{p2}) and dominant positive zero frequency (ω_z). Compare your calculations with simulations (5 pt).


Uncompensated 2-stage OP-Amp (2)

 

Now, let's assume that you are applying unity feedback as shown in the figure. **Note that unity feedback is the worst case feedback when you consider stability. And you should design stability (i.e., compensate op-amp) to guarantee > 60 -deg of phase margin in this worst case feedback.**


- Q-7) Simulate voltage gain ($A_v = \frac{V_o}{V_i}$). Do you observe any peaking in the A_v ? If yes, why? Simulate loop-gain (T) and phase margin (ϕ_M) (10 pt).

OP-Amp Frequency Compensation (1)

 


- Q-8) Determine (Calculate) C_C and R_Z so that $\phi_M \sim 45$ deg. Calculate dominant pole (ω_{p1}), second pole (ω_{p2}) and dominant zero (ω_z). What's the unity gain frequency (ω_u)? Verify your calculation through simulation (20 pt).

OP-Amp Frequency Compensation (2)

 


- Q-9) Set C_C and R_Z as in Q-7, and then apply unity feedback. Simulate voltage gain ($A_v = \frac{V_o}{V_i}$). Do you observe any peaking in the A_v ? (5 pt).

OP-Amp Frequency Compensation (3)

 

- Q-10) Determine (Calculate) C_C and R_Z so that $\phi_M \sim 80$ deg. Calculate dominant pole (ω_{p1}), second pole (ω_{p2}) and dominant zero (ω_z). What's the unity gain frequency (ω_u)? Verify your calculation through simulation (10 pt).


OP-Amp Frequency Compensation (4)

 

- Q-11) Set C_C and R_Z as in Q-8, and then apply unity feedback. Simulate voltage gain ($A_v = \frac{V_o}{V_i}$). Do you observe any peaking in the A_v ? (5 pt).

OP-Amp Application: Linear Regulator (1)

 
**** This is an example to generate 1.8 V from 3 V supply voltage.**



Note: $V_{n,vdd}$ and $V_{n,vss}$ could represent a low-frequency supply noise and ground noise, respectively. You should observe that these low-frequency noise will be suppressed by the feedback loop-gain in the simulation. \Rightarrow Alternatively speaking, VDD and GND will be **regulated** by the feedback loop.

OP-Amp Application: Linear Regulator (2)

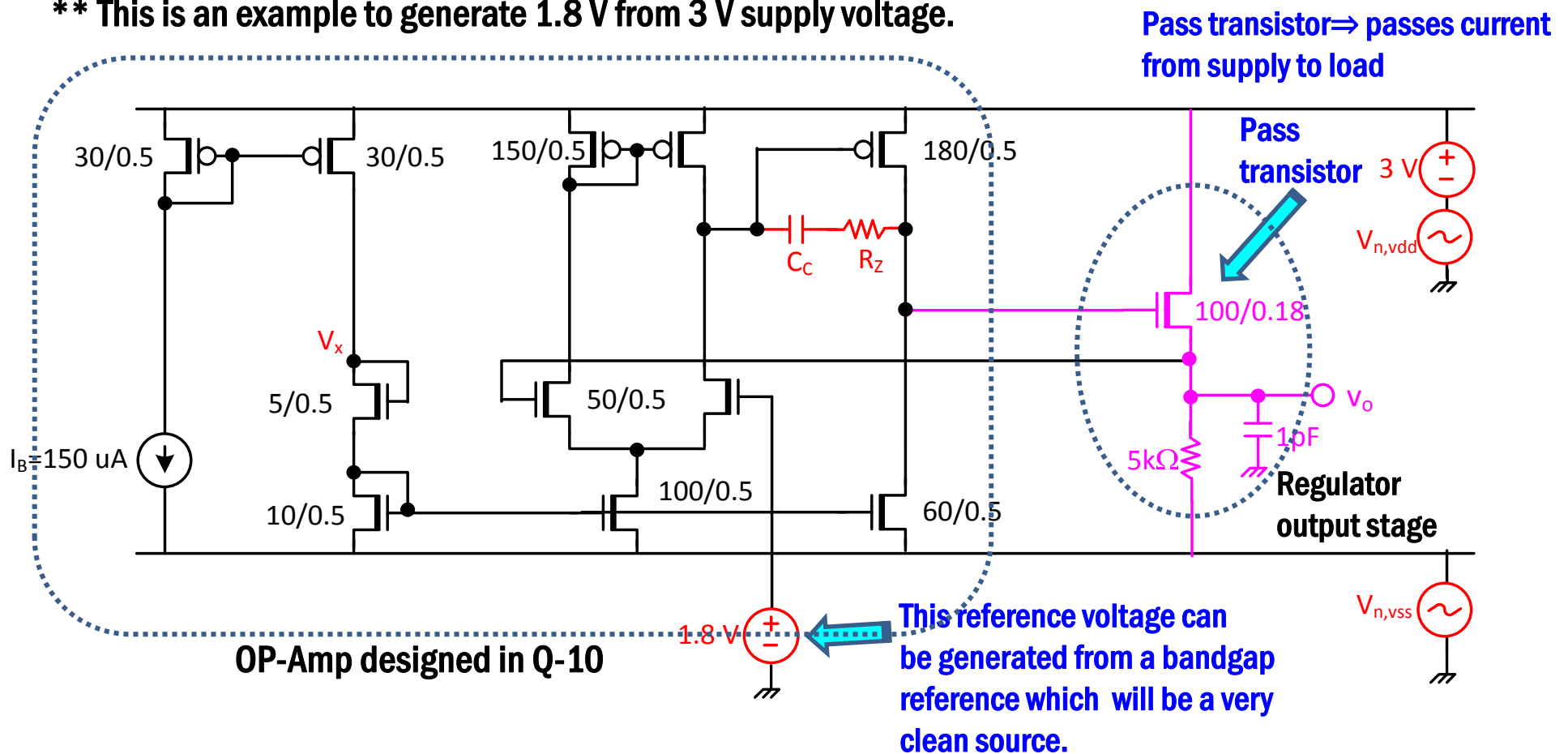**** This is an example to generate 1.8 V from 3 V supply voltage.**



□ Q-12) Set $V_{n,vss}=0$ and simulate voltage gain, $A_{v,nvdd} = \frac{V_o}{V_{n,vdd}}$ (Note: $1/A_{v,nvdd}$ is PSRR+) (5 pt).

□ Q-13) Set $V_{n,vdd}=0$ and simulate voltage gain, $A_{v,nvss} = \frac{V_o}{V_{n,vss}}$ (Note: $1/A_{v,nvss}$ is PSRR-) (5 pt).