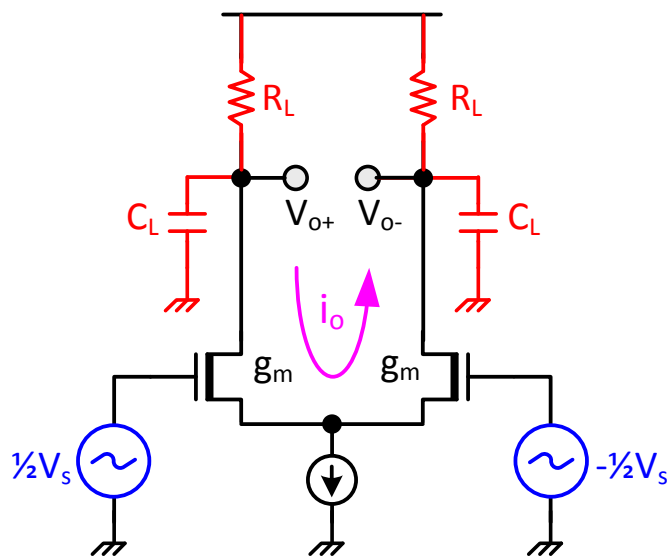


# Differential Amplifier: Frequency Response

- ❑ In typical analog systems, input is driven by another feedback amplifier which has very low source impedance. Therefore, input node becomes non-significant parasitic pole in most cases.
- ❑ Dominant pole (3-dB BW) is determined by a load pole (load resistance and capacitance).



$$\frac{v_{o+}}{v_s} = \underbrace{\left(-\frac{1}{2}g_m R_L\right)}_{DC-gain} \underbrace{\left(\frac{1}{1 + \frac{s}{\omega_p}}\right)}_{Pole-frequency}, \omega_p = \frac{1}{R_L C_L}$$


$$\frac{v_{o-}}{v_s} = \underbrace{\left(+\frac{1}{2}g_m R_L\right)}_{DC-gain} \underbrace{\left(\frac{1}{1 + \frac{s}{\omega_p}}\right)}_{Pole-frequency}, \omega_p = \frac{1}{R_L C_L}$$

$$A_v = \frac{v_{o+} - v_{o-}}{v_s} = \frac{v_{o+}}{v_s} - \frac{v_{o-}}{v_s} = \underbrace{\left(-g_m R_L\right)}_{DC-gain} \underbrace{\left(\frac{1}{1 + \frac{s}{\omega_p}}\right)}_{Pole-frequency}, \omega_p = \frac{1}{R_L C_L}$$

- ❑ With perfectly matched loads, differential amplifier will have one pole.
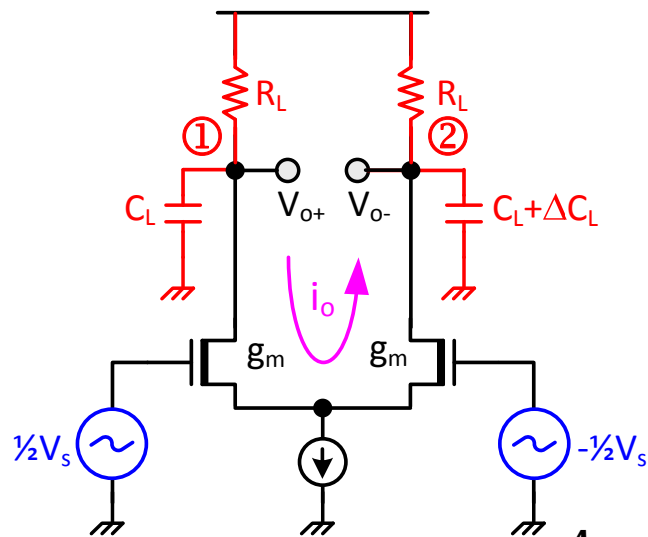
# Differential Amplifier: Pole-Zero Doublet (1)

- ❑ What happens if the load are not matched exactly ?
- ❑ Let's assume that the load capacitances have a slight mismatch of  $\Delta C_L$ .



$$\frac{v_{o+}}{v_s} = \underbrace{\left(-\frac{1}{2}g_m R_L\right)}_{\text{DC-gain}} \underbrace{\left(\frac{1}{1 + \frac{s}{\omega_{p1}}}\right)}_{\text{Pole-frequency at node ①}}, \omega_{p1} = \frac{1}{R_L C_L}$$


$$\frac{v_{o-}}{v_s} = \underbrace{\left(+\frac{1}{2}g_m R_L\right)}_{\text{DC-gain}} \underbrace{\left(\frac{1}{1 + \frac{s}{\omega_{p2}}}\right)}_{\text{Pole-frequency at node ②}}, \omega_{p2} = \frac{1}{R_L C_L \left(1 + \frac{\Delta C_L}{C_L}\right)}$$

$$A_v = \frac{v_{o+} - v_{o-}}{v_s} = \frac{v_{o+}}{v_s} - \frac{v_{o-}}{v_s} = \left(-\frac{1}{2}g_m R_L\right) \left(\frac{1}{1 + \frac{s}{\omega_{p1}}} + \frac{1}{1 + \frac{s}{\omega_{p2}}}\right)$$

$$= (-g_m R_L) \left( \frac{1 + s \frac{1}{2} \left( \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)} \right) = \underbrace{(-g_m R_L) \left( \frac{1}{1 + \frac{s}{\omega_{p1}}} \right)}_{\text{original response without mismatch}} \underbrace{\left( \frac{1 + s \frac{1}{2} \left( \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right)}{\left(1 + \frac{s}{\omega_{p2}}\right)} \right)}_{\text{additional pole-zero pair due to mismatch}}$$
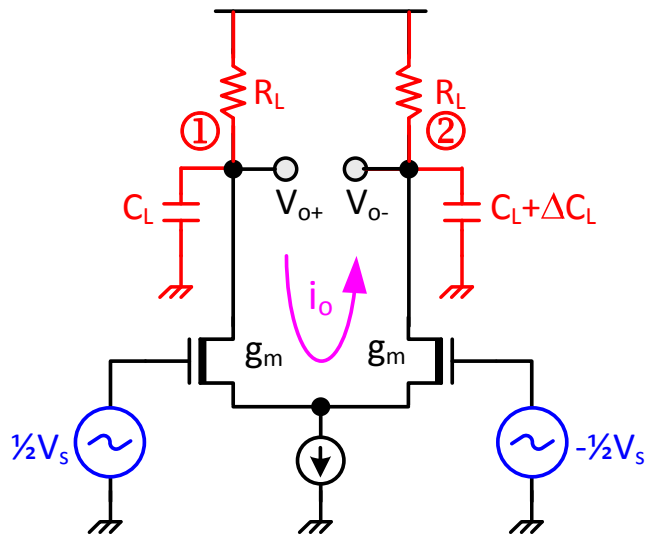
# Differential Amplifier: Pole-Zero Doublet (2)

- ❑ From previous result, mismatch generates another pole-zero pair called as “doublet”.
- ❑ But most typical cases of differential amplifier designs , mismatch is very small enough to be negligible,  $\omega_{p1} \approx \omega_{p2}$ .



$$A_v = \underbrace{(-g_m R_L) \left( \frac{1}{1 + \frac{s}{\omega_{p1}}} \right)}_{\text{original response without mismatch}} \underbrace{\left( \frac{1 + s \frac{1}{2} \left( \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right)}{\left( 1 + \frac{s}{\omega_{p2}} \right)} \right)}_{\text{additional pole-zero pair due to mismatch called "doublet"}}$$


$$A_v \approx \underbrace{(-g_m R_L) \left( \frac{1}{1 + \frac{s}{\omega_{p1}}} \right)}_{\text{original response without mismatch}} \underbrace{\left( \frac{1 + s \frac{1}{2} \left( \frac{1}{\omega_{p2}} + \frac{1}{\omega_{p2}} \right)}{\left( 1 + \frac{s}{\omega_{p2}} \right)} \right)}_{\text{typical differential amplifiers, } \omega_{p1} \approx \omega_{p2}}$$

$$= (-g_m R_L) \left( \frac{1}{1 + \frac{s}{\omega_{p1}}} \right)$$

- ❑ Key observation here is that “Any mismatch in differential amplifier loads will generate another pole-zero pair (doublet)”.
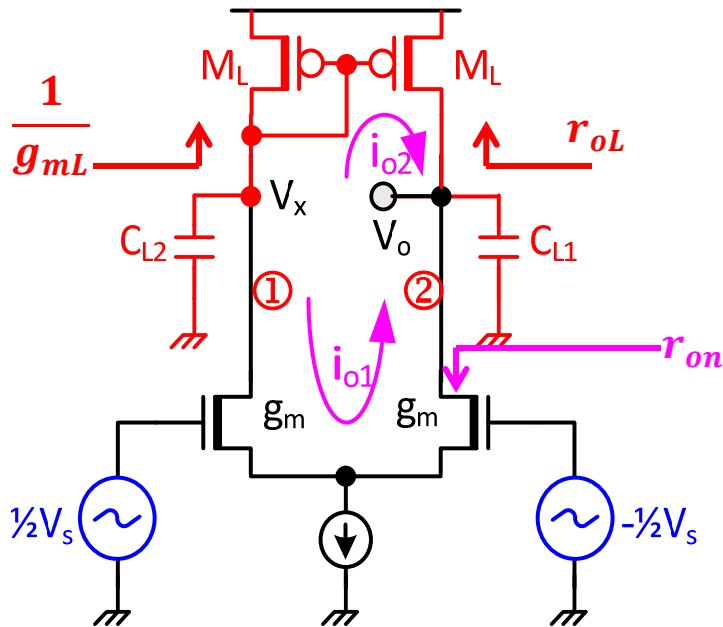
# Differential Amplifier with Active Load (1)

□ Differential amplifier with active loading is **heavily mismatched case**  $\Rightarrow$  “pole-zero doublet”.



$$v_x = i_{o1} \times \frac{1}{g_{mL}} \times \underbrace{\left( \frac{1}{1 + \frac{s}{\omega_{px}}} \right)}_{\text{Pole-frequency at node ①}}, \omega_{px} = \frac{g_{mL}}{C_{L2}}$$


$$\begin{aligned} i_{o2} &= g_{mL} \times v_x \\ &= g_{mL} \times \left[ i_{o1} \times \frac{1}{g_{mL}} \times \left( \frac{1}{1 + \frac{s}{\omega_{px}}} \right) \right] \\ &= i_{o1} \left( \frac{1}{1 + \frac{s}{\omega_{px}}} \right) \end{aligned}$$

$$v_o = (i_{o1} + i_{o2}) \times (r_{on} \parallel r_{oL}) \times \underbrace{\left( \frac{1}{1 + \frac{s}{\omega_p}} \right)}_{\text{Pole-frequency at node ②}}, \omega_p = \frac{1}{(r_{on} \parallel r_{oL}) C_{L1}}$$

$$\begin{aligned} &= i_{o1} (r_{on} \parallel r_{oL}) \times \left( 1 + \frac{1}{1 + \frac{s}{\omega_{px}}} \right) \left( \frac{1}{1 + \frac{s}{\omega_p}} \right) \\ &= 2i_{o1} (r_{on} \parallel r_{oL}) \times \frac{\left( 1 + \frac{s}{2\omega_{px}} \right)}{\left( 1 + \frac{s}{\omega_p} \right) \left( 1 + \frac{s}{\omega_{px}} \right)} \end{aligned}$$
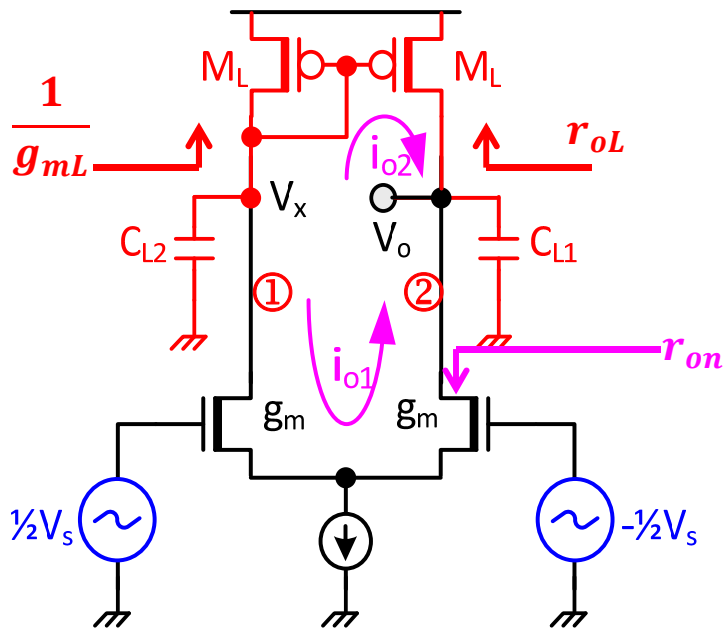
# Differential Amplifier with Active Load (2)

□ Differential amplifier with active loading is **heavily mismatched case**  $\Rightarrow$  “pole-zero doublet”.



$$v_o = 2i_{o1}(r_{on} \parallel r_{oL}) \times \frac{\left(1 + \frac{s}{2\omega_{px}}\right)}{\left(1 + \frac{s}{\omega_p}\right) \left(1 + \frac{s}{\omega_{px}}\right)}$$

zero-frequency =  $2 \times$  pole at node ①

Pole-frequency at output node

Second pole-frequency from node ①

“pole-zero doublet”

□ In differential amplifier with active-load,

1) Output node contributes dominant pole

2) Non-dominant pole (the second pole) comes from the other path

3) There is a zero frequency which is 2x larger than the non-dominant pole frequency.

$\Rightarrow$  2-pole & 1-zero system

□ Note that 2x frequency difference is often regarded as “close frequency”, and the system can be approximated as one-pole system frequently.