

1) Equivalent input noise generators.

① Computing $\overline{v_{neq}} \Rightarrow$ short input to ground.

From original circuit, output noise ~~voltage~~ ^{current} is

$$\overline{i_{on}} = \overline{v_{ng}} \cdot \frac{g_m}{1 + g_m S L_s} + \overline{i_{ind}} \cdot \frac{\frac{1}{g_m}}{\frac{1}{g_m} + S L_s}$$

$$= \frac{1}{1 + g_m S L_s} (\overline{v_{ng}} g_m + \overline{i_{ind}}) \quad \text{--- (A)}$$

From model, output noise current is

$$\overline{i_{on}} = \overline{v_{neq}} \frac{g_m}{1 + g_m S L_s} \quad \text{--- (B)}$$

\Rightarrow From (A) and (B),

$$\overline{v_{neq}} = \overline{v_{ng}} + \frac{\overline{i_{ind}}}{g_m}$$

② Computing $\overline{i_{n\text{eq}}} \Rightarrow$ open input node.

From original circuit, output noise current is

$$\overline{i_{on}} = \overline{i_{nd}} \quad \text{--- (A)}$$


From model, output noise current is

$$\overline{i_{on}} = \overline{i_{n\text{eq}}} \cdot \frac{1}{sC_{gs}} \cdot g_m \quad \text{--- (B)}$$

\Rightarrow From (A) and (B)

$$\overline{i_{n\text{eq}}} = \overline{i_{nd}} \cdot \frac{sC_{gs}}{g_m} = \overline{i_{nd}} \frac{j\omega C_{gs}}{g_m}$$

2) Input referred noise voltage

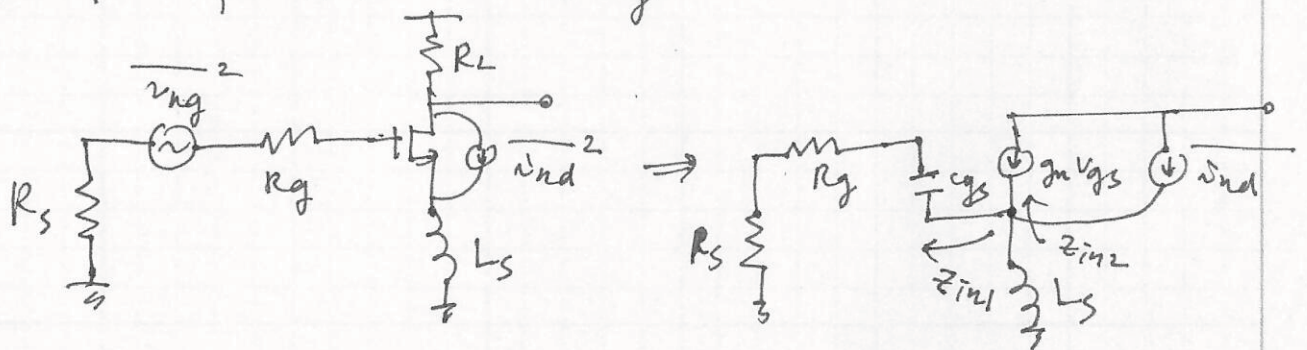

From equivalent circuit shown in ~~the~~ right side,

$$Z_{in1} = \frac{1}{sC_{gs}} + R_g + R_s \approx \frac{1}{sC_{gs}} + R_s$$

$$Z_{in2} = \frac{\frac{1}{sC_{gs}} + R_s + R_g}{\frac{g_m}{sC_{gs}}} \approx \frac{1 + sC_{gs}R_s}{g_m}$$

\Rightarrow Output ^{noise} Current due to $\overline{i_{nd}}$ is

$$\overline{i_{no}} \Big|_{\text{due to } \overline{i_{nd}}} = \frac{Z_{in2}}{Z_{in1} \parallel sL_s + Z_{in2}} \cdot \overline{i_{nd}}$$

Therefore equivalent input noise voltage to create this noise current is

$$\overline{V_{n_{eq}}} \cdot \frac{\frac{g_m}{s C_{gs}}}{R_s + R_g + \frac{1}{s C_{gs}} + \left(1 + \frac{g_m}{s C_{gs}}\right) \cdot s L_s} = \hat{i}_{no} \Big|_{\text{due to } \hat{i}_{nd}}$$

$$\Rightarrow \overline{V_{n_{eq}}} = \frac{\left(\frac{\hat{i}_{in2}}{\hat{i}_{in1} // s L_s + \hat{i}_{in2}} \cdot \overline{\hat{i}_{nd}} \right)}{\left(\frac{\frac{g_m}{s C_{gs}}}{R_s + R_g + \frac{1}{s C_{gs}} + \left(1 + \frac{g_m}{s C_{gs}}\right) \cdot s L_s} \right)}$$



(if $|\hat{i}_{in1}| \gg \omega L_s$)

\Rightarrow

$$\frac{1 + s C_{gs} R_s}{g_m s L_s + 1 + s C_{gs} R_s} \cdot \overline{\hat{i}_{nd}}$$

$$\frac{\frac{g_m}{s C_{gs}}}{R_s + \frac{g_m L_s}{C_{gs}} + \frac{1}{s C_{gs}}}$$

$$\downarrow \text{if } |1 + j \omega C_{gs} R_s| \gg g_m \cdot \omega L_s$$

$$\approx \frac{1}{g_m} \left(1 + s C_{gs} \left(R_s + \frac{g_m L_s}{C_{gs}} \right) \right) \overline{\hat{i}_{nd}}$$

\therefore Input referred noise voltage, $\overline{V_{n, in}}$

$$\overline{V_{n, in}} = \overline{V_{n_g}} + \overline{V_{n_{eq}}}$$

$$\approx \overline{V_{n_g}} + \overline{\hat{i}_{nd}} \cdot \frac{1}{g_m} \left(1 + s C_{gs} \left(R_s + \frac{g_m L_s}{C_{gs}} \right) \right)$$

3) correlation admittance

$$Y_c = \frac{\overline{V_{neg}}^* \overline{i_{neg}}}{\overline{V_{neg}}^2}$$

$$\approx j\omega C_{gs} \leftarrow \text{same as without } L_s \text{ (see lecture note, page-65)}$$

4) Uncorrelated noise current

$$\overline{i_{nu}} = \overline{i_{neg}} - Y_c \overline{V_{neg}}$$

$$= -j\omega C_{gs} \overline{V_{ng}} \leftarrow \text{see lecture note, page-65}$$

correlated noise current

$$\overline{i_{nc}} = \overline{i_{neg}} - \overline{i_{nu}}$$

4) Optimum admittance

$$Y_{opt} = \omega C_{gs} \sqrt{\frac{g_m R_g}{r}} - j\omega C_{gs} \leftarrow \text{see lecture note page-66}$$

5) F_{min}

$$F_{min} = 1 + 2\omega C_{gs} \sqrt{r \frac{R_g}{g_m}} \leftarrow \text{see lecture note page-67.}$$

Think about why these results are same as in the case of without source inductor