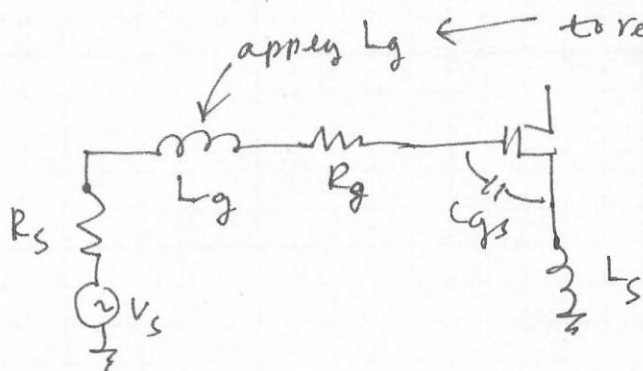


$$4) \quad Z_{in} = \underbrace{R_g + \frac{g_m L_s}{C_{gs}}}_{= R_s} + \underbrace{s L_s + \frac{1}{s C_{gs}}}_{\text{Since } \omega_0 L_s < \frac{1}{\omega_0 C_{gs}}, \text{ we need inductance to resonate the capacitance.}}$$



$$\omega_0 (L_g + L_s) = \frac{1}{\omega_0 C_{gs}}$$

$$\therefore L_g = \frac{1}{\omega_0^2 C_{gs}} - L_s$$

5) Under matched condition

$$\hat{i}_g = \frac{V_s}{2R_s} \rightarrow V_{gs} = \hat{i}_g \frac{1}{s C_{gs}} = \frac{1}{2R_s s C_{gs}} \cdot V_s$$

$$\rightarrow \hat{i}_{out} = g_m V_{gs} = \hat{i}_g \cdot \beta$$

$$= \frac{V_s}{2R_s} \cdot \frac{g_m}{s C_{gs}}$$

$$6) \quad A_v = \frac{V_{out}}{V_s} = \frac{-\hat{i}_{out} \cdot R_L}{V_s} = - \frac{1}{2R_s} \cdot \frac{g_m}{s C_{gs}} \cdot R_L$$

$\Rightarrow$  Under matched condition, gain will be increased by a factor of  $\left(1 + \frac{s L_s + \frac{1}{s C_{gs}}}{2R_s}\right)$ .

$$\Rightarrow 1 + \frac{s L_s + \frac{1}{s C_{gs}}}{2R_s} = 1 - \frac{s L_g}{2R_s} = 1 - j \frac{1}{2} \frac{\omega_0 L_g}{R_s} \approx 1 - j \frac{1}{2} Q$$

$\therefore$  if  $Q$  is large enough, the gain factor is  $\frac{1}{2} Q$ , where  $Q$  is quality factor of matching circuit.

7)  $L_s$  provides real impedance for matching.