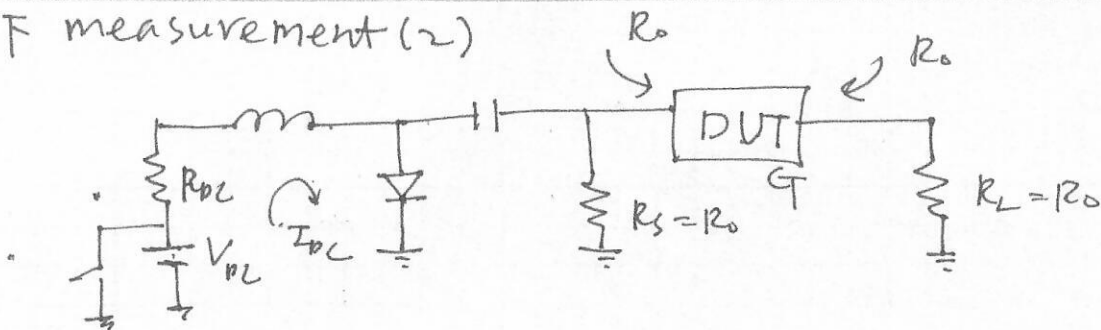


NF measurement (2)



- Step-1) Turn-on switch $\rightarrow I_{DC} = 0$
 \Rightarrow output noise power ($= P_{on}$)

$$P_{on} = \underbrace{KT\Delta f \cdot G}_{\text{noise power from } R_s} + \underbrace{P_{on, DUT}}_{\text{noise power from DUT}}$$

- Step-2) Turn-off switch and adjust V_{DC}
 Until output power becomes $2 \cdot P_{on}$

$$\Rightarrow 2P_{on} = \underbrace{2qI_{DC}\Delta f (R_s \parallel R_o)^2 \cdot G}_{\text{output noise power due to diode noise}}$$

$$+ KT\Delta f \cdot G + P_{on, DUT}$$

$$= \frac{1}{2} q I_{DC} \Delta f R_s^2 G + P_{on}$$

$$\therefore P_{on} = \frac{1}{2} q I_{DC} \Delta f R_s^2 G$$

$$\Rightarrow P_{on, DUT} = q I_{DC} \Delta f R_s^2 G - KT\Delta f \cdot G$$

From Step-1) and Step-2),

$$\text{Noise factor, } F = 1 + \frac{P_{on, DUT}}{KT\Delta f \cdot G} = \frac{\frac{1}{2} q I_{DC} R_s^2}{2KT} = \frac{I_{DC}}{2V_T} \cdot R_s^2$$

* Note: In this method, you don't need to know bandwidth of the DUT.