

② Computing $\overline{i_{n_{eq}}} \Rightarrow$ open input node.

From original circuit, output noise current is

$$\overline{i_{on}} = \overline{i_{nd}} \quad \text{--- (A)}$$


From model, output noise current is

$$\overline{i_{on}} = \overline{i_{n_{eq}}} \cdot \frac{1}{sC_{gs}} \cdot g_m \quad \text{--- (B)}$$

\Rightarrow From (A) and (B)

$$\overline{i_{n_{eq}}} = \overline{i_{nd}} \cdot \frac{sC_{gs}}{g_m} = \overline{i_{nd}} \frac{j\omega C_{gs}}{g_m}$$

2) Input referred noise voltage

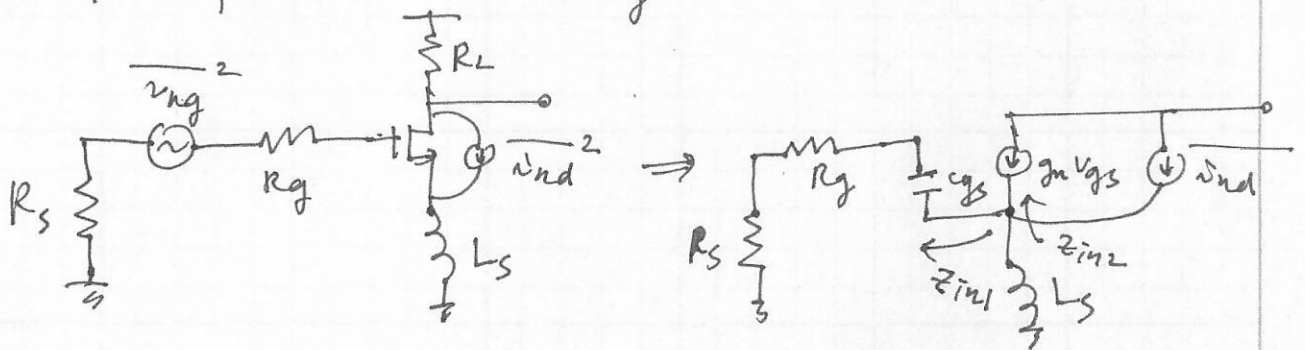

From equivalent circuit shown in ~~the~~ right side,

$$Z_{in1} = \frac{1}{sC_{gs}} + R_g + R_S \approx \frac{1}{sC_{gs}} + R_S$$

$$Z_{in2} = \frac{\frac{1}{sC_{gs}} + R_S + R_g}{\frac{g_m}{sC_{gs}}} \approx \frac{1 + sC_{gs}R_S}{g_m}$$

\Rightarrow Output ^{noise} Current due to $\overline{i_{nd}}$ is

$$\overline{i_{no}} \Big|_{\text{due to } \overline{i_{nd}}} = \frac{Z_{in2}}{Z_{in1} \parallel sL_S + Z_{in2}} \cdot \overline{i_{nd}}$$