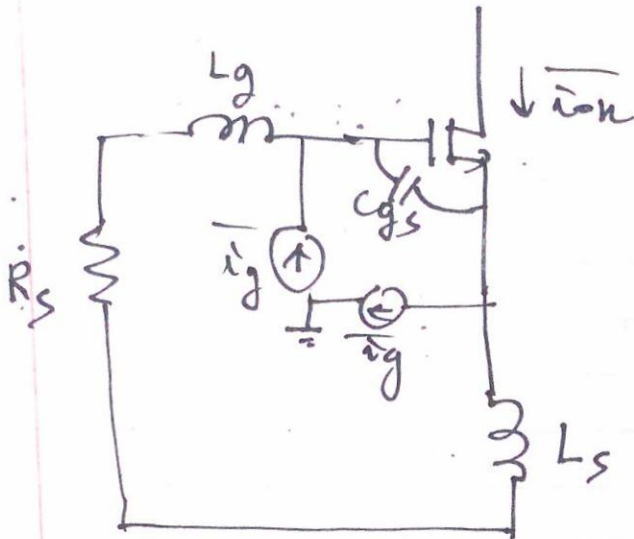


6) Output noise current due to induced gate noise current

①



$$\begin{aligned} \overline{i_{on}} \Big|_{\text{due to } \overline{i_g}} &= \frac{R_s + sL_g + sL_s}{R_s + sL_g + sL_s + \frac{1}{sC_{gs}} + \frac{g_m L_s}{C_{gs}}} \times \overline{i_g} \times \frac{g_m}{sC_{gs}} \\ &= \frac{1}{2R_s} \frac{\omega_T}{j\omega} (R_s + j\omega L_g + j\omega L_s) \cdot \overline{i_g} \\ &\approx \frac{1}{2R_s} \frac{\omega_T}{j\omega} (R_s + j\omega L_g) \overline{i_g} \end{aligned}$$

$$\begin{aligned} \therefore \overline{i_{on}} \Big|_{\text{Total}} &= \overline{i_{on}} \Big|_{\text{due to } R_s} + \overline{i_{on}} \Big|_{\text{due to } R_g} + \overline{i_{on}} \Big|_{\text{due to } \overline{v_d}} \\ &\quad + \overline{i_{on}} \Big|_{\text{due to } \overline{i_g}} \end{aligned}$$