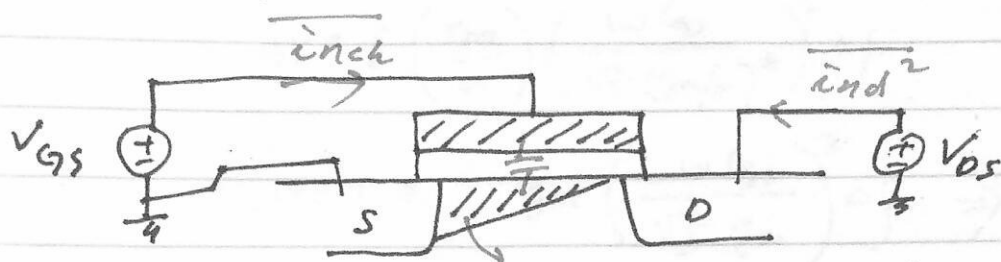


(3)

- ④ Now let's introduce another noise ~~no~~ which is
 Induced gate noise (or induced channel noise).



drain thermal noise current
 generates noise voltage across
 channel.

This noise voltage will be coupled
 capacitively into the gate terminal,
 causing a gate noise current.

⇒ this is "induced channel noise"
 (or induced gate noise).

$$\overline{i_{nd}^2} = 4KT r_{gd0} \Delta f$$

⇒ effective channel noise voltage

$$\overline{v_{nd}^2} \propto \overline{i_{nd}^2} \times \left(\frac{1}{g_{d0}}\right)^2 = \frac{4KT r}{g_{d0}} \Delta f$$

⇒ effective induced ~~gate~~ gate noise current

$$\begin{aligned} \overline{i_{nch}^2} &\propto \overline{v_{nd}^2} \times \omega^2 C_{gs}^2 = 4KT r \frac{\omega^2 C_{gs}^2}{g_{d0}} \Delta f \\ &= 4KT r g_{d0} \left(\frac{\omega C_{gs}}{g_{d0}}\right)^2 \Delta f \end{aligned}$$

⇒ More exact expression
 (according to "Van Der Ziel" noise model)

$$\overline{i_{nch}^2} = 4KT \int g_{d0} \left(\frac{\omega C_{gs}}{\sqrt{5} \cdot g_{d0}}\right)^2 \Delta f$$

~~gate noise~~ $\cdot \int$ = induced gate noise coefficient.
 typically $\int = 2\pi$.