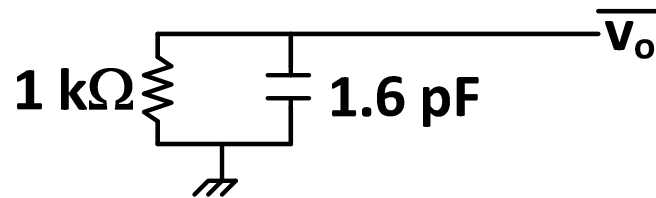

ECE 5220 RFIC HW -2

(Due: 03/05/2012, Hand in by the end of class time,
10:45AM)


Homework will not be acceptable after the class.

Problem-1: Noise concept




Assumption: Temperature
 $T=300\text{ K}$.

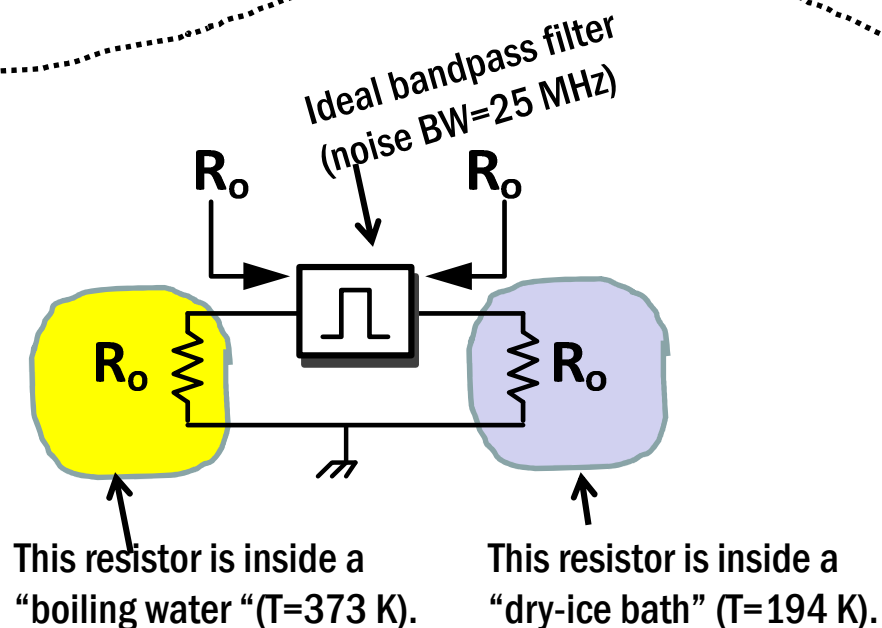- 1) Calculate effective noise voltage $\overline{V_o}$.
- 2) How often will the magnitude of the noise voltage be greater than $88\text{ }\mu\text{V}$? (you may need a numerical calculator for compute probability, or alternatively you can use a Gaussian distribution table which is uploaded in the “resource” part of “Scholar class website”.)



- 3) Compute net power flow and direction of the system shown in left side.


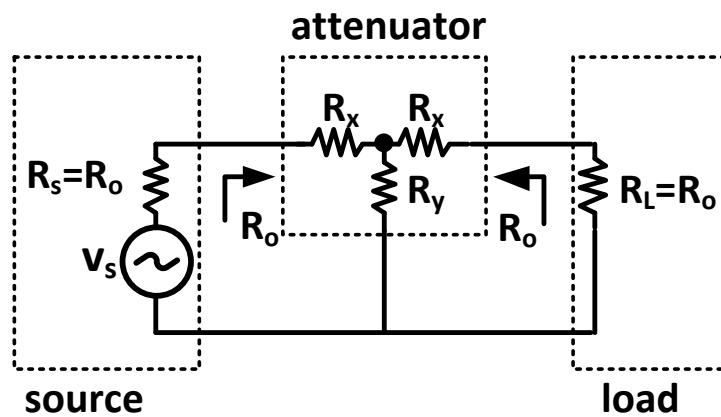
Problem-2: Noise consideration in lossy network



Assumption: R_L is noiseless.

- 1) Calculate noise power delivered to load by the source resistor only.
- 2) Calculate noise power delivered to load by each of three resistors in the attenuator one by one.
- 3) From 1) and 2), verify that noise power keep constant between input and output of attenuator.
- 4) Verify that noise factor, $F=L$ (L =loss).
- 5) Numerical example: Repeat 1)-4) when $R_o=50\Omega$, $R_x=8.55\Omega$, $R_y=141.9\Omega$.

Problem-3: BJT noise factor calculation

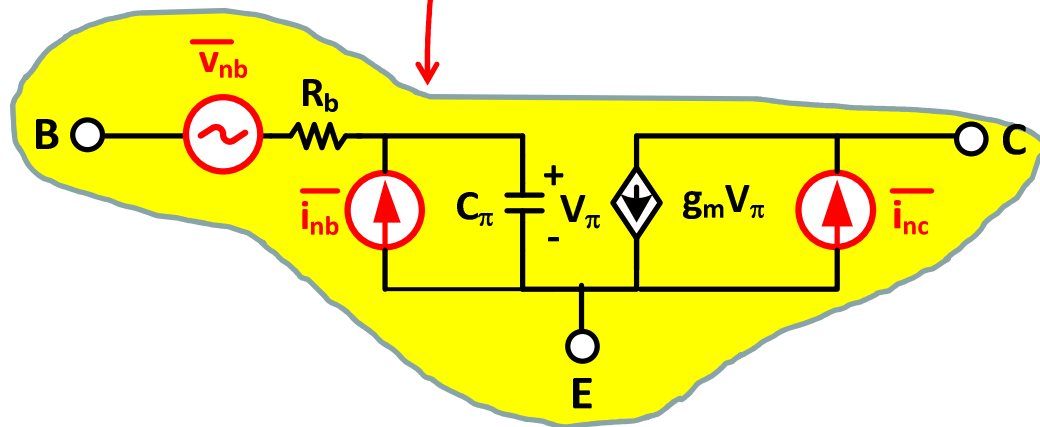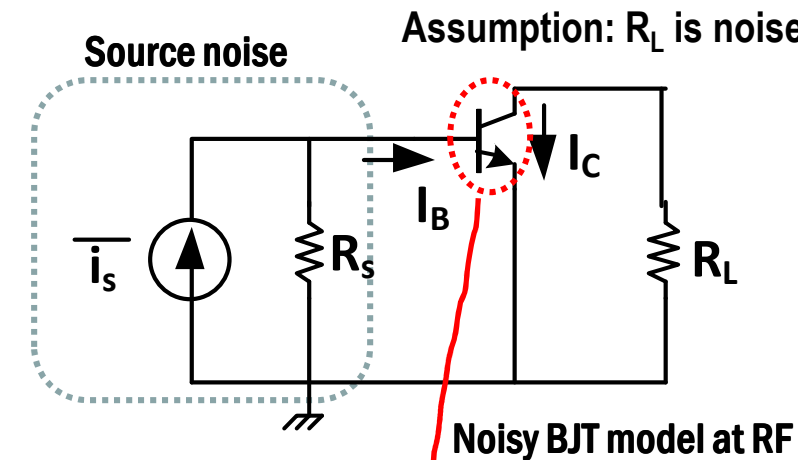


□ BJT can be modeled as shown in the figure at RF, where R_b is base resistance V_{nb} is the effective noise voltage from the base resistance, and i_{nb} and i_{nc} are effective shot noise current from bias currents of I_B and I_C , respectively.

- 1) Calculate input referred noise (assume R_L is noiseless).
- 2) Calculate noise factor of the system.

Problem-4: NF Measurement (1)


Assumption: R_L is noiseless.

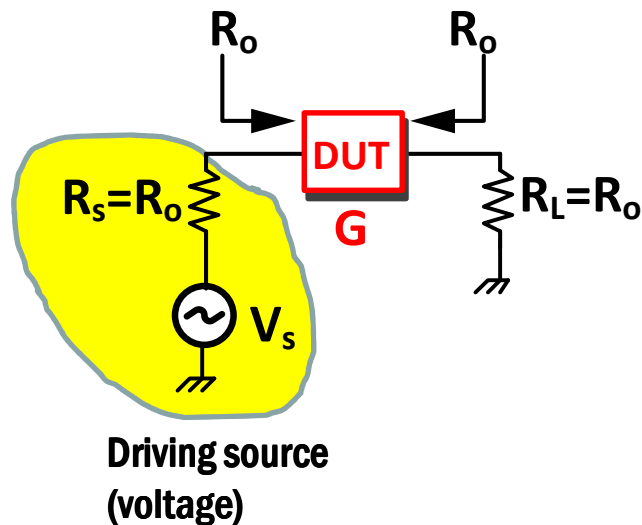

- Let's do some mental experiment to measure noise factor (F) of the device under test (DUT). The only known factor of the DUT is input and output impedance which are matched to R_o , and available power gain, G .
- Step-1) make $V_s=0$, then measure output power delivered to load, R_L .
- Step-2) turn on V_s , and adjust V_s so that your output power delivered to R_L can be twice of the power in Step-1.

Q) Calculate F from the results in Step-1 and Step-2 (assume DUT bandwidth is Δf).

Problem-4: NF Measurement (2)

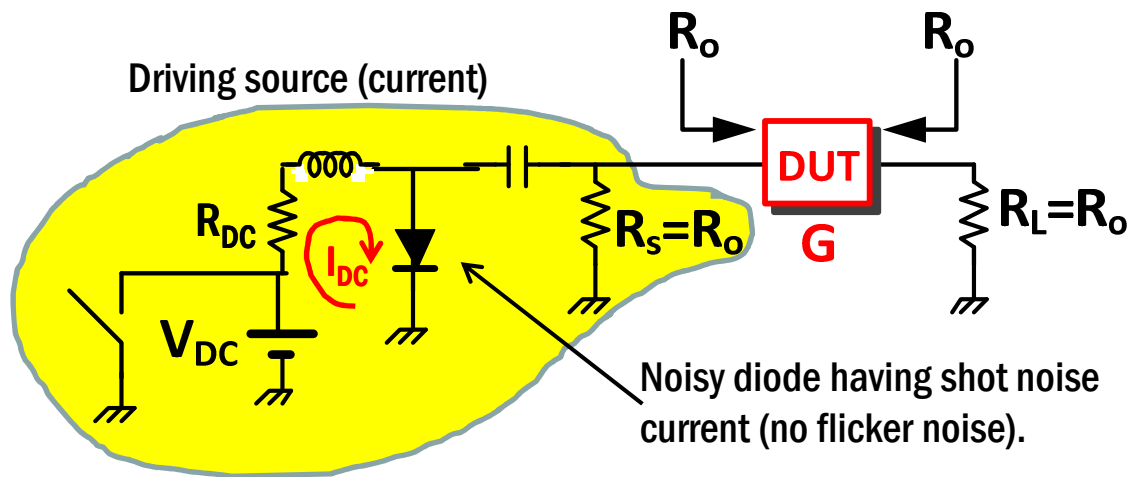

Assumption:


- R_L is noiseless.
- Diode output resistance is much larger than R_s .
- C: blocks DC current and passes all noise current from diode.
- L: blocks any noise current from R_{DC} and pass DC current from V_{DC} .

- Let's do similar mental experiment to measure noise factor (F) of the device under test (DUT). The only known factor of the DUT is input and output impedance which are matched to R_o , and available power gain, G (now, you don't know the DUT bandwidth).
- Step-1) turn on switch and no DC current. Then measure out put power delivered to load, R_L .
 - Step-2) turn off the switch and adjust V_{DC} so that your output power delivered to R_L can be twice of the power in Step-1.

Q) Calculate F from the results in Step-1 and Step-2.

(Note: You don't need to know the gain of the DUT either in this method.)

Problem-5: Inductively degenerated LNA

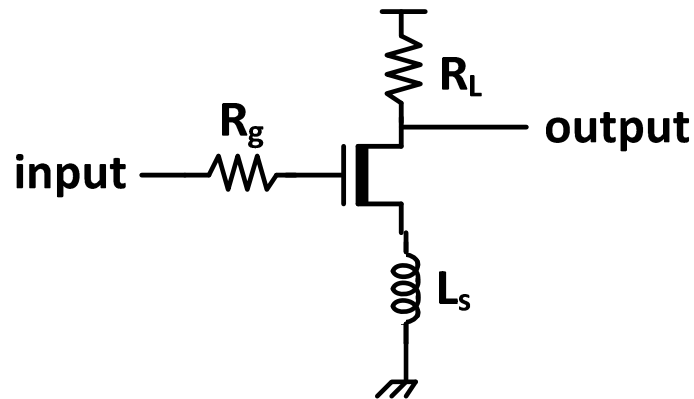


Assumption:

- R_L is noiseless and no flicker noise in NMOS.
- No drain-gate parasitic capacitance, C_{gd} .
- $R_g \ll 1/\omega C_{gs}$
- $g_m R_g \ll 1$

- 1) Calculate equivalent input noise generators (voltage and current generators).
- 2) Calculate input referred noise (voltage or current) with an assumption of source impedance of R_s .
- 3) Calculate correlation admittance between the voltage and current noises in 1), and separate the current noise into correlated and uncorrelated parts.
- 4) Find optimum admittance for minimum F .
- 5) Find expression for F_{min} .

Problem-6: Common-gate LNA

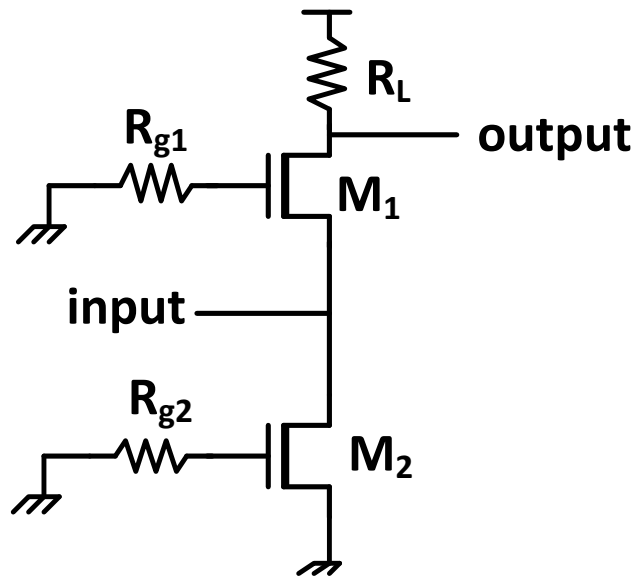

- 1) Calculate equivalent input noise generators (voltage and current generators).
- 2) Calculate input referred noise (voltage or current) with an assumption of source impedance of R_s .
- 3) Calculate correlation admittance between the voltage and current noises in 1), and separate the current noise into correlated and uncorrelated parts.
- 4) Find optimum admittance for minimum F.
- 5) Find expression for F_{min} .

Assumption:

- R_L is noiseless and no flicker noise in M1 and M2.
- No drain-gate parasitic capacitance, C_{gd} .
- g_m of M1 = g_{m1} , g_m of M2 = g_{m2} .
- C_{gs} of M1 = C_{gs1} , C_{gs} of M2 = C_{gs2} .
- $R_g \ll 1/\omega C_{gs}$ (for M1 and M2)
- $g_m R_g \ll 1$ (for M1 and M2)