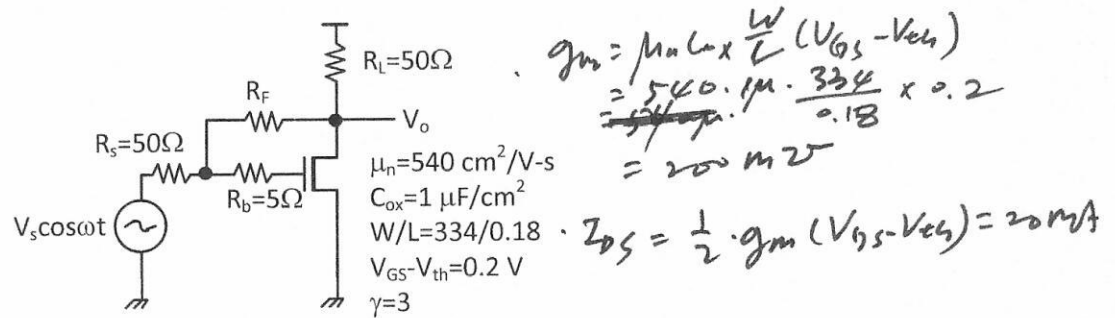


1. In the amplifier shown below, DC characteristic of the NMOS is set by square-law characteristic, i.e.

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2.$$

Assume that $R_s \ll 1/\omega C_{gs}$, **all resistors are noisy** and NMOS has drain thermal noise current.

The drain thermal noise coefficient is γ .



- 1) Determine feedback resistance, R_F , to match input and output impedance to R_s and R_L , respectively (5pt).

$$Z_{in} = \frac{R_F + R_L}{1 + g_m R_L} \approx \frac{R_F}{g_m R_L} = R_s \rightarrow R_F = g_m \cdot R_L \cdot R_s = 520 \Omega$$

$$Z_{out} = \frac{R_F + R_s}{1 + g_m R_s} \approx \frac{R_F}{g_m R_s} = 50 \Omega = R_L$$

- 2) Express output noise voltages due to R_s , R_F , R_b , R_L and drain current (I_{DS}), respectively, under matched condition (20pt). **You don't need to calculate them numerically.**

$$(V_{on})_{\text{due to } R_s} = \sqrt{R_s} \cdot \frac{1}{2} \frac{R_F}{R_s} = \sqrt{4kTR_s \Delta f} \left(\frac{1}{2} \frac{R_F}{R_s} \right)$$

$$(V_{on})_{\text{due to } R_F} = \sqrt{R_F} \cdot \frac{R_L}{Z_o + R_L} = \sqrt{R_F} \cdot \frac{1}{2} = \sqrt{4kTR_F \Delta f} \left(\frac{1}{2} \right)$$

$$(V_{on})_{\text{due to } R_b} = \sqrt{R_b} \cdot g_m \frac{1}{2} R_L = \sqrt{R_b} \cdot \frac{1}{2} \frac{R_F}{R_s} = \sqrt{4kTR_b \Delta f} \left(\frac{1}{2} \frac{R_F}{R_s} \right)$$

$$(V_{on})_{\text{due to } R_L} = \sqrt{R_L} \cdot \frac{1}{2} = \sqrt{4kTR_L \Delta f} \left(\frac{1}{2} \right)$$

$$(V_{on})_{\text{due to } I_{DS}} = \sqrt{i_{no}} \cdot \frac{1}{2} R_L = \sqrt{4kTRg_m \Delta f} \left(\frac{1}{2} R_L \right)$$

3) Calculate noise factor (F) under the impedance matched condition (10pt).

$$\begin{aligned}
 F &= 1 + \frac{4kTR_f \Delta f \left(\frac{1}{2}\right)^2 + 4kTR_b \Delta f \left(\frac{1}{2} \frac{R_F}{R_S}\right)^2 + 4kTR_L \Delta f \left(\frac{1}{2}\right)^2 + 4kT r_{gm} \Delta f \left(\frac{1}{2}\right)^2}{4kTR_S \Delta f \left(\frac{1}{2} \frac{R_F}{R_S}\right)^2} \\
 &= 1 + \frac{R_S}{R_F} + \frac{R_b}{R_S} + \frac{R_L}{R_S} \left(\frac{R_S}{R_F}\right)^2 + \frac{r_{gm}}{R_S} \left(\frac{R_S}{R_F}\right)^2 \cdot R_L \\
 &= 1 + \frac{R_S}{R_F} + \frac{R_b}{R_S} + \frac{R_L}{R_S} \left(\frac{R_S}{R_F}\right)^2 + r_{gm} \frac{R_L}{R_F} \\
 &= 1 + 0.1 + 0.1 + (0.1)^2 + 3 \times 0.1 = 1.51 \rightarrow 1.79 \text{ dB}
 \end{aligned}$$

4) Calculate THD without feedback ($R_F = \infty$). Assume that $V_S = 40 \text{ mV}_p$ (10pt).

$$\begin{aligned}
 I_b &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th} + V_S \cos \omega t)^2 \\
 &= I_{D1} + \underbrace{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) V_S \cos \omega t}_{= g_m = \alpha_1} + \underbrace{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_S^2 \cos^2 \omega t}_{= \alpha_2}
 \end{aligned}$$

$$\begin{aligned}
 \therefore \text{THD} = \text{HD}_2 &= \frac{1}{2} \frac{\alpha_2}{\alpha_1} V_S = \frac{V_S}{4(V_{GS} - V_{th})} = \frac{40 \text{ mV}_p}{4 \times 0.2} \\
 &= 0.05 \\
 &= 5\%
 \end{aligned}$$

5) With R_F , determine feedback factor and loop gain (10pt).

$$\begin{aligned}
 - \text{feedback factor } f &= \frac{R_S}{R_F + R_S} \approx \frac{R_S}{R_F} = 0.1 \\
 - \text{loop gain} &= (g_m \cdot R_L) \cdot f = \frac{R_F}{R_S} \cdot \frac{R_S}{R_F} = 1
 \end{aligned}$$

6) Calculate THD with feedback. Also assume that $V_S = 40 \text{ mV}_p$ (10pt).


$$\begin{aligned}
 \text{When applying feedback, } \alpha_1 &\rightarrow \frac{\alpha_1}{1 + \text{loop gain}} \\
 \alpha_2 &\rightarrow \frac{\alpha_2}{(1 + \text{loop gain})^2}
 \end{aligned}$$

$$\Rightarrow (\text{HD}_2)_{\text{with feedback}}$$


$$= (\text{HD}_2)_{\text{without feedback}} \times \frac{1}{(1 + \text{loop gain})^2}$$

$$= 0.05 \times \frac{1}{4} = 0.0125 \rightarrow 1.25\%$$

$$A_v = g_m R_L$$

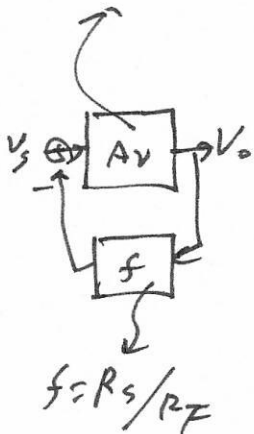

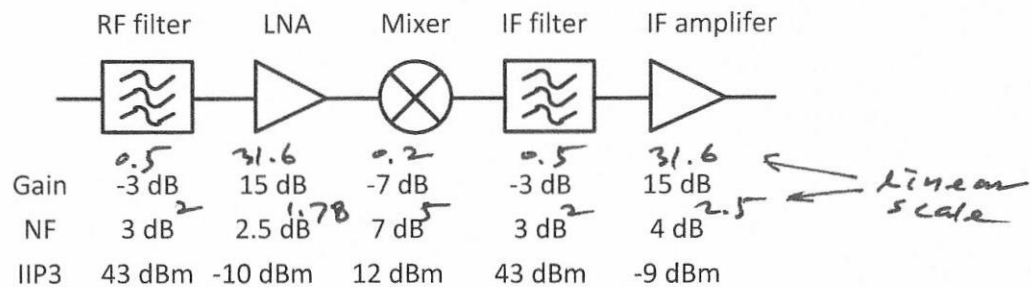2. Consider the cascaded system shown below. All interfaces are matched to $50\ \Omega$ and signal bandwidth is 1 MHz. The required output SNR is 20 dB.



- 1) Determine input noise floor and input minimum detectable signal (MDS) of the system in dBm scale (10pt). Note, $10 \log(KT) = -174\text{ dBm}$ @ $T=300\text{K}$.

$$\text{Overall } F = 2 + \frac{1.78-1}{0.5} + \frac{5-1}{0.5 \times 31.6} + \frac{2-1}{0.5 \times 31.6 \times 0.2} + \frac{2.5-1}{0.5 \times 31.6 \times 0.2 \times 0.5}$$

$$= 5.078 \rightarrow 7.05\text{ dB}$$

$$\therefore \text{Input Noise floor} = KT \Delta f \cdot F = -174\text{ dBm} + 10 \log(1\text{ MHz}) + 7.05\text{ dB}$$

$$= -107\text{ dBm}$$

$$\Rightarrow \text{MDS} = \text{Input noise floor} + \text{SNR}_{\min}$$

$$= -107\text{ dBm} + 20\text{ dB} = -87\text{ dBm}$$

- 2) Determine spurious free dynamic range (SFDR) of the system (10pt).


$$\frac{1}{\text{overall } \text{IIP3}} = \frac{1}{10^{4.3}} + \frac{0.5}{10^1} + \frac{0.5 \times 31.6}{10^{1.2}} + \frac{0.5 \times 31.6 \times 0.2}{10^{4.3}} + \frac{0.5 \times 31.6 \times 0.2 \times 0.5}{10^{0.9}}$$

$$\rightarrow \text{Overall IIP3} = 54 \times 10^{-3}\text{ mW} \rightarrow -12.7\text{ dBm}$$

$$\therefore \text{SFDR} = \frac{2}{3} (\text{IIP3} - \text{Noise floor}) + \text{SNR}_{\min}$$

$$= 62.87\text{ dBm} - 20\text{ dB} = 42.87\text{ dB}$$

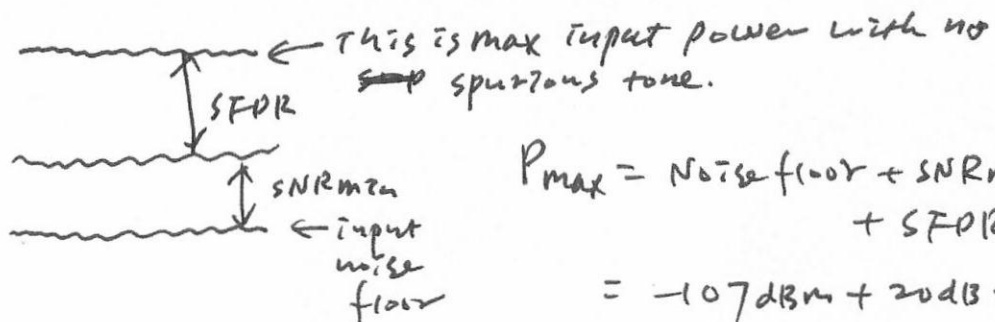- 3) What is the maximum input power that allows no spurious tone? (10pt).



$$P_{\max} = \text{Noise floor} + \text{SNR}_{\min} + \text{SFDR}$$

$$= -107\text{ dBm} + 20\text{ dB} + 42.87\text{ dBm}$$

$$= -44.13\text{ dBm}$$