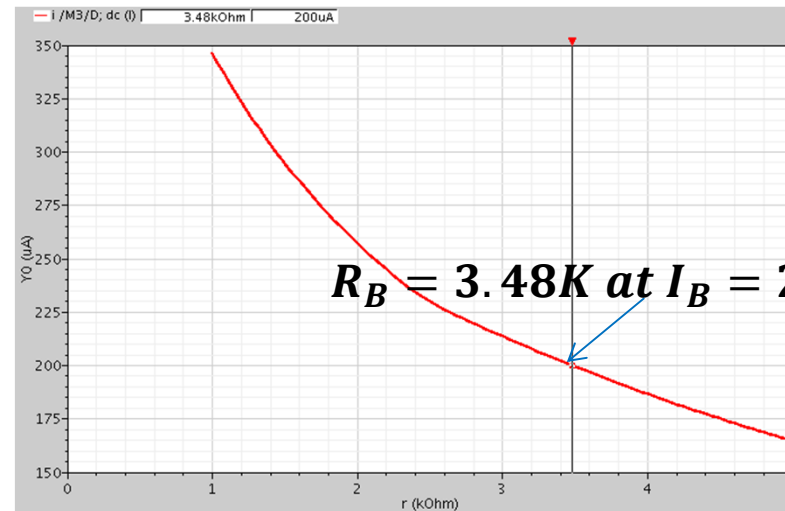


ECE 4220 Class Project #2

Solution


By Mr. Smith

Differential Amplifier Design (1)- Q-1,3



Q-3) Answer: PMOS enters from saturation region to triode region or cut-off due to V_B . For this reason, node-A, B can be sensitive to V_B .

Differential Amplifier Design (1)- Q-2

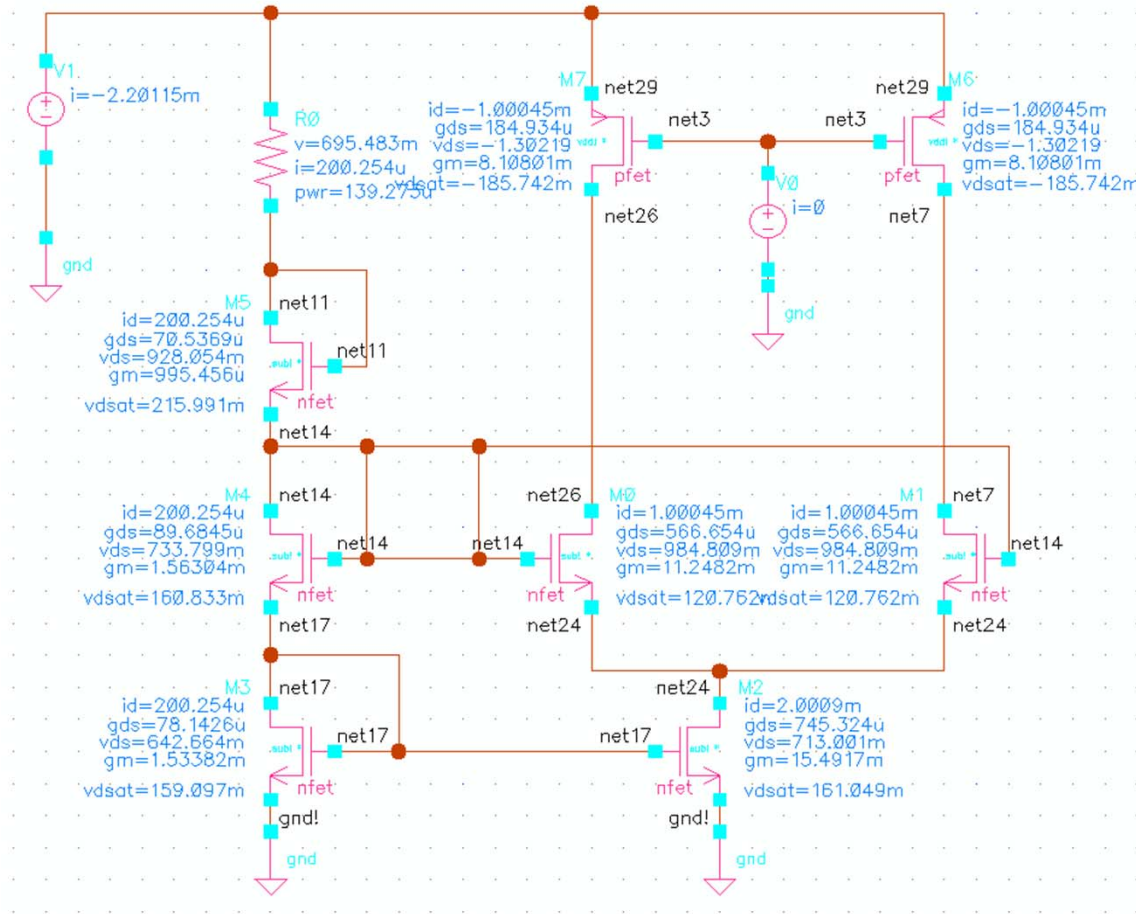


$$g_m = 11.24\text{m}$$

$$r_{op} = 1/g_{p,ds} = 5.4K$$

$$r_{on} = 1/g_{n,ds} = 1.764K$$

Differential Amplifier Design (2)- Q-4,5

➤ Simulation result

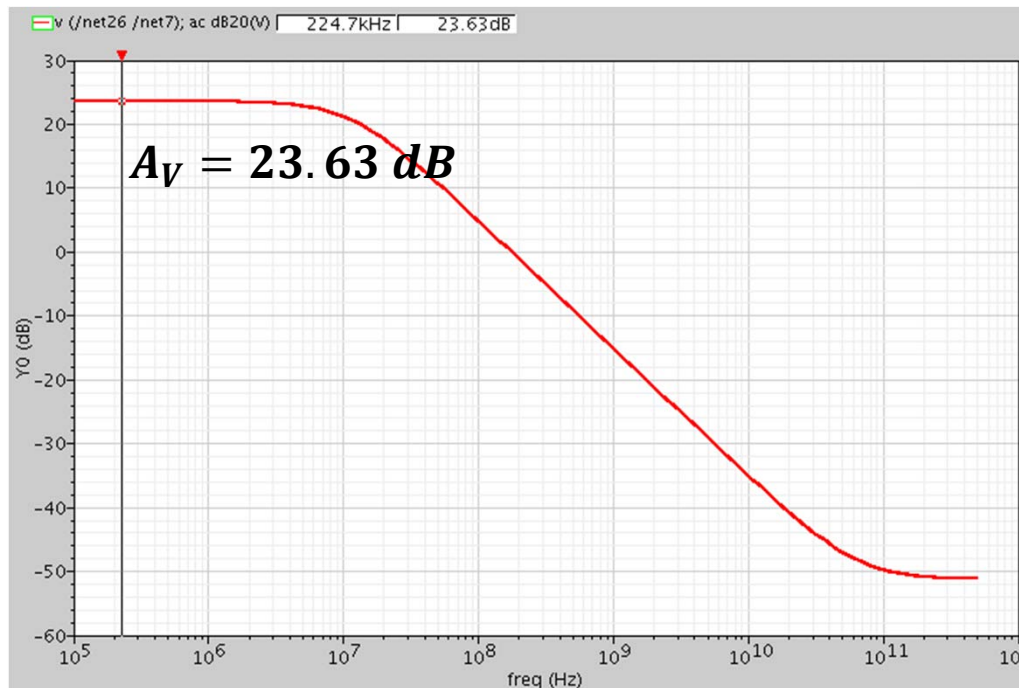

➤ Small signal parameters in Step-(1)

$$g_m = 11.2 \text{ mS}$$


$$r_{op} = 1/g_{p,ds} = 5.41 \text{ K}\Omega$$

$$r_{on} = 1/g_{n,ds} = 1.8 \text{ K}\Omega$$

$$\begin{aligned} A_v &= g_m \cdot (r_{on} \parallel r_{op}) \\ &= 11.2 \text{ mS} \cdot (1.8 \text{ K}\Omega \parallel 5.41 \text{ K}\Omega) \\ &= 11.2 \text{ mS} \cdot 1.35 \text{ K}\Omega = 15.12 \\ &= 23.59 \text{ dB} \end{aligned}$$

→ Same as simulation result

Differential Amplifier Design (2)- Q-6

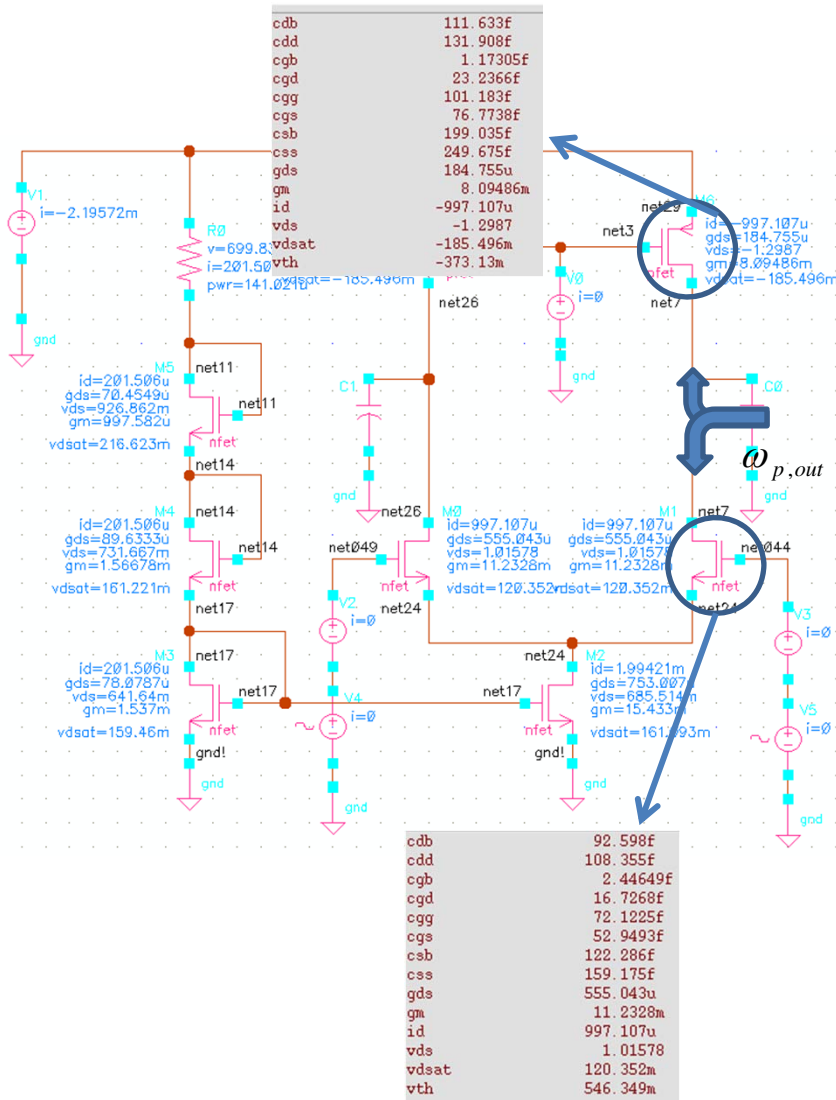

$$F_{3dB} = \omega_p / 2\pi$$


$$= 1/2 \cdot \pi \cdot \{1.35K \cdot (10p + 92f + 16f + 112f)\}$$

$$= 11.5MHz \rightarrow \text{Same as simulation result}$$

$$C_{DB,n} = 92f, \quad C_{GD,n} = 16f, \quad C_{DB,p} = 112f, \quad C_L = 10p$$

$$\omega_{p,out} = \frac{1}{R_L (C_L + C_{DB,n} + C_{GD,n} + C_{DB,p})}$$


$$F_{3dB} = 11.5MHz$$

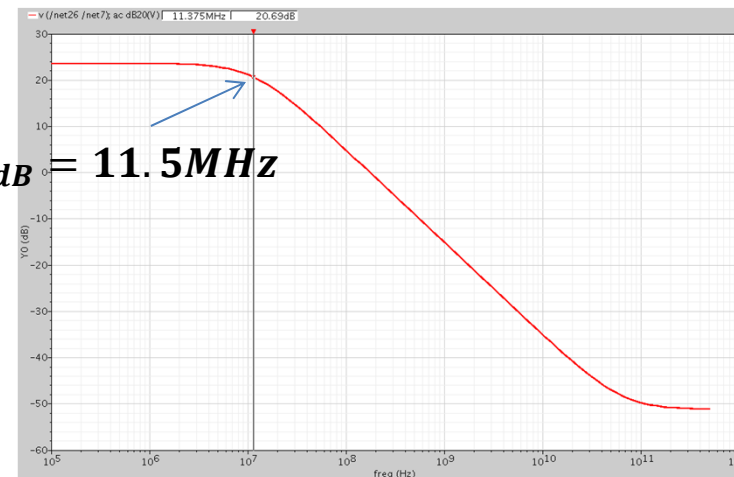

➤ Simulation result


Differential Amplifier Design (3)- Q-7

➤ *Simulation result*

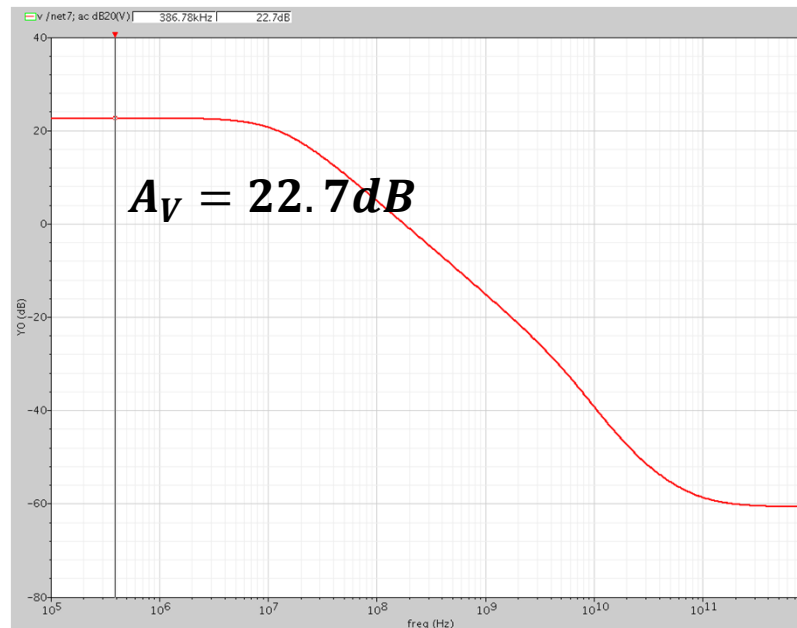

Due to current mirror, the gain of single-ended output is about the same as one of Q-4.

Differential Amplifier Design (3)- Q-8

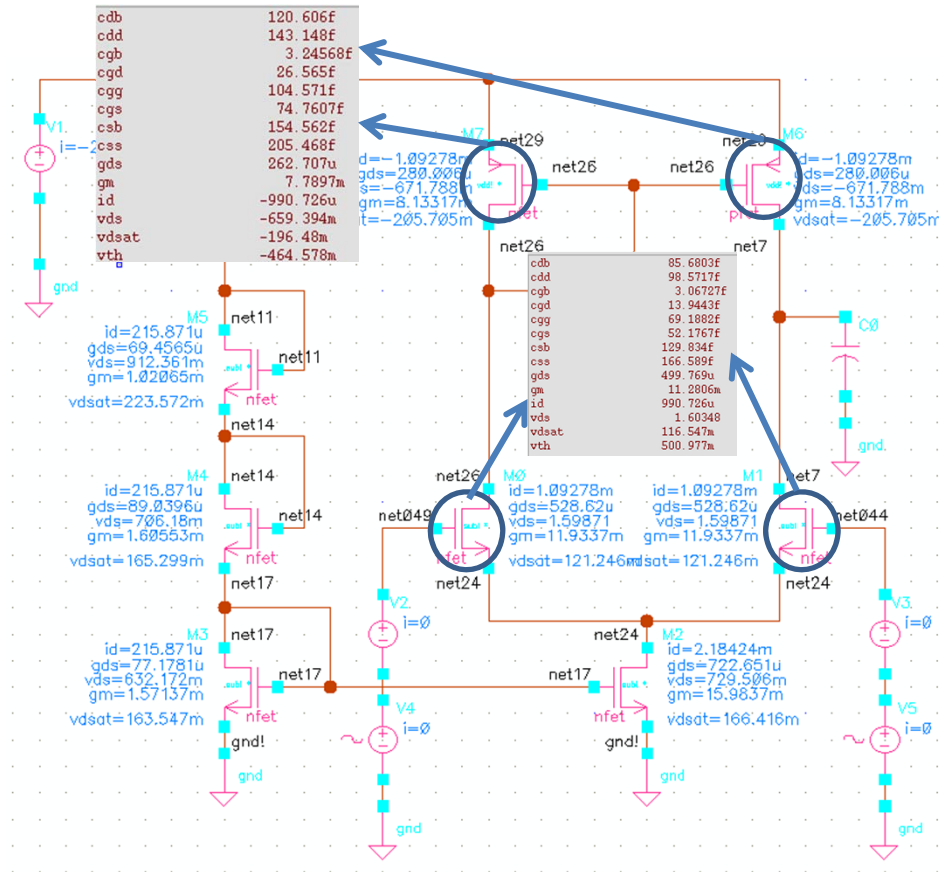

$$\omega_{p,1st} = \frac{1}{R_L (C_L + C_{DB,n} + C_{GD,n} + C_{DB,p})}$$

$$\omega_{p,2nd} = \frac{1}{R_{L,2nd} (C_{DB,n} + C_{GD,n} + C_{DB,p} + 2C_{GS,p})}$$

$$\omega_z = 2\omega_{p,2nd}$$

$$\begin{aligned} \mathcal{F}_{p,1st} &= \omega_{p,1st}/2\pi \\ &= 1/2 \cdot \pi \cdot \{1.236K \cdot (10p + 92f + 16f + 112f)\} \\ &= 12.6MHz \end{aligned}$$


$$\begin{aligned} \mathcal{F}_{p,2nd} &= \omega_{p,2nd}/2\pi \\ &= 1/2 \cdot \pi \cdot \{123 \cdot (92f + 16f + 120f + 150f)\} \\ &= 3.42GHz \end{aligned}$$

$$\mathcal{F}_z = 2 \cdot \omega_{p,2nd} = 6.84GHz$$

$$\begin{aligned} C_{DB,n} &= 92f, \quad C_{GD,n} = 16f, \quad C_{DB,p} = 112f, \quad C_{GS,p} = 75f, \\ C_L &= 10p, \quad R_{L,2nd} = \frac{1}{g_m} = 123 \, Ohm \end{aligned}$$

Differential Amplifier Design (3)- Q-8

➤ Simulation result

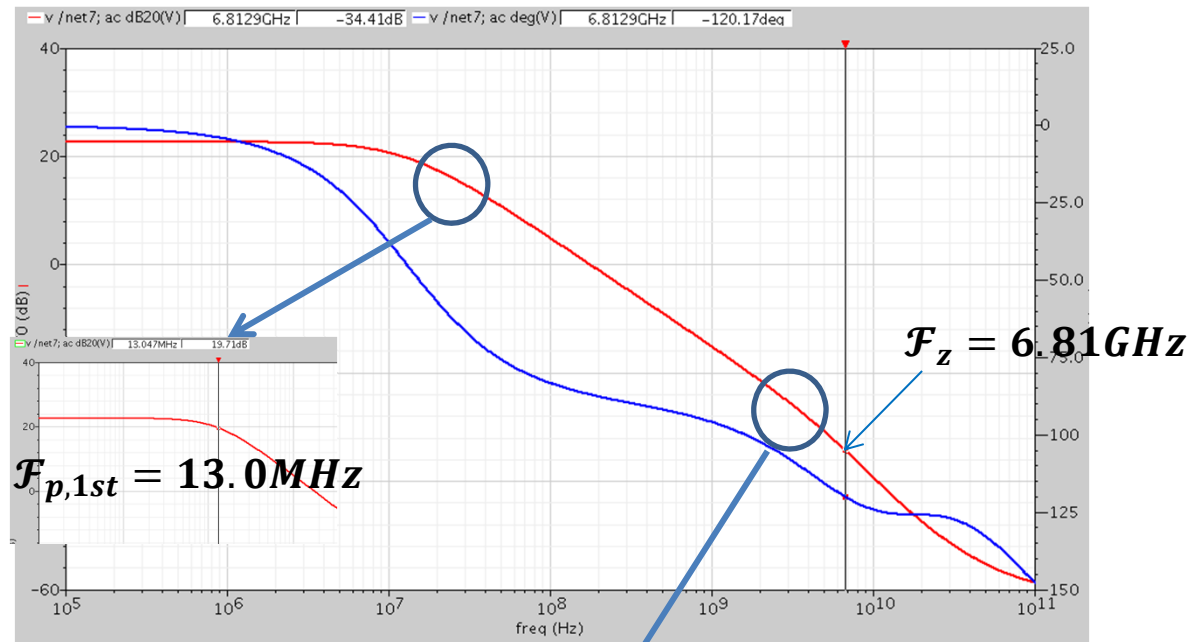


➤ Calculation

$$f_{p,1st} = \omega_p / 2\pi = 12.6 \text{ MHz}$$


$$f_{p,2nd} = \omega_{p,2nd} / 2\pi = 3.42 \text{ GHz}$$

$$f_z = 2 \cdot \omega_{p,2nd} = 6.84 \text{ GHz}$$


→ Same as simulation result

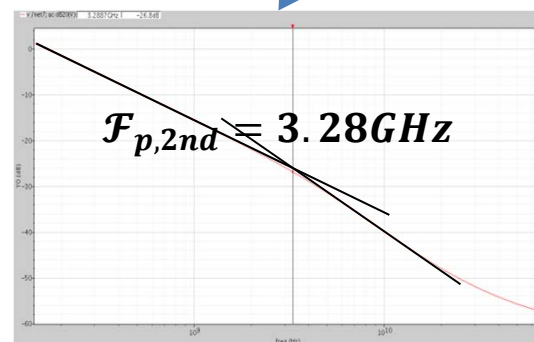


Differential Amplifier Design (4)- Q-9

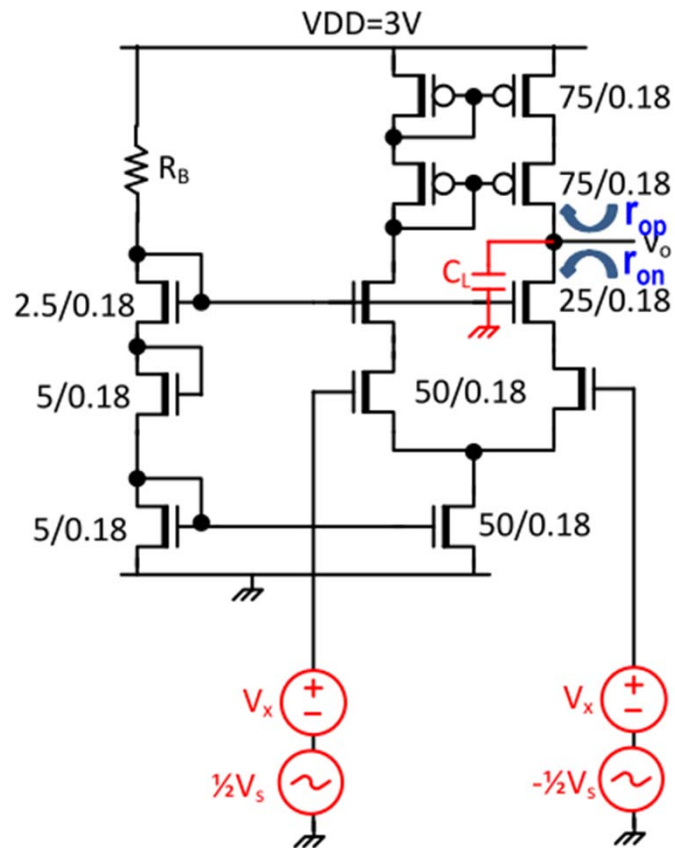

➤ *Simulation result*

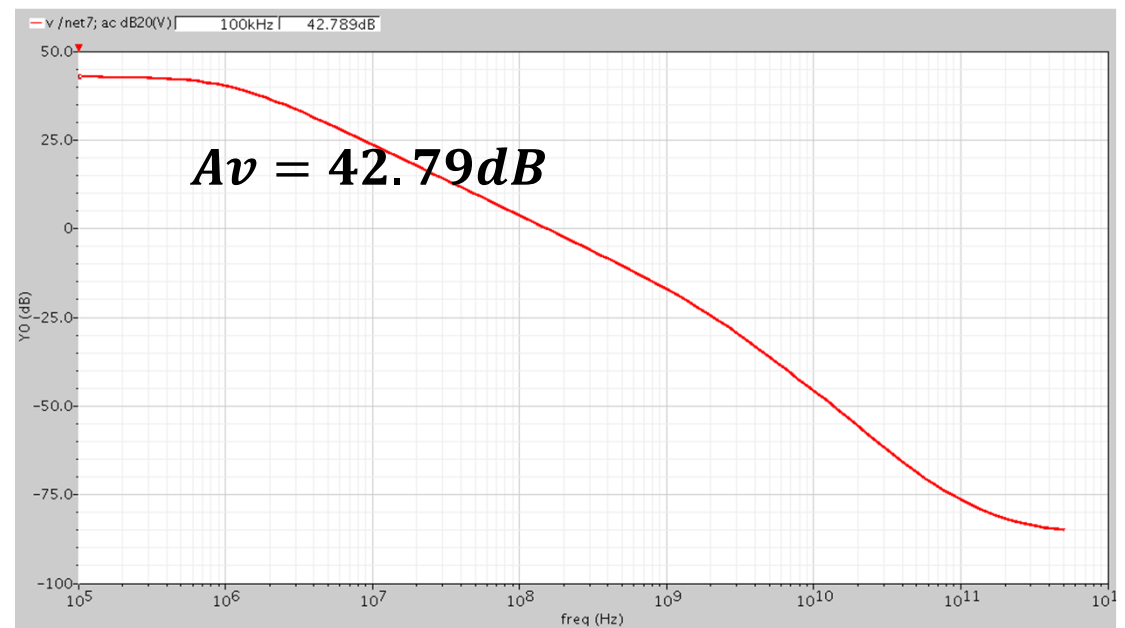

Differential Amplifier Design (4)- Q-10

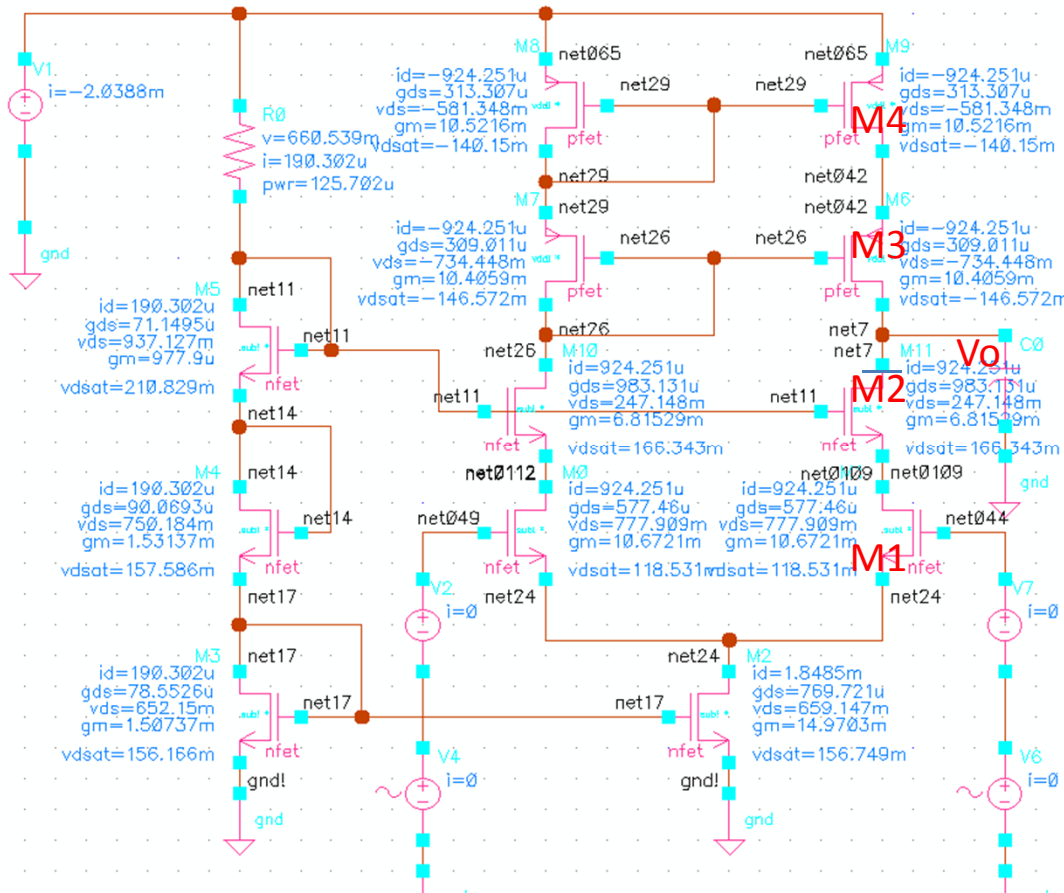


$$\begin{aligned}
 A_v &= g_{m1} \cdot (r_{on} \parallel r_{op}) \\
 &= 10.4m \cdot (14.5K \parallel 113.6K) \\
 &= 10.4m \cdot 12.858K = \mathbf{133.7 = 42.52dB}
 \end{aligned}$$

➤ It is the same as the simulation result.

$$\begin{aligned}
 r_{on} &= r_{o1} + r_{o2} + g_{m2} \cdot r_{o1} \cdot r_{o2} = 14.5K \\
 r_{op} &= r_{o3} + r_{o4} + g_{m3} \cdot r_{o3} \cdot r_{o4} = 113.6K
 \end{aligned}$$


$$\begin{aligned}
 g_{m1} &= 10.6m \\
 g_{m2} &= 6.8m \\
 r_{o1} &= 1/g_{ds1} = 1.73K \\
 r_{o2} &= 1/g_{ds2} = 1.0K \\
 g_{m3} &= 10.4m \\
 r_{o3} &= 1/g_{ds3} = 3.23K \\
 r_{o4} &= 1/g_{ds4} = 3.19K
 \end{aligned}$$

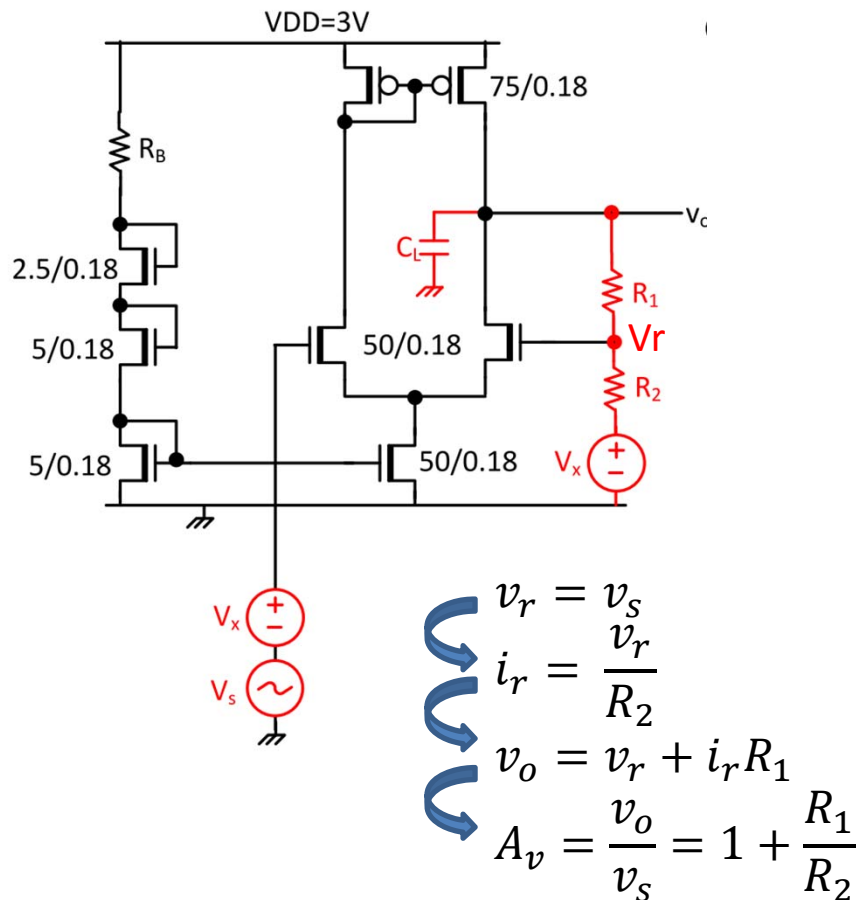Differential Amplifier Design (5)- Q-11,12



- If $R_1 = R_2$, the A_v is 6dB.
- Set $R_1=R_2=1M$ ohm.

➤ Simulation result


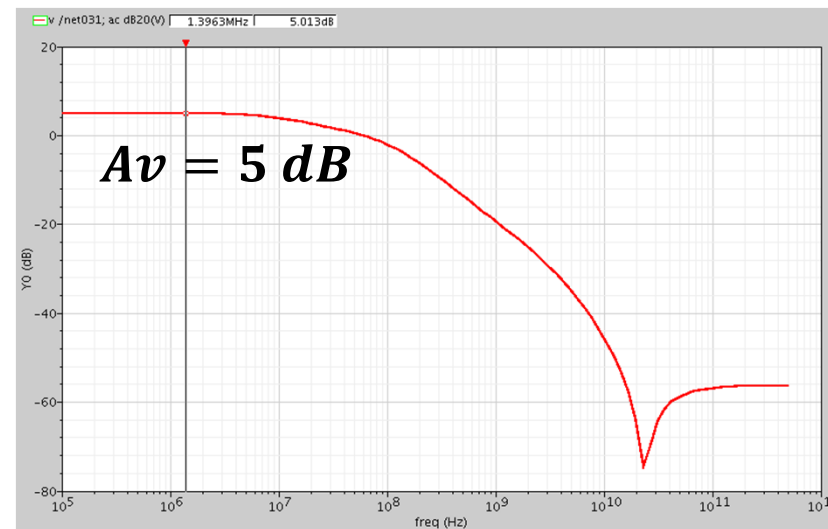


- Due to small loop gain, the simulation gain is less than the expected 6dB.

❖ Using the calculated gain in Q-13,
 $A_v = \left(1 + \frac{R_1}{R_2}\right) \cdot \left(\frac{T}{T+1}\right) = 2 \cdot 0.88 =$
1.76 = 4.91dB → Same as the simulation result

Differential Amplifier Design (6)- Q-13

➤ *Simulation result*

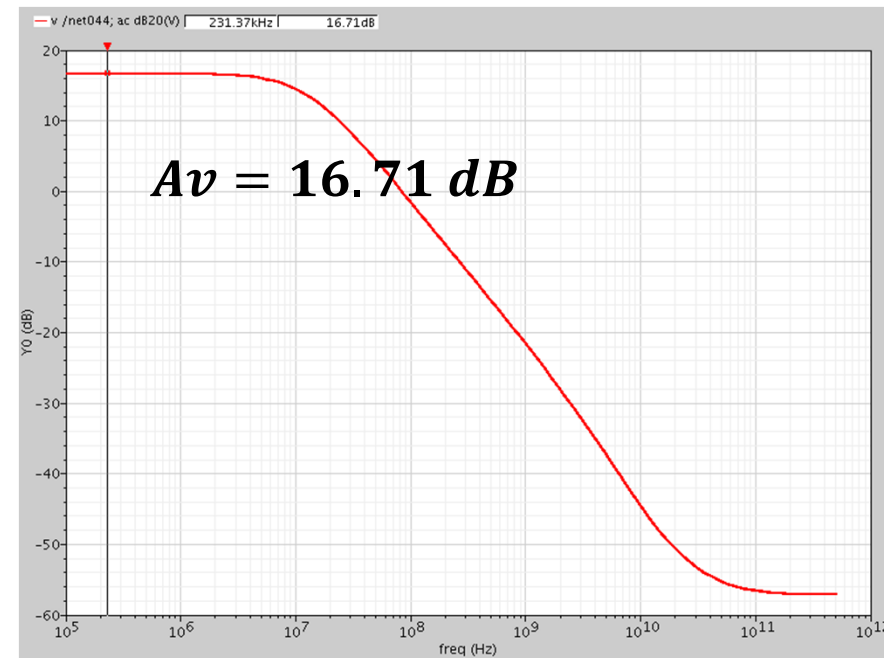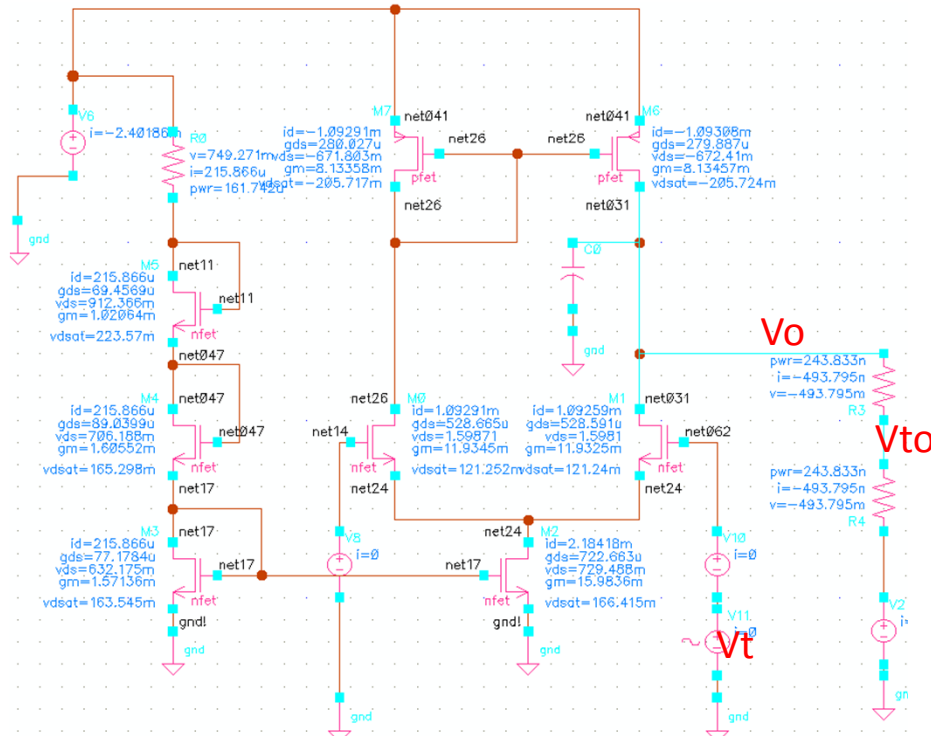

$$T = \frac{v_{to}}{v_t} = \frac{v_o}{v_t} \cdot \left(\frac{R_2}{R_1 + R_2} \right) = 0.5 \cdot g_m \cdot \{r_{on} \parallel r_{op} \parallel (R_1 + R_2)\}$$

$$= 0.5 \cdot 11.9m \cdot (3.57K \parallel 1.89K \parallel 2M)$$

$$= 0.5 \cdot 11.9m \cdot 1.234K = 7.34$$

$$= 17.31dB$$

➔ *Same as simulation result*