
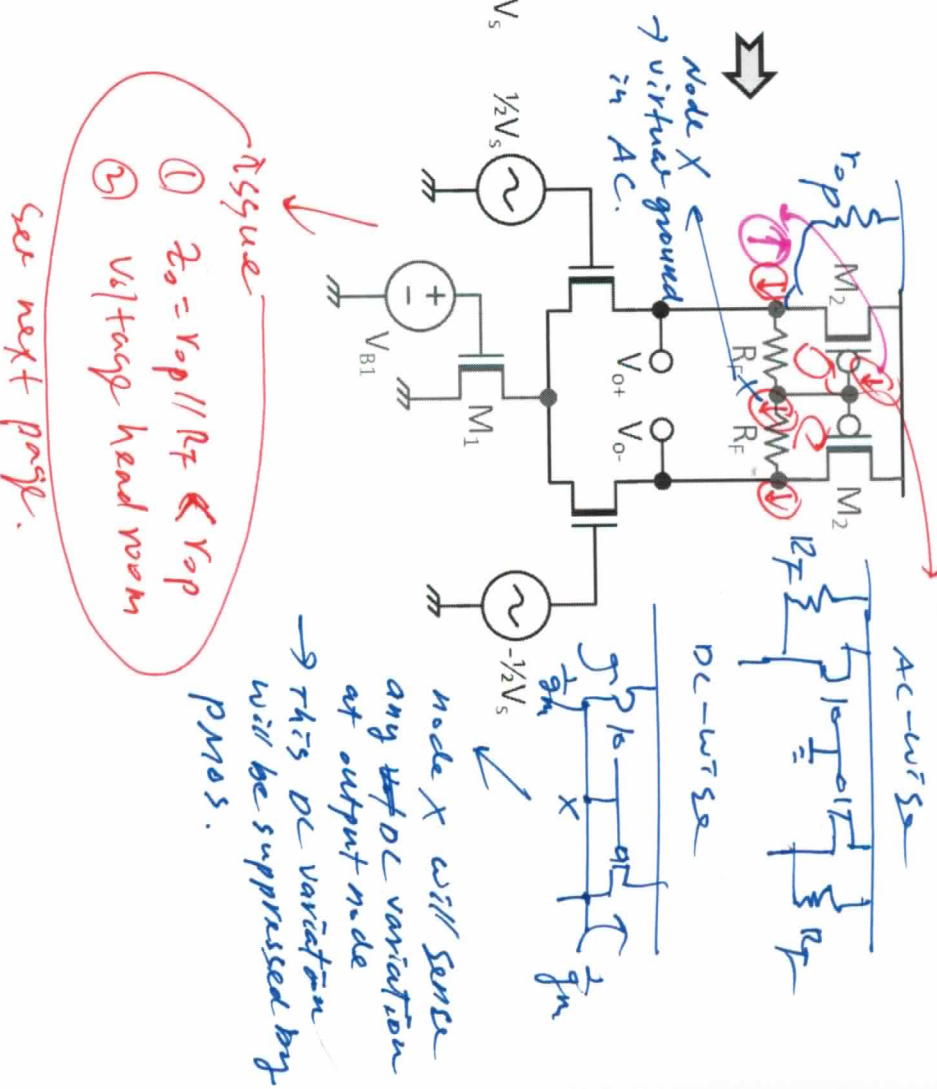


DC Stability (2)


①

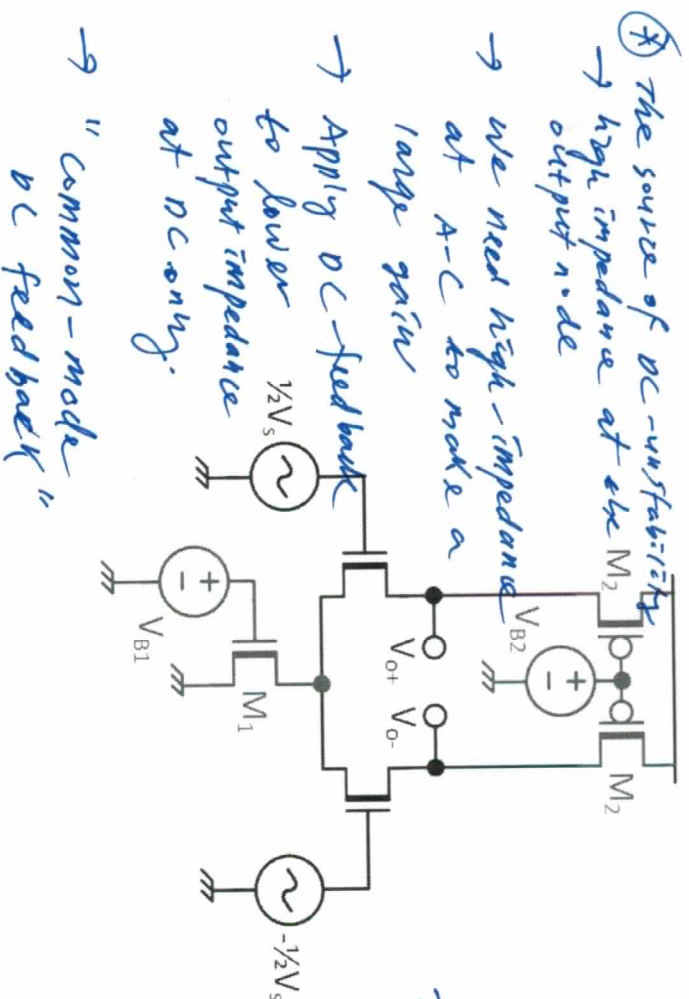- ☐ Common-mode DC feedback \Rightarrow common-mode feedback load
- ☐ What could be an issue in this common-mode feedback load?



DC Stability (2)


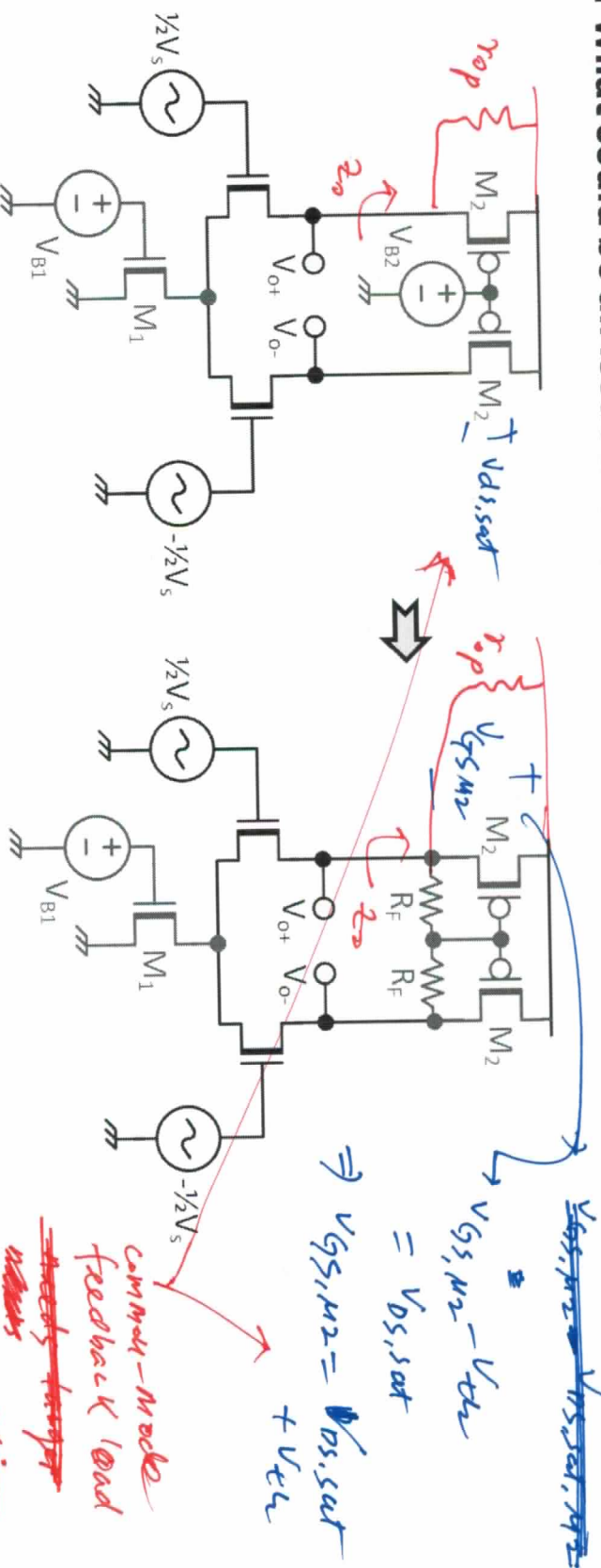
- Common-mode DC feedback \Rightarrow common-mode feedback load
- What could be an issue in this common-mode feedback load?



DC Stability (3)

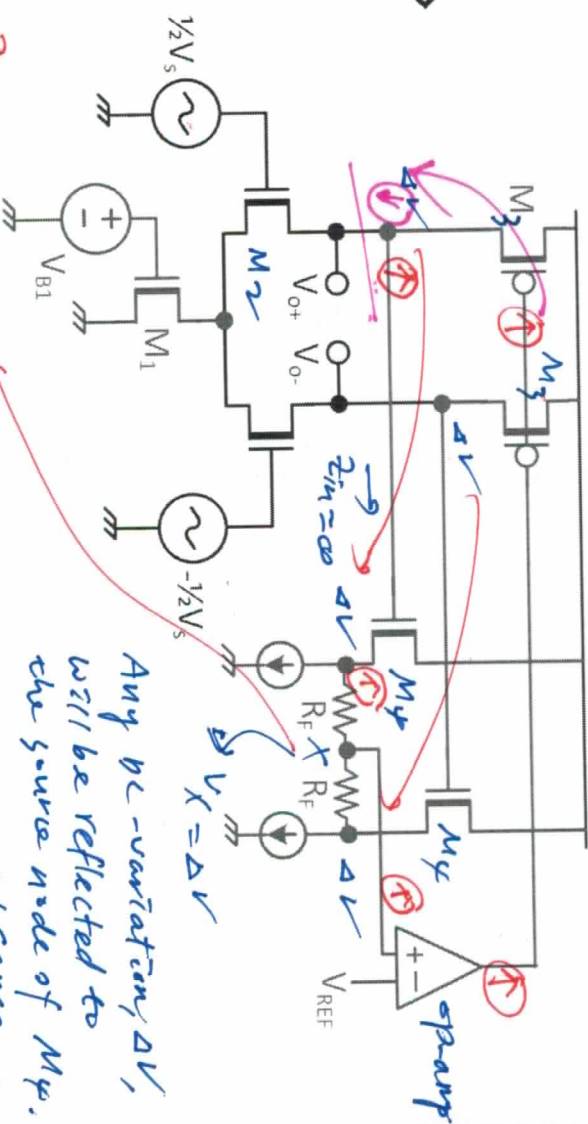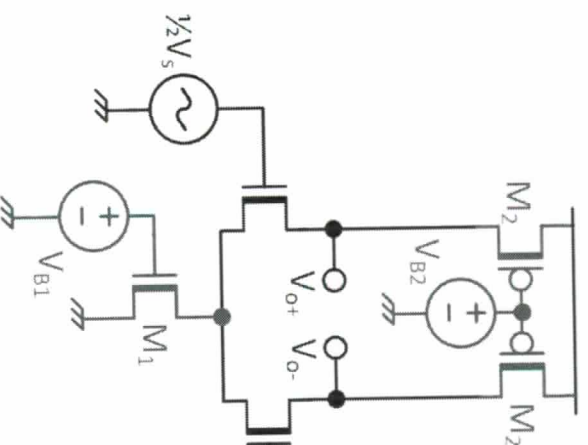(3)

□ Apply buffering first, then common-mode DC feedback (why?)



Buffering

*No voltage headroom sacrifice
No output impedance degradation*

AC-wise node X is virtual ground.

Any dc variation, ΔV , will be reflected to the source node of M_{Y2} .
→ node X will sense ΔV ,

→ op-amp generates a control voltage for PMOS

→ PMOS will suppress the dc variation, ΔV , in negative direction

→ DC negative feedback

⑦




1


Active Loading

□ These topologies are for single-ended output.


Differential output
(passive loading)

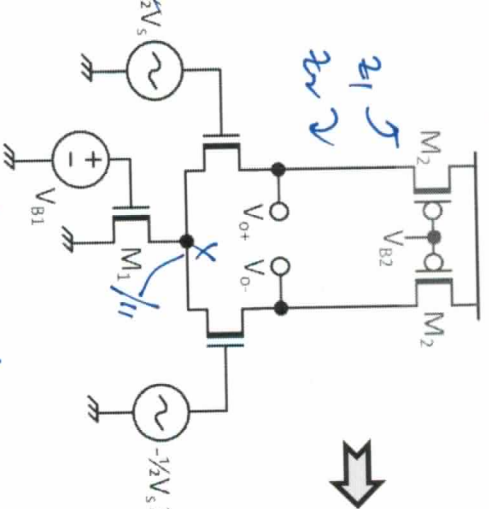


Single-ended output
(passive loading)

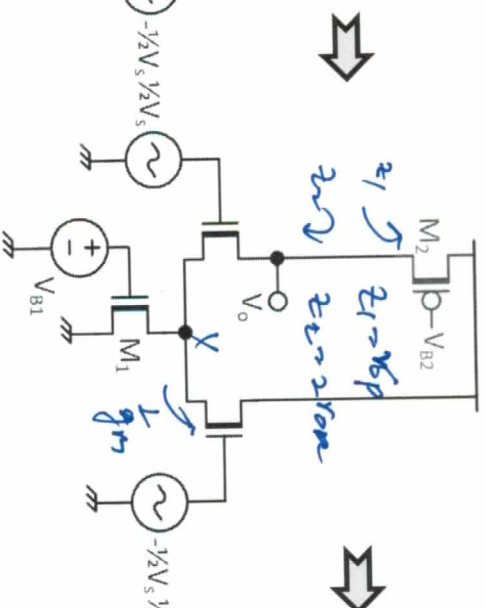

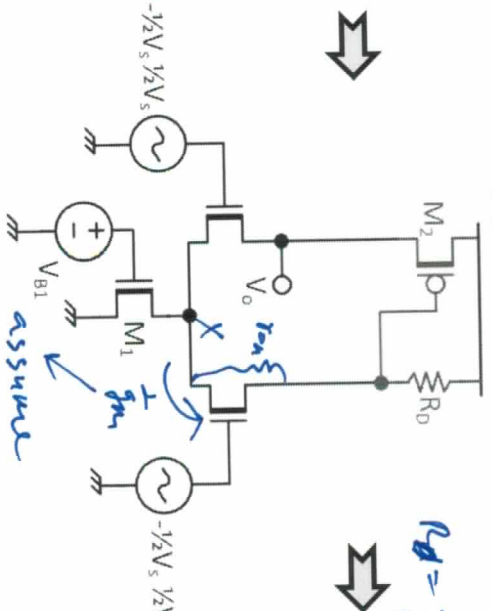Single-ended with active-loading
(by resistor sensing)



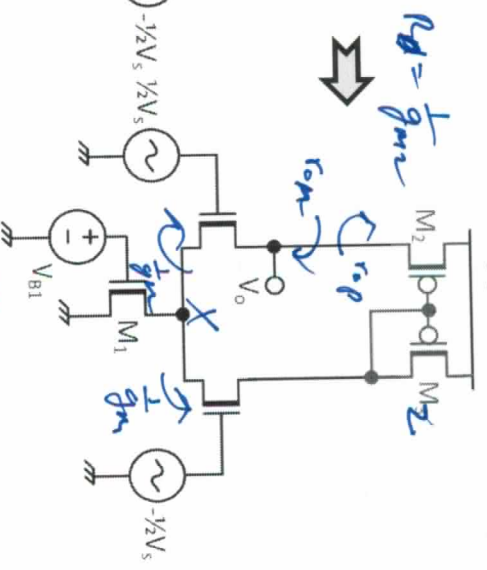Single-ended with active-loading
(by mirroring)



perfect symmetry

→ X ⇒ virtual ground node

$$\rightarrow |Z_1| = r_{op}$$

$$(Z_2 = r_{on})$$

$$\rightarrow A_v = g_m(r_{on} || r_{op})$$

Not symmetry

→ X ⇒ Not virtual ground

assume $R_D \ll r_{on}$

$$R_D = \frac{1}{g_m}$$

$$r_{on} \ll r_{op}$$

can be regarded as symmetry circuit


→ X ⇒ virtual ground

$$\rightarrow A_v = g_m(r_{on} || r_{op})$$

same (see next slides for more details)

Some Comments On Applying Virtual Grounding

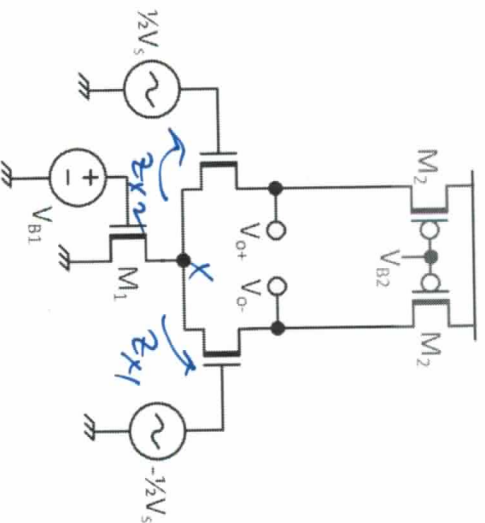□ When can we apply virtual grounding in differential topologies (and when can't)?




$$Z_{X1} = Z_{X2} = Z_X$$

$$V_X \text{ by } \frac{1}{2} V_s \text{ only} \rightarrow V_{X1} = \frac{g_m Z_X}{1 + g_m Z_X} \left(\frac{1}{2} V_s \right)$$

$$V_X \text{ by } \left(-\frac{1}{2} V_s \right) \text{ only} \rightarrow V_{X2} = \frac{g_m Z_X}{1 + g_m Z_X} \left(-\frac{1}{2} V_s \right)$$

$$V_X = V_{X1} + V_{X2} = 0$$

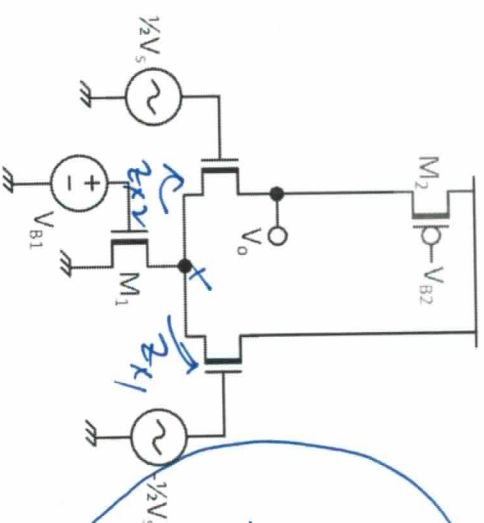$Z_{X1} = Z_{X2} \rightarrow$ can apply virtual ground at node - X.




$$Z_{X1} \neq Z_{X2}$$

$$V_{X1} = \frac{g_m Z_{X1}}{1 + g_m Z_{X1}} \left(\frac{1}{2} V_s \right)$$

$$V_{X2} = \frac{g_m Z_{X2}}{1 + g_m Z_{X2}} \left(-\frac{1}{2} V_s \right)$$

$$V_X = V_{X1} + V_{X2} \neq 0$$

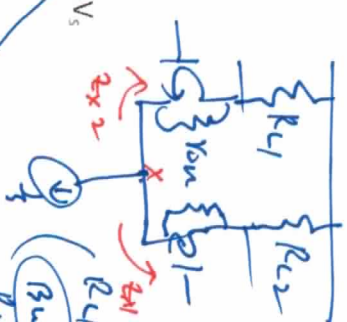\rightarrow can't apply virtual ground at node - X




How about this one?

$$R_{L2} \ll R_{on}$$

$$Z_{X1} \approx Z_{X2} \approx \frac{1}{g_m}$$

\Rightarrow can apply virtual ground at node X

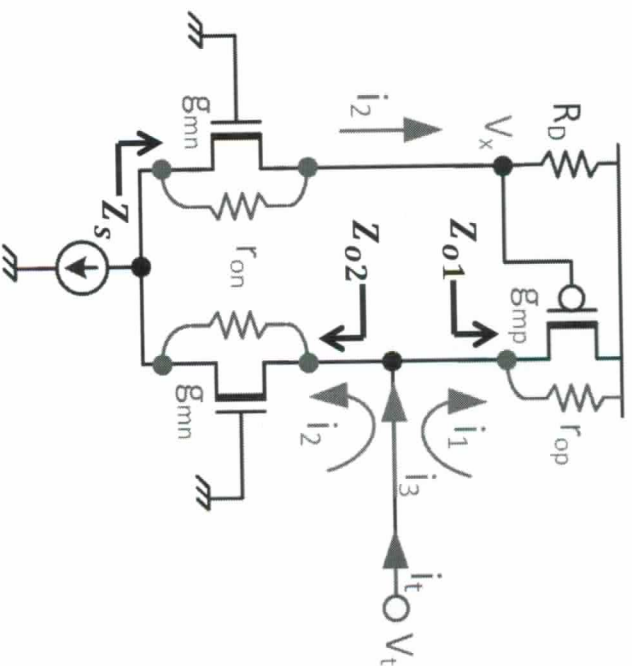Active-Load Output Impedance Calculation (1) (7) (6)



- Assume that $R_D \ll r_{on} \Rightarrow Z_s = \frac{1}{g_{mn}} \Rightarrow Z_{o2} = \frac{v_t}{i_2} = 2r_{on}$
- $Z_{o1} = \frac{v_t}{i_1} = r_{op}$
- There is another current component in the output due to active loading: PMOS will sense V_x and create i_3 .


$$i_3 = g_{mp} v_x = i_2 \times g_{mp} R_D$$

$$\therefore \text{total current } i_t = i_1 + i_2 + i_3 = i_1 + i_2 (1 + g_{mp} R_D)$$

$$\Rightarrow Y_{out} = \frac{i_t}{v_t} = \frac{i_1 + i_2 (1 + g_{mp} R_D)}{v_t} = \frac{1}{Z_{o1}} + \frac{1}{Z_{o2}} (1 + g_{mp} R_D)$$

$$\Rightarrow Z_{out} = \frac{1}{Y_{out}} = Z_{o1} \parallel \frac{Z_{o2}}{(1 + g_{mp} R_D)} = r_{op} \parallel \frac{2r_{on}}{(1 + g_{mp} R_D)}$$

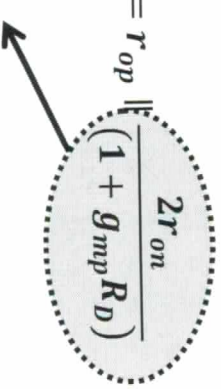
Note: Z_{o2} is divided by $(1 + g_{mp} R_D)$ due to active loading effect.





$$Z_{out} = r_{op} \parallel \frac{2r_{on}}{\left(1 + g_{mp} \frac{1}{g_{mp}}\right)} = r_{op} \parallel r_{on}$$

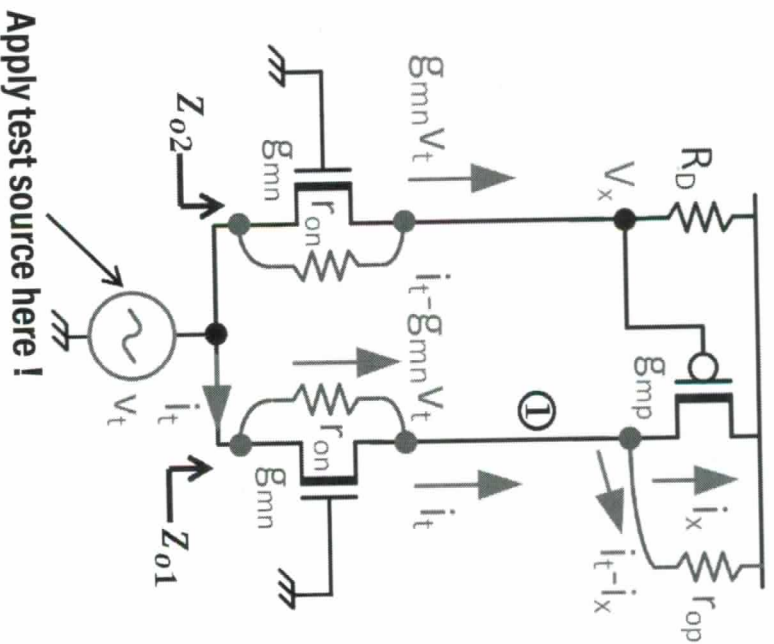Active-Load Source-side Impedance Calculation (1)



□ Assume that $R_D \ll r_{on} \Rightarrow Z_{O2} = \frac{1}{g_{mn}}$

$$\dot{I}_x = g_{mp} v_x = g_{mn} g_{mp} R_D v_t$$

$$\Rightarrow v_{\textcircled{1}} = (i_t - i_x) r_{op} = i_t (1 - g_{mm} g_{mp} R_D v_t) r_{op}$$


$$\Rightarrow v_t = v_{\oplus} + (i_t - g_{mn} v_t) r_{on} = i_t (r_{on} + r_{op}) - (g_{mn} g_{mp} R_D r_{op} + g_{mn} r_{on}) v_t$$

$$\Rightarrow Z_{o1} = \frac{v_t}{i_t} = \frac{r_{on} + r_{op}}{1 + (g_{m1}g_{mp}R_{Dop} + g_{m1}r_{on})}$$

$$\approx \frac{1}{g_{mn} r_{on} + g_{mp} R_{D'} r_{op}}$$

This is a little bit involved expression. But most cases of active-loading, they use PMOS rather than R_D , which will simplify the expression (see next page).

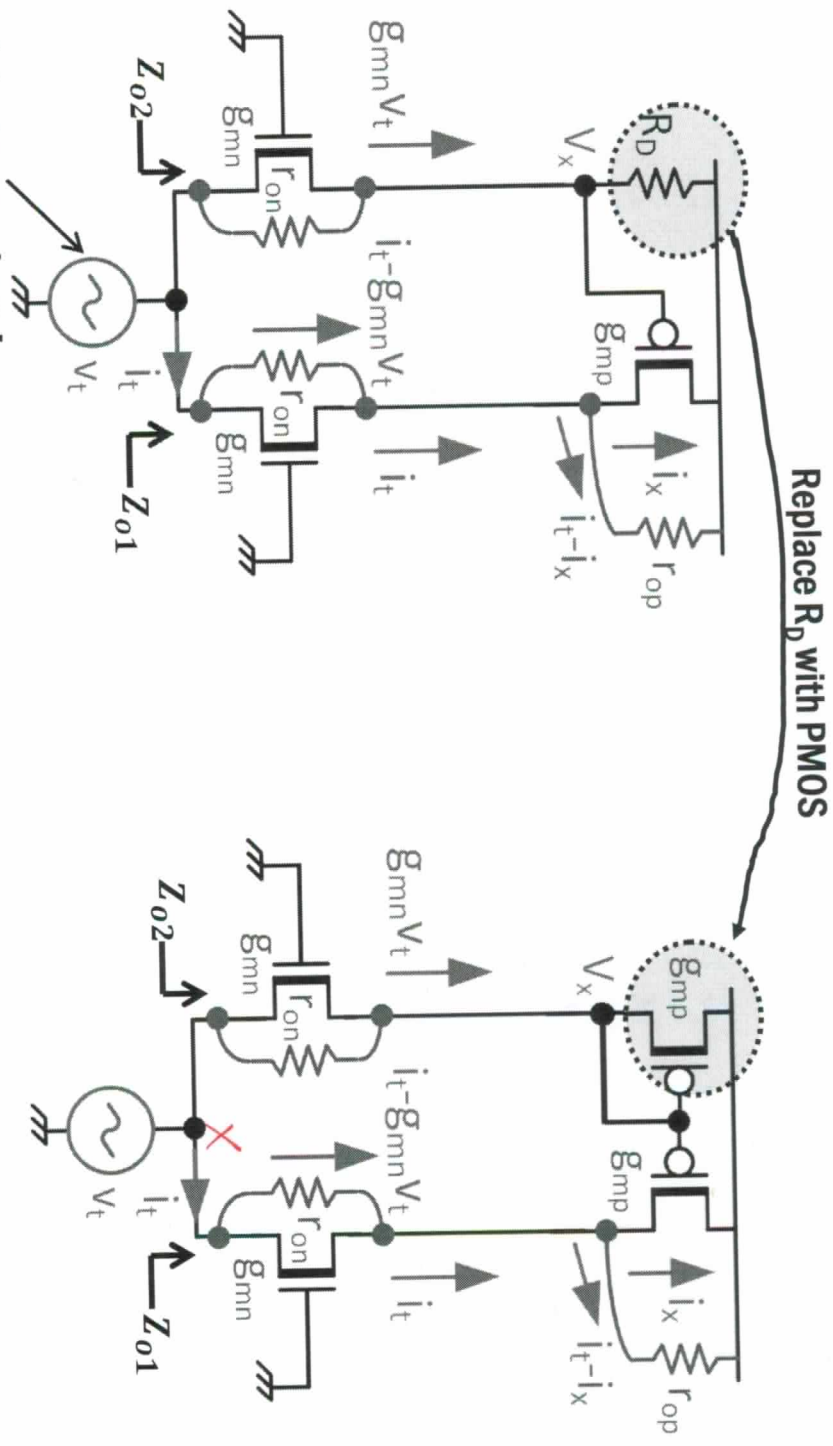Active-Load Source-side Impedance Calculation (2)



Apply test source here !

$$\square Z_{o1} = \frac{v_t}{i_t} \approx \frac{1}{g_{mn} r_{on} + g_{mp} R_D r_{op}}$$

$$\square Z_{o2} = \frac{1}{g_{mn}}$$

$$\square Z_{o1} = \frac{v_t}{i_t} \approx \frac{1}{g_{mn}}$$


$$\square Z_{o2} = \frac{1}{g_{mn}}$$

can apply virtual ground at node X

Common-Mode Rejection Ratio (CMRR)

(11)


Differential-mode

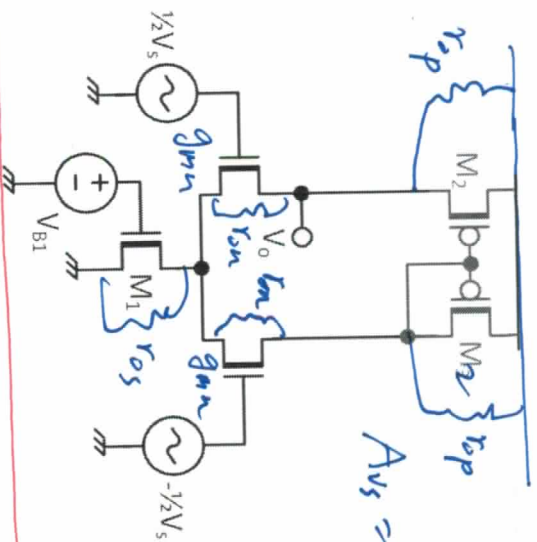

$$A_{vs} = \frac{v_o}{v_s} = g_{m1} R_{out} // R_{op}$$

$$CMRR = \frac{A_{vs}}{A_{v,cm}} = g_{m1} (R_{out} // R_{op}) (2g_{mp} R_{os})$$

Common-mode

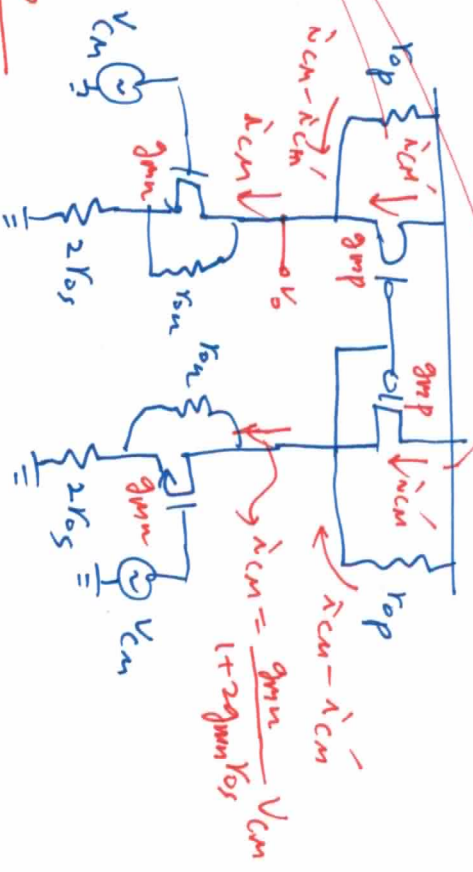

$$\hat{i}_{cm} = \hat{i}_{cm} \cdot \frac{r_{op}}{g_{mp} + r_{op}}$$

$$= \hat{i}_{cm} \frac{g_{mp} r_{op}}{1 + g_{mp} r_{op}}$$

$$\therefore \hat{i}_L = \hat{i}_{cm} - \hat{i}_{cm}' = \hat{i}_{cm} \left(1 - \frac{g_{mp} r_{op}}{1 + g_{mp} r_{op}} \right) = \frac{\hat{i}_{cm}}{1 + g_{mp} r_{op}}$$

$$V_{o,cm} = \hat{i}_L \times R_{op} = \frac{r_{op}}{1 + g_{mp} r_{op}} \cdot \hat{i}_{cm} = \frac{r_{op}}{1 + g_{mp} r_{op}} \frac{g_{m1}}{1 + 2g_{m1} r_{os}} V_{cm}$$


$$\Rightarrow A_{v,cm} = \frac{V_{o,cm}}{V_{cm}} = \frac{g_{m1} r_{op}}{(1 + g_{mp} r_{op}) (1 + 2g_{m1} r_{os})}$$

$$\approx \frac{1}{2g_{mp} r_{os}}$$

Power Supply Rejection Ratio (PSRR)

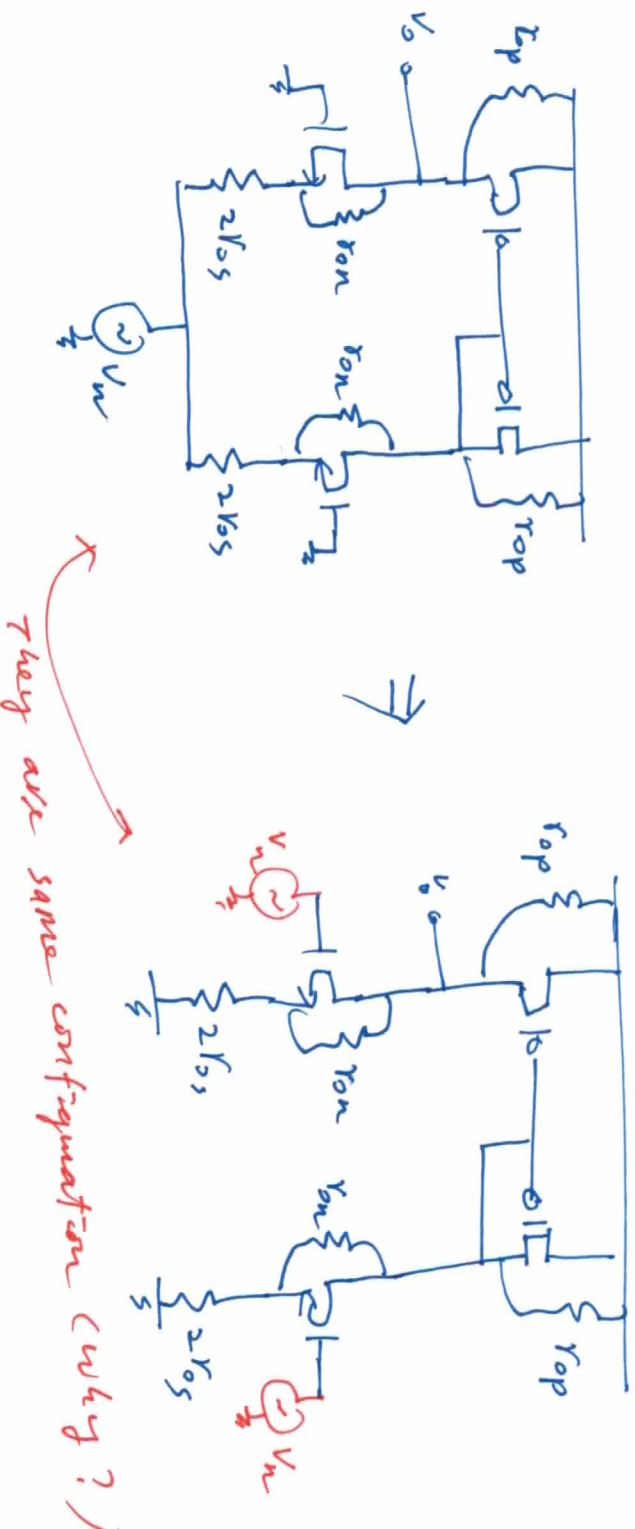(12)


Ground supply rejection ratio ($GSRR$) = $PSRR -$



$$\therefore GSRR (PSRR-) = CMRR$$


Power Supply Rejection Ratio (PSRR)

Power supply rejection Ratio (PSRR)

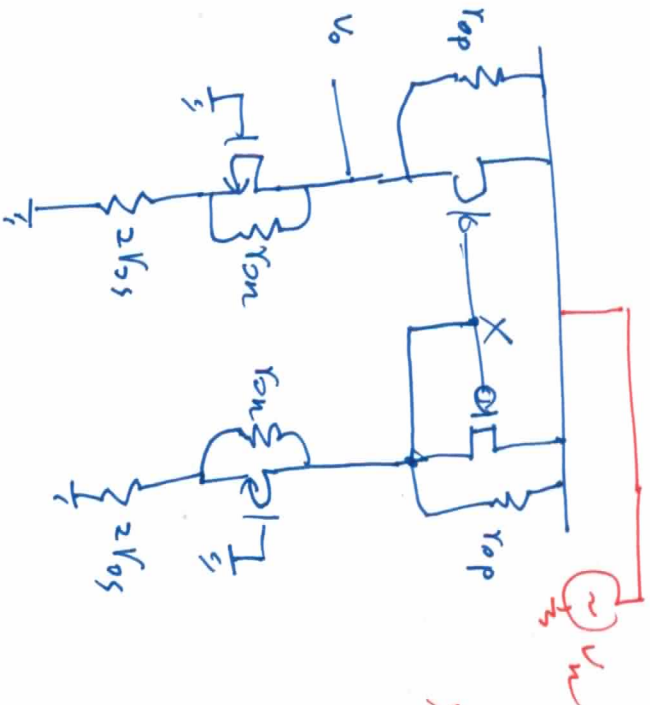

X \rightarrow low impedance node

AC-wise, this PMOS will be off.

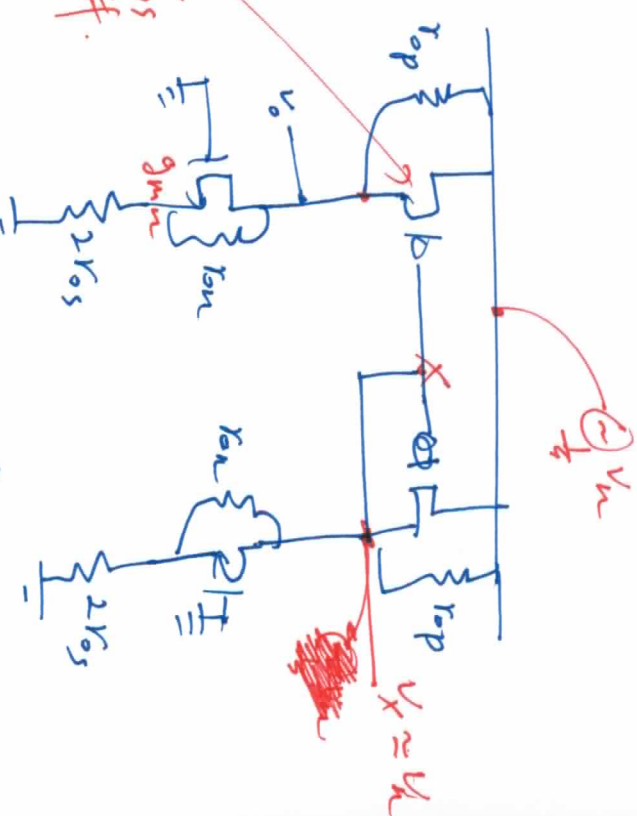

$$\therefore \frac{V_o}{V_n} = \frac{r_{on}(1 + g_{mn} \cdot 2r_{os})}{r_{op} + r_{on}(1 + g_{mn} \cdot 2r_{os})} \approx 1$$

$$\text{PSRR} = \frac{\text{differential-mode signal gain}}{\left(\frac{V_o}{V_n}\right)} = \frac{A_{Vs}}{\left(\frac{V_o}{V_n}\right)} = A_{Vs} = g_{mn}(r_{on} || r_{op})$$

\rightarrow larger gain, better suppression of supply noise