

Mm-Wave Phase Shifter and Phase Array IC Design


Outline

- Introduction- mm-Wave **phase shifter design**
- Passive phase shifters
 - Switched transmission line phase shifter
 - The high-pass/low-pass phase shifter
 - Reflection type phase shifter
- Active Phase shifters
 - Vector-Summing Phase Shifter
 - Quadrature all-pass filters
 - 90° hybrid coupler
- Conclusion

Outline


PHASED ARRAY IC DESIGN

 - PHASED ARRAY RECEIVER @ 12 GHz
 - IC-design, chip & board level verification
- PHASED ARRAY TRANSMITTER @ 44 GHz
 - IC-design & chip level verification
- CONCLUSIONS




Introduction

RF-SCANNED PHASED ARRAY

 

- Need 1 mixer (simple)
- Mixer “sees” high directivity pattern
- Widely used (since 1950)

IF (LO)-SCANNED PHASED ARRAY

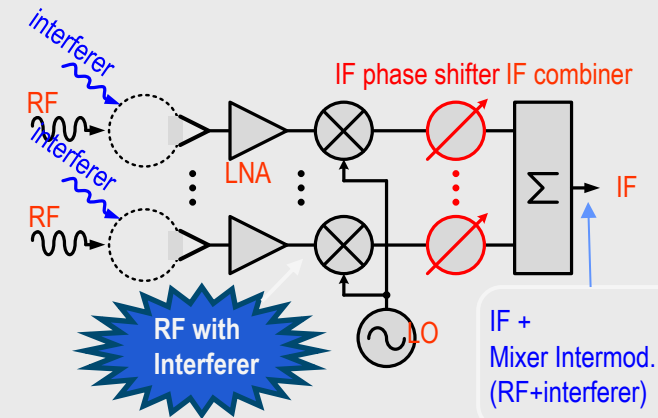

- Need # N mixers (complex)
- Mixer “sees” low directivity pattern
- Limited applications

- For on-chip integration, RF phase shifting is much better (lower power, high linearity)
- RF phase shifting architecture meets backward compatibility with existing systems

Passive Phase Shifters

Switched transmission line phase shifter

Multiple, quasi-distributed, transmission-line Π -sections, combined with MOSFET switches.

This phase shifter has:

➤ **Good linearity performance.**

The main challenge is:


➤ **The loss associated with the MOSFET switches.**

Performance:

4 bit phase-shifter implemented in a $0.13\mu\text{m}$ SiGe BiCMOS technology.

The insertion loss is **13dB** from **30-38GHz**.

Phase error is less than **7°** .

 

Ref: B.W. Min, et al, "Ka-Band BiCMOS 4-Bit Phase Shifter with Integrated LNA for Phased Array T/R Modules", IEEE/MTT-S, June, 2007.

Passive Phase Shifters

The high-pass/low-pass phase shifter

Phase Shift: Difference between the phase response of a high-pass path and a low-pass path.

- Each individual bit is designed for different phase differences.
- Good Linearity Performance

The challenges:


- Losses in the passive elements and the switches.

Performance:

5 bit phase-shifter implemented in a 200GHz SiGe BiCMOS technology,

the insertion loss is **18dB** from **8-12GHz**.

 Absolute rms phase error is less than **8°**




M. Morton, et al "Sources of Phase Error and Design Considerations for Silicon-Based Monolithic High Pass/Low-Pass Microwave Phase Shifters," *IEEE Transactions on Microwave Theory and Techniques*, Dec. 2006.

Passive Phase Shifters

Reflection-Type Phase Shifter (RTPS)

 - ❑ Includes: 4-port directional coupler and purely reflective (imaginary) loads.
- ❑ Phase of the output varies by varying the imaginary termination.



The total phase shift: $-\pi/2 - 2\tan^{-1}(Z_0/X)$,

Z_0 is the impedance to which the ports are matched.

C. T. Charles, et al "A 2-GHz Integrated CMOS Reflective-type Phase Shifter with 675° Control Range," IEEE International Symposium on Circuits and Systems, May 2006.

- For a total phase variation of 180°, the termination capacitance must vary from 0 to ∞ , cannot be realized with varactor.
- To maximize the achievable phase shift range, higher order terminations are employed, such as series LC networks.


Passive Phase Shifters

Reflection-Type Phase Shifter (RTPS)

- **Good linearity performance.**

The main challenge is


- **Loss Associated by Switch and TLs.**

 


Performance:

2GHz phase-shifter implemented in a 0.18 um CMOS process, phase change 343°.

 
The insertion loss is -10dB, and noise figure is 19 dB, for 0-1.8V operation.



Varactor

 

Single resonated load (SRL)

 


Transformed single resonated load (TSRL),

Active Phase Shifters

Vector-Summing Phase Shifter

- Quadrature generation block.
- Variable-gain amplifiers
- Combiner.

 Phase of the output is $\tan^{-1}(A_2/A_1)$




The quadrature generation block can be implemented in a number of ways.

- Quadrature all-pass filters (QAF).
- 90° hybrid coupler.



Vector-Summing Phase Shifter (Quadrature all-pass filters)

Passive signal interpolation for quadrature vector synthesis !

1. Single-ended quadrature generation

 


2. Differential configuration

  

4. Differential Quadrature All-pass Filter (QAF)

3. Elimination by series resonance

 

NOTE

- Step-1: 3-dB gain @ resonance
- Step-3: bandwidth extension
(by removing L-C energy storage pair, de-Q)
- All-pass filter with 3dB NF


TRANSFER FUNCTION

$$\begin{pmatrix} V_{OI\pm} \\ V_{OQ\pm} \end{pmatrix} = V_{in\pm} \times \begin{pmatrix} \underbrace{\frac{s^2 + \frac{2\omega_o}{Q}s - \omega_o^2}{s^2 + \frac{2\omega_o}{Q}s + \omega_o^2}}_{\text{I-path}} \\ \underbrace{\frac{s^2 - \frac{2\omega_o}{Q}s - \omega_o^2}{s^2 + \frac{2\omega_o}{Q}s + \omega_o^2}}_{\text{Q-path}} \end{pmatrix}$$


$$\text{where, } Q = \frac{\omega_o L}{R}, \omega_o = \frac{1}{\sqrt{LC}}$$

Ref: K.-J. Koh et al, "0.13- μ m CMOS phase shifters for X-, Ku-, and K-Band Phased Arrays", IEEE JSSC, Nov. 2007

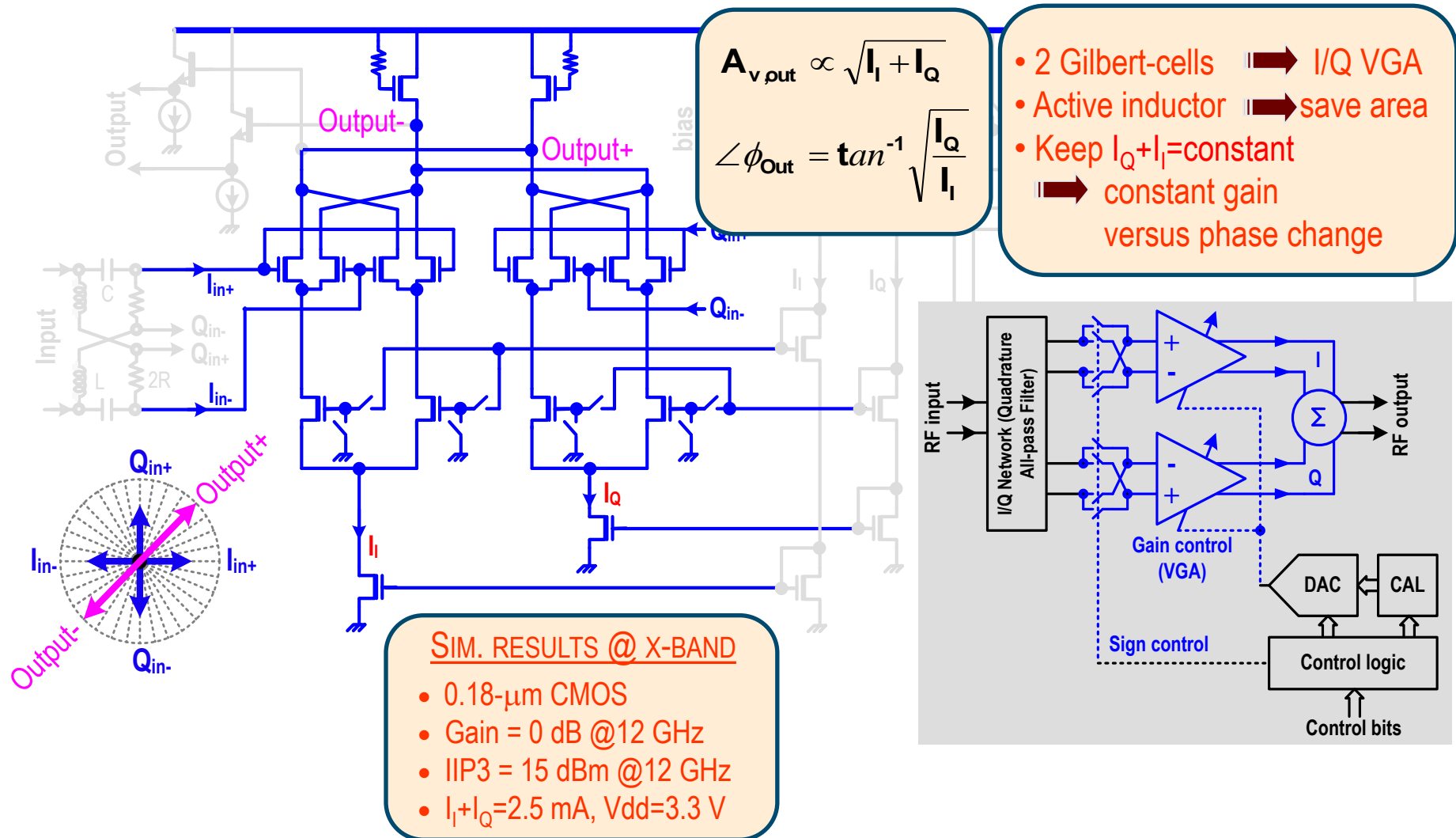Vector-Summing Phase Shifter (Quadrature all-pass filters)



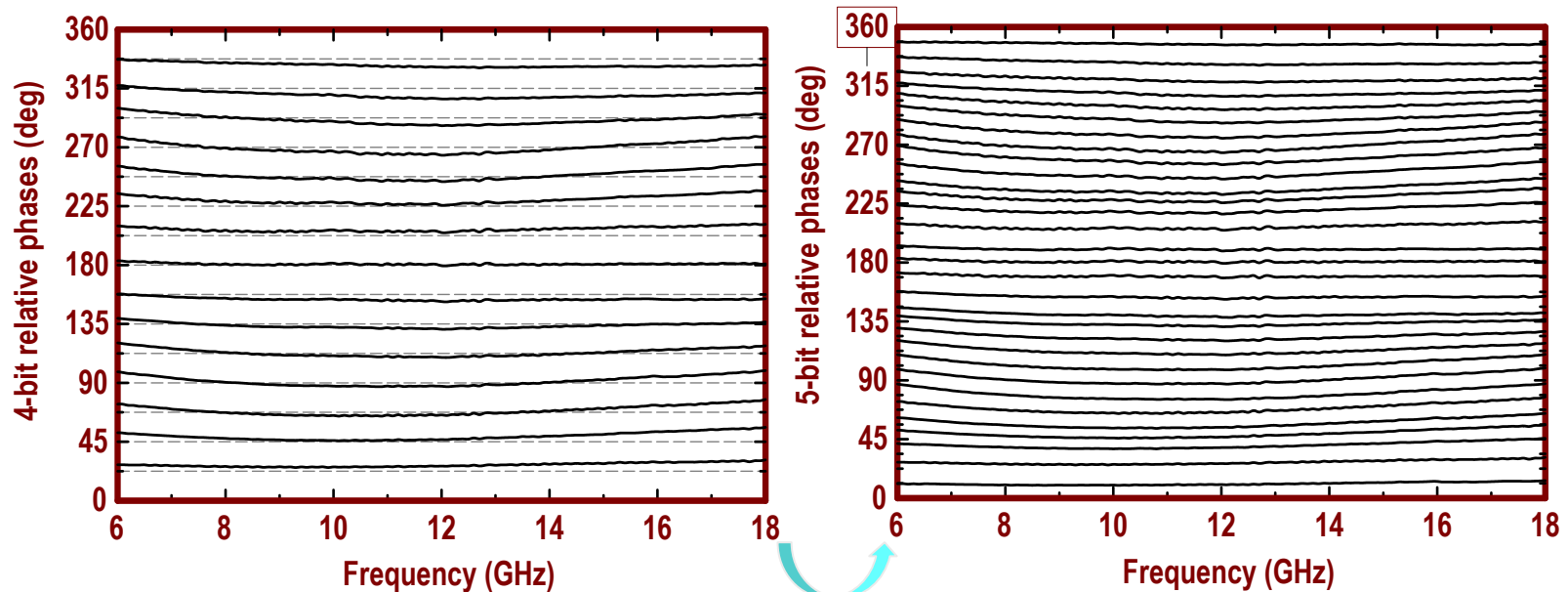ACTIVE PHASE SHIFTER – 4/5-BIT RELATIVE PHASES



After DAC calibration


(Relative phases referenced to 0°-bit phase, RMS phase error < 5.6° @6-18 GHz)

NOTE

- Phase interpolation is an independent process of frequency
- Operational BW is limited by the I/Q network, i.e. the accuracy of I/Q network
- Phase can be easily calibrated using a high resolution DAC (not easy in passive design)

First realization of integrated 5-bit active phase shifter in silicon achieving 6-18 GHz coverage (3:1 BW)

 Vector-Summing Phase Shifter (90° hybrid coupler)




①: **LNA** Compensates for the loss of phase shifter.

② & ④: **Switch Amplifier (functioning as an active switch)**


These switches are used to select the appropriate quadrant that the two orthogonally-phased inputs create the desired phase.

③: **VGA** varies the amplitudes of two orthogonally-phased input signals to get the desired phase within the selected quadrant.

1- 94 GHz Phased Array Front End

 



Frequency(GHz)

 

Frequency(GHz)


- Continuous 360° phase control (shown only 3-bit control here)
- S21: 21-25 dB @94 GHz
- These gain variation can be offset by adjusting VGA (not shown here)
- NF: 8-9 dB @94 GHz

2-120 GHz Phased Array Front End

  


- Continuous 360° phase control (shown only 3-bit control here)
- S21: 16-20 dB @120 GHz
- These gain variation can be offset by adjusting VGA (not shown here)
- NF: 11-12 dB @120GHz

94 GHz Phased Array Front End: Layout

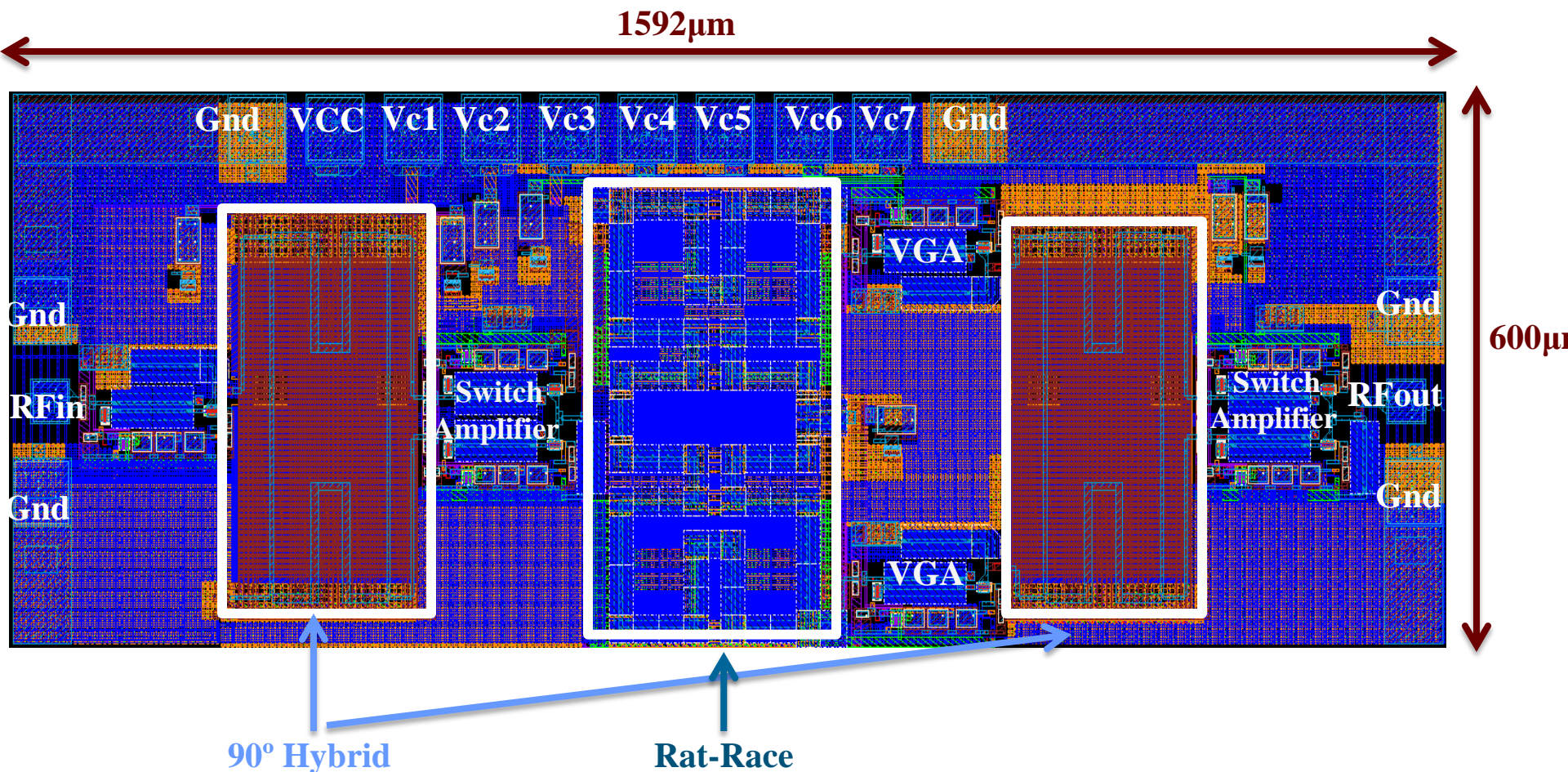

□ Supply 2.5 V , Total current 44mA

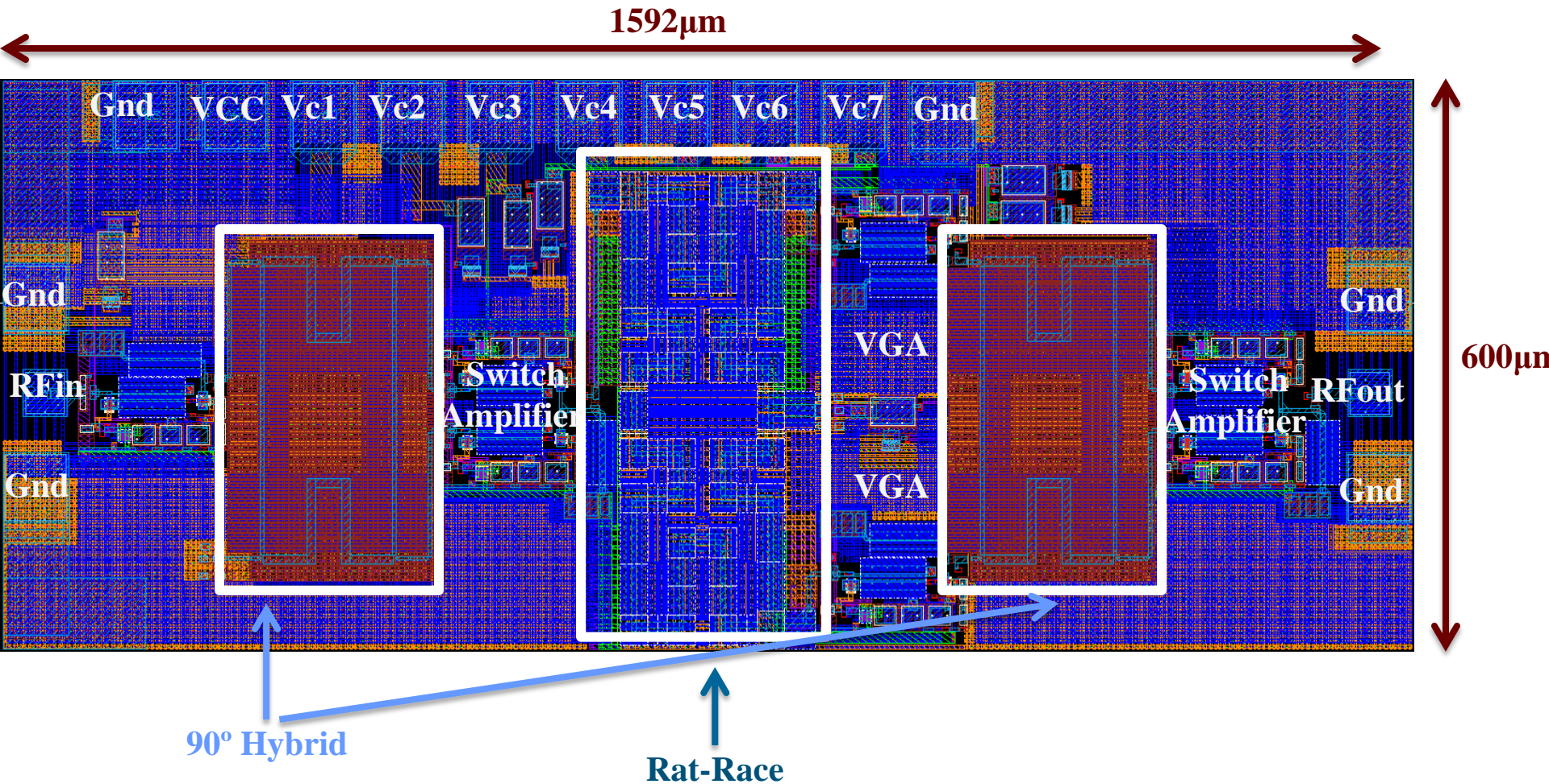2. 120 GHz Phased Array Front End: Layout




□ Supply 2.5V ,Total Current 37mA

Conclusion


- Passive phase shifters have good linearity performance, but the main challenge is the loss associated with the passive elements and switches.
- Their physical sizes make them impractical for integration with multiple arrays in a commercial IC process, especially below K band frequencies (< 30 GHz).
- Active phase shifters can achieve a high integration level with decent gain and accuracy along with a fine digital phase control under a constrained power budget.
- The most challenging part of realizing active phase shifters is the quadrature generation block which can be implemented by quadrature all-pass filters (at lower frequencies) and a 90° hybrid coupler (at higher frequencies).

PHASE ARRAY IC DESIGN

 
- PHASED ARRAY RECEIVER @ 12 GHz
 - IC-design, chip & board level verification
- PHASED ARRAY TRANSMITTER @ 44 GHz
 - IC-design & chip level verification
- CONCLUSIONS



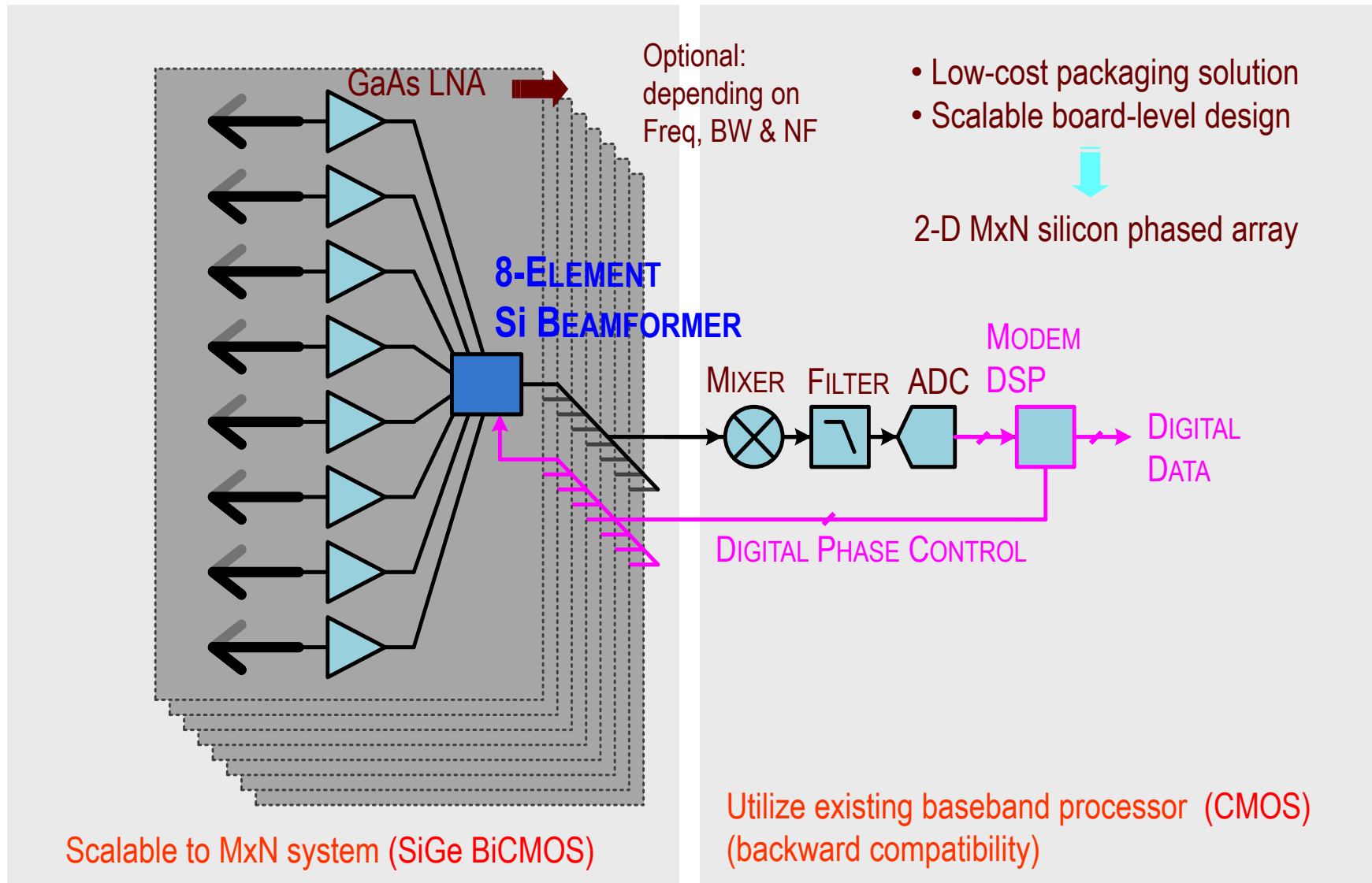8-ELEMENT PHASED-ARRAY (12 GHz, SCALABLE ARRAY)



8 ELEMENT SI BEAMFORMER: PHASE SHIFTER

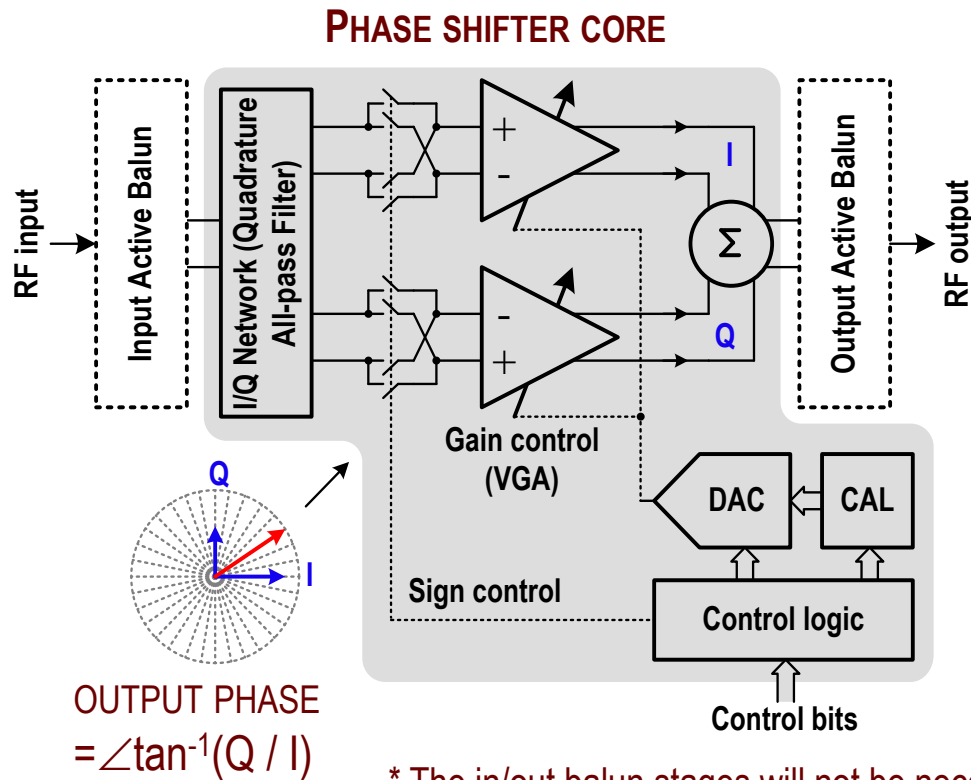

* The in/out balun stages will not be necessary for fully integrated differential systems

OPERATION

- Balun provides differential signal
- I/Q network splits signal into I & Q vector signals
- VGA controls gain for I & Q path
- I/Q signals are added in V-domain (phase interpolation)
- DAC provides 4-bit phase control
- CAL calibrates DAC to get 5-bit phase resolution


Mostly active circuits ➡

Small chip area & Gain

DAC control ➡


Fine accurate phase control & calibration

ACTIVE PHASE SHIFTER - SCHEMATIC

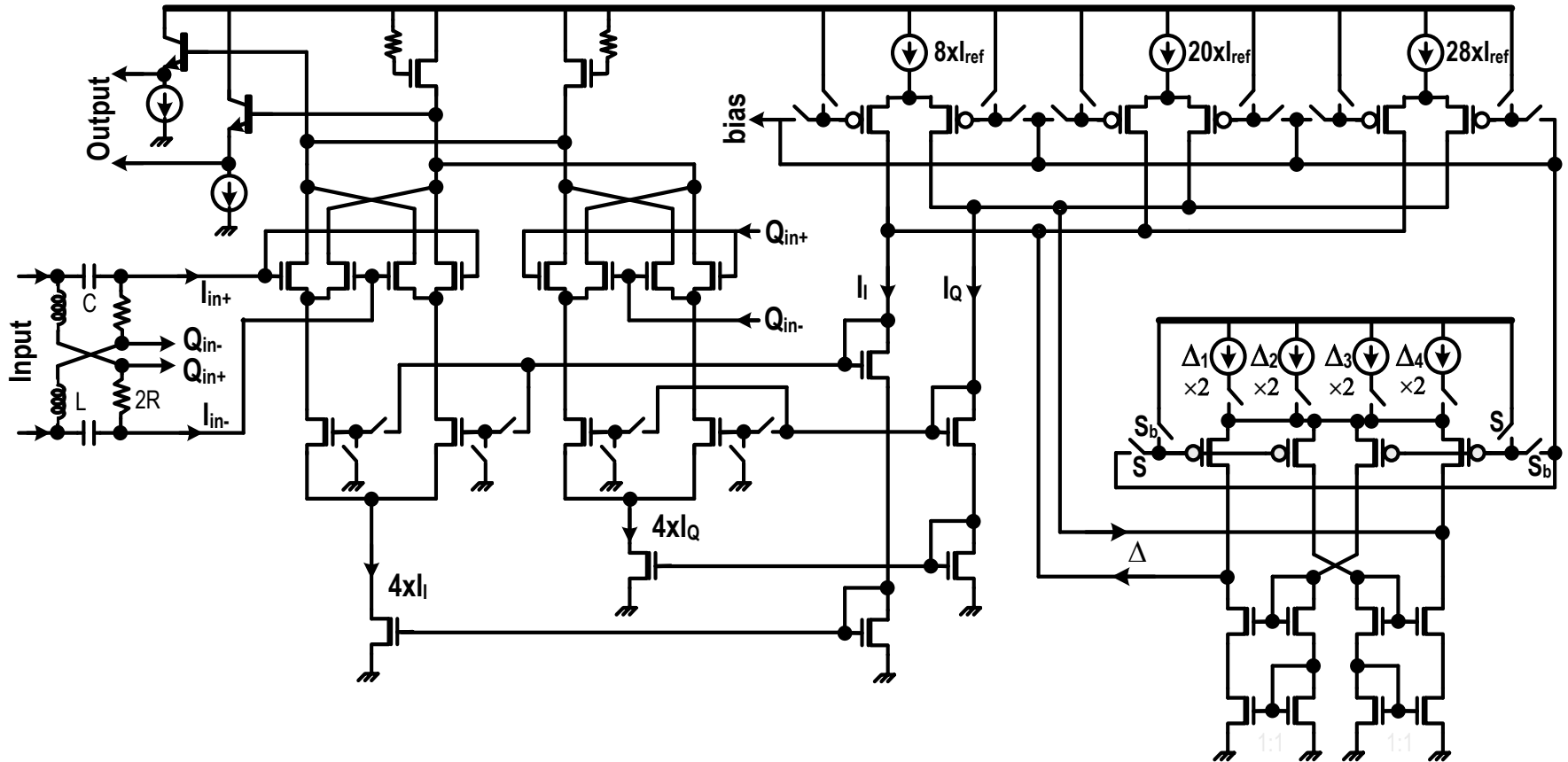


Ref: K.-J. Koh et al, "0.13- μ m CMOS phase shifters for X-, Ku-, and K-Band Phased Arrays", IEEE JSSC, Nov. 2007

ACTIVE PHASE SHIFTER – CHIP PHOTO

 



- Supported by “DARPA SMART project” (2006-2008)
- Presented at the DARPA meeting & MTT-s 2010
- Lockheed Martin bought the designs (schematic & layout), 2009

 - 0.18- μm SiGe BiCMOS process (Phase shifter: 0.18- μm CMOS)
- Chip size: 1.2 x 0.7 mm² (Phase shifter: 0.4 x 0.3 mm²)
- Total current: 18.7 mA ($V_{DD}=3.3$ V)




- All pads are ESD protected (HBM rating: 3kV, 2A)

 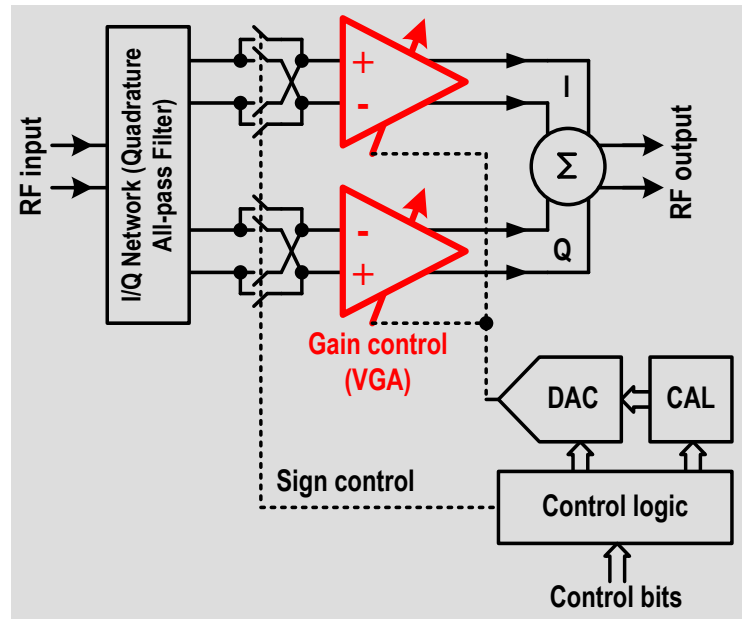ACTIVE PHASE SHIFTER – TEMPERATURE MEASUREMENTS




- I & Q paths are biased with a reference PTAT circuit
- Output phase depends on I:Q gain ratio (not absolute gain)
- I & Q amplifiers track each other vs. PVT, resulting in low sensitivity to PVT
- RMS phase error < 6° @ 25°-100° C

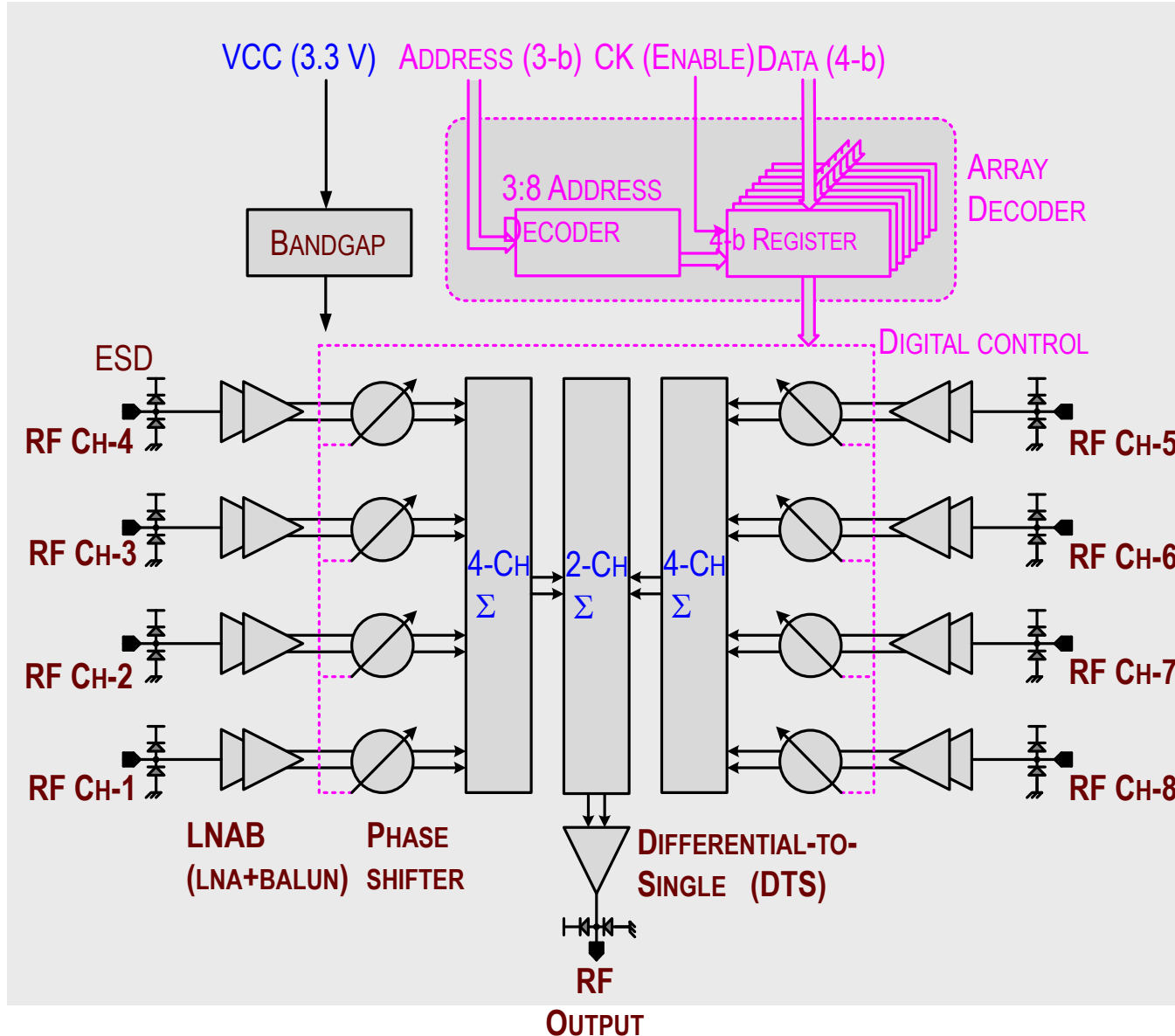8-ELEMENT PHASED-ARRAY (12 GHz, ARCHITECTURE)




- Integrate 8-CHs in SiGe
- Integrate “RF + DIGITAL”
- 4-bit active phase shifter
- 2-step signal combining (active adders)
- ESD protection (3kV, 2A)




 
8-ELEMENT PHASED-ARRAY (12 GHz, CHIP PHOTO)






 
- 0.18- μm SiGe BiCMOS
(Jazz SiGe120, 1P6M, $f_T=150$ GHz)
- Area = $2.2 \times 2.4 \text{ mm}^2$
- Near perfect corporate-feed layout
(E-length btw any input to output is identical)
- Metallic barrier: max CH-CH isolation
- $V_{CC}=3.3 \text{ V}$, $I_{total}=170 \text{ mA}$
(561 mW, Active- $\Sigma < 10\%$)



    
8-ELEMENT PHASED-ARRAY (12 GHz, GAIN, NF, MATCHING)



    
8-ELEMENT PHASED-ARRAY (12 GHz, PHASE, GROUP DELAY)



 
8-ELEMENT PHASED-ARRAY (12 GHz, CH-TO-CH VARIATION)



 - Comparison of 128 S-Parameters
= 8 (channels) x 16 (4-bit phases)
- Excellent matching between array elements
→ Major benefit in the on-chip integration



 8-ELEMENT PHASED-ARRAY (12 GHz, CHIP-ON-BOARD, ANGLED-DIPOLE)




Rogers RT5880 Teflon substrate ($\epsilon_r=2.2$, $h=10$ mils)

ANGLED-DIPOLE ANTENNA:


Wider beam width, Lower mutual coupling , Wideband S11
 HPBW: 102°, S11<-10 dB @10.5-14 GHz, S21<-17 dB
 Scan angle: +/- 60° w/ 4dB drop in element factor

ANGLED-DIPOLE SINGLE ELEMENT E-PATTERN


 


Ref: Y. A. Atesal, B. Cetinoneri, K.-J. Koh, G. M. Rebeiz, "X/Ku-Band 8-Element Phased Arrays Based on Single Silicon Chips", 2010 IMS, May 2010

 8-ELEMENT PHASED-ARRAY (12 GHz, CHIP-ON-BOARD, CHIP MOUNTING)




BONDWIRE & COUPLING SIMULATION WITH HFSS

  

Worst-case coupling < -17 dB, bondwire inductance: 0.5 nH


 
SILICON PHASED ARRAY CHIP (2.2 x 2.4 mm²)



Ref: Y. A. Atesal, B. Cetinoneri, K.-J. Koh, G. M. Rebeiz, "X/Ku-Band 8-Element Phased Arrays Based on Single Silicon Chips", 2010 IMS, May 2010

8-ELEMENT PHASED-ARRAY (12 GHz, BOARD MEASUREMENT SETUP)


ANECHOIC ANTENNA CHAMBER

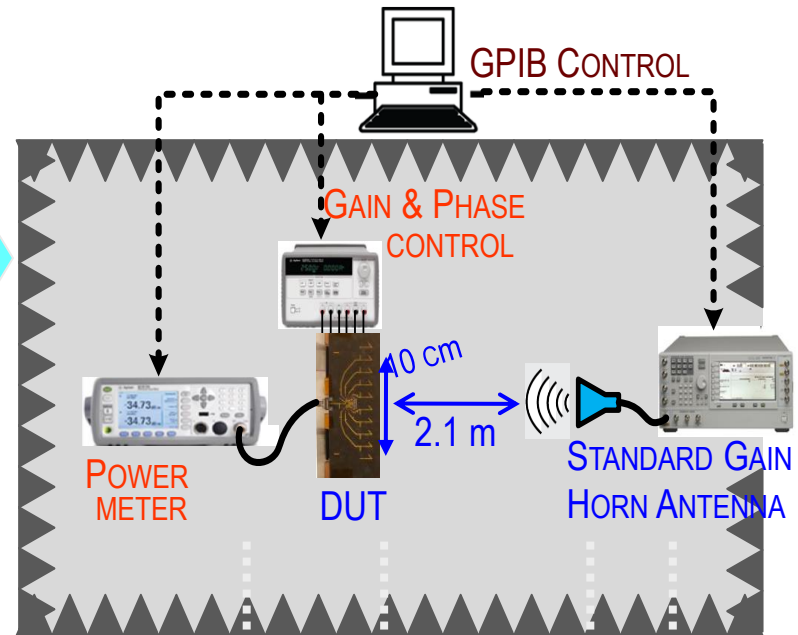 

Friis TRANSMISSION EQUATION


$$\frac{P_R}{P_T} = \underbrace{G_T}_{\text{Horn ANT gain}} \times \underbrace{\left(\frac{\lambda}{4\pi \cdot R} \right)^2}_{\text{Free space path loss}} \times \underbrace{G_R}_{\text{Phased array gain}}$$

= 20 dB	= -60.5 dB	= 41 dB
	R: 2.1 m	Channel gain (20 dB)
	λ : 2.5 cm	Array factor (18 dB)
	@12 GHz	Antenna gain (3 dB)

 


8-ELEMENT PHASED-ARRAY RX (12 GHz, BOARD MEASUREMENT)

MEASURED PATTERN @12 GHz

 

MEASURED PATTERN @11.4-12.6 GHz

 


- Scanned from -60° to 60°
- Element factor causes 3-4 dB drop at 60°
- HPBW: 15° @ 0° -scan, 19° @ 30° -scan, 26° @ 60° -scan
- Excellent agreement with simulations

- No-true-time delay on each element
- Slight beam walk @ 60° - scan angle
- Instantaneous BW limited to 11.4-12.6 GHz ($\Delta=1.2$ GHz, 10%)

First system-level (w/ antenna) demo of an X-band array based on a single silicon chip !

AREA COMPARISON: SINGLE VS 8-ARRAY

 

3.5 mm

SINGLE ELEMENT


PHASE SHIFTER

3.8 mm

Ref: Comeau et al (Georgia Tech), "A SiGe Receiver for X-Band T/R Radar Modules", IEEE JSSC, Sept. 2008

Integration ($A=13.3 \text{ mm}^2$):
LNA + Phase shifter + bias c.k.t.
(single element: analog)

 COMPARE
(8-element array
is 40% size
of the passive
single-element)



2.4 mm

8 ELEMENTS + DIGITAL


2.2 mm

Ref: K.-J. Koh et al, "An X- and Ku-Band 8-Element Phased-Array Receiver in 0.18- μm SiGe BiCMOS Technology", IEEE JSSC, June 2008

Integration ($A=5.3 \text{ mm}^2$):
8 LNAs + 8 Phase shifters + bandgap
(8 elements: analog)
+
Array decoder (digital control)


PHASE ARRAY IC DESIGN

 - PHASED ARRAY RECEIVER @ 6-18 GHz
 - IC-design, chip & board level verification
- PHASED ARRAY TRANSMITTER @ 44 GHz
 - IC-design & chip level verification
- CONCLUSION



16-ELEMENT mm-WAVE PHASED-ARRAY TX (LARGE ARRAY, 3-D INTEGRATION)

 PROJECT: DARPA SCALABLE MILLIMETER-WAVE ARRAY TECHNOLOGY (SMART, 2006-2008)




- Q-band satellite comm. (43-45 GHz, $\lambda/2=3.4$ mm)
- Large array: 20x20 elements
- Microstrip antenna size = 3.4×3.4 mm²
- Integrate 1 sub-array (4x4) in a single package (Area < 3x3 cm²)



Multi-layered integration in a single package

TILE-BASED 2-D LARGE ARRAY (20x20) CONSTRUCTION
ONE TILE (SUB-ARRAY): 4x4 ELEMENT, ONE SUPER-TILE: 5x5 TILES

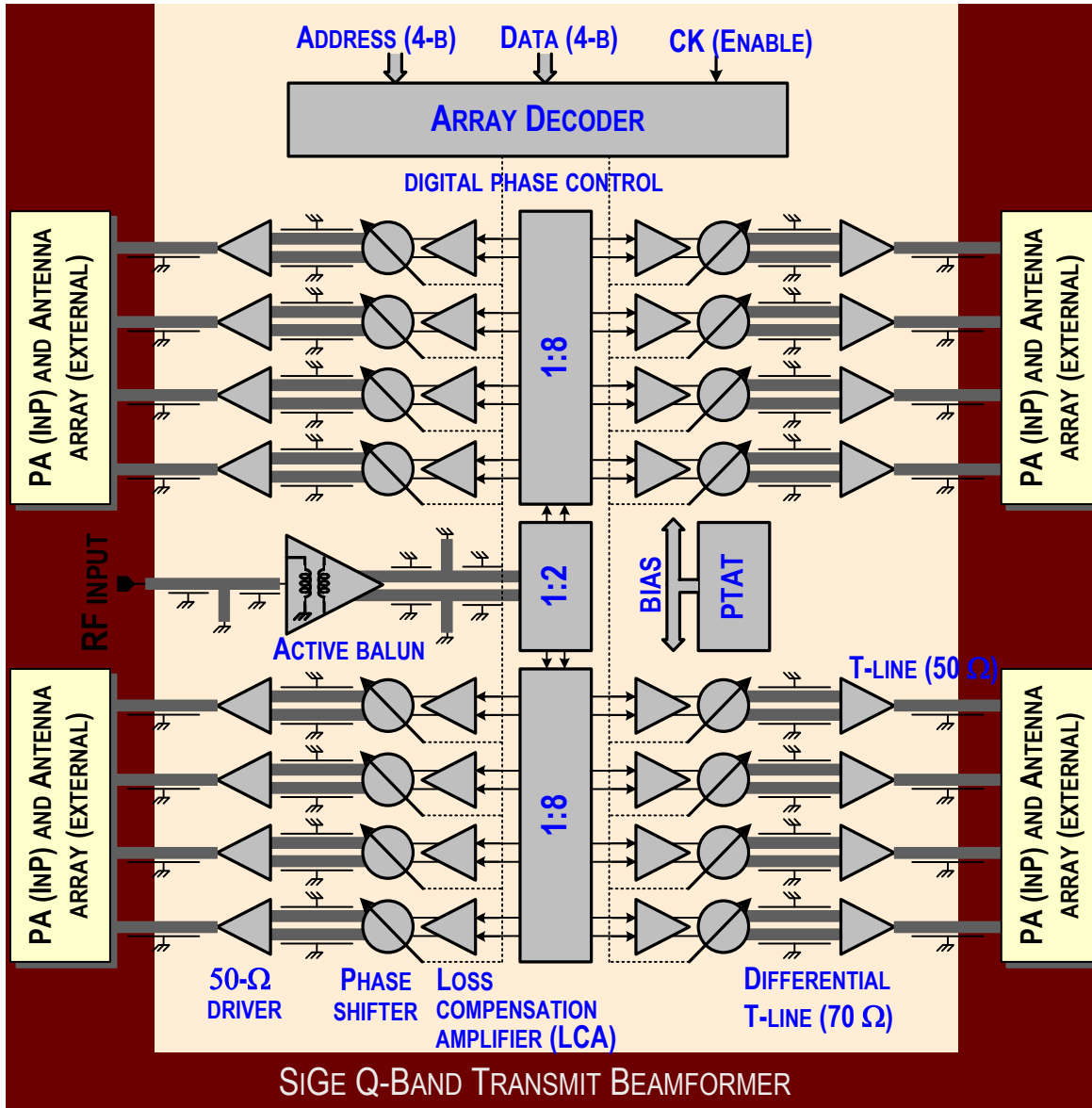
16-ELEMENT mm-WAVE PHASED-ARRAY Tx (44 GHz, ARCHITECTURE)




- 44 GHz satellite comm. application
- Integrate 16 elements (4x4)
- Corporate feed architecture
 - Active balun, 1:2 active, 1:8 passive
- Single channel elements
 - LCA: compensate 1:8 division loss
 - 4-bit active phase shifter
 - 50-Ω driver drives external PA
- Array decoder
 - control each channel independently

Ref: K.-J. Koh *et al*, "A Millimeter-wave (40-45 GHz) 16-Element Phased-Array Transmitter in 0.18-μm SiGe BiCMOS Technology", IEEE JSSC, May 2009


 
16-ELEMENT mm-WAVE PHASED-ARRAY TX (44 GHz, CHIP PHOTO)



 
- 0.18- μm SiGe BiCMOS technology
 - 1P6M, $f_T=150$ GHz
- Size: 2.6 x 3.2 mm² (overall)
- Near perfect corporate-feed layout
 - E-length is identical for all channels
- Metallic barrier
 - Grounded via stacks from M1-M6
 - Decrease ch-to-ch coupling
- Current consumption: 724 mA (5 V, 3.6 W)



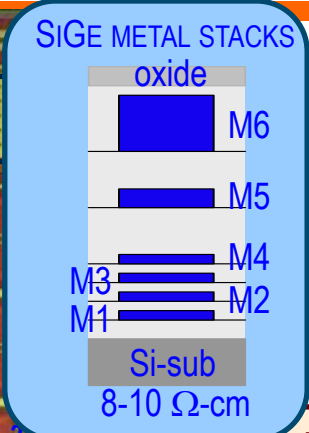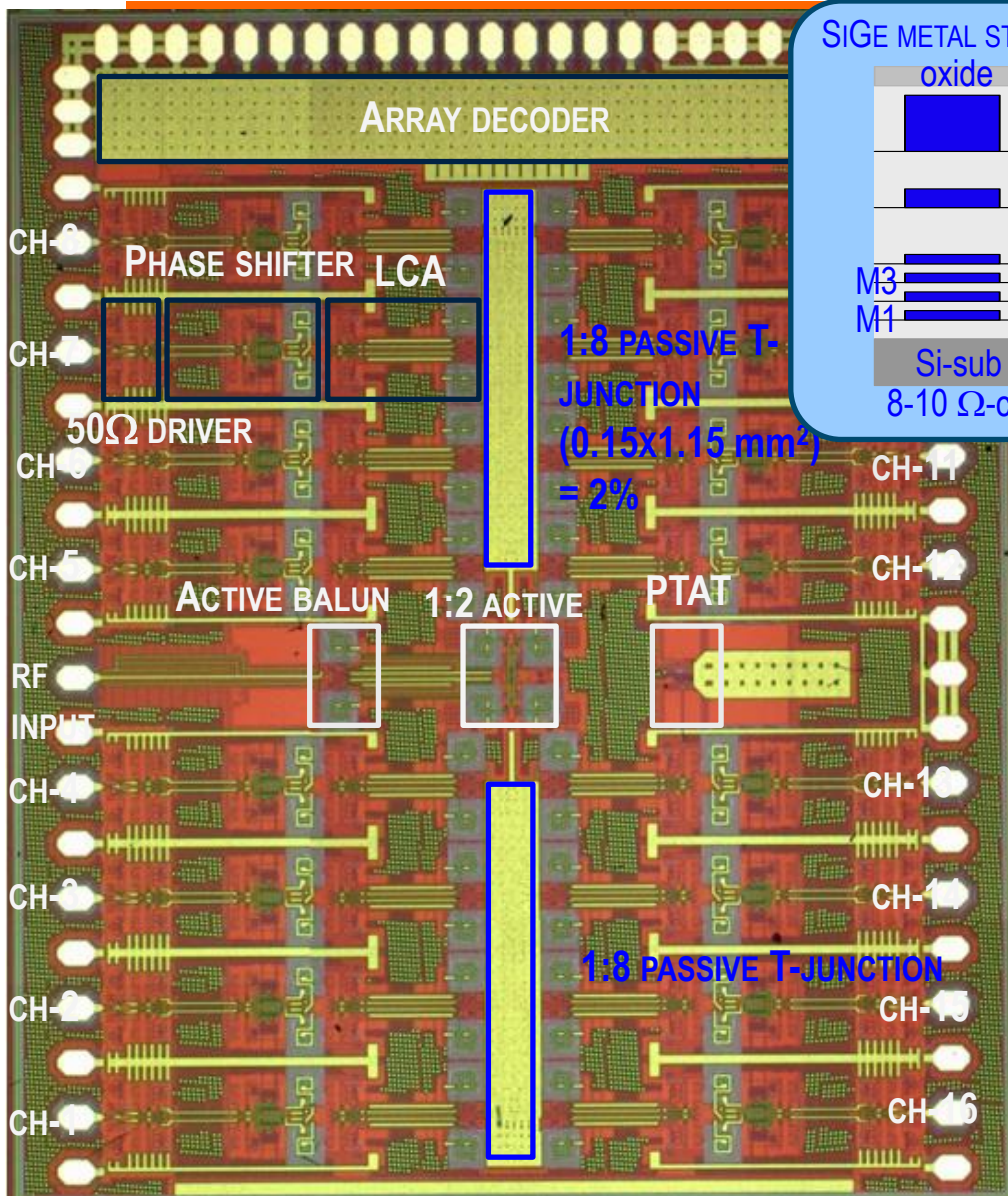16-ELEMENT mm-WAVE PHASED-ARRAY TX (44 GHz, 1:8 T-JUNCTION)




SHIELDED BROADSIDE-COUPLED DIFF-T-LINE

 


- Perfectly shielded (no coupling btw T-lines)
- Allow compact integration of many diff T-lines


1:8 TEE-JUNCTION DIVIDER

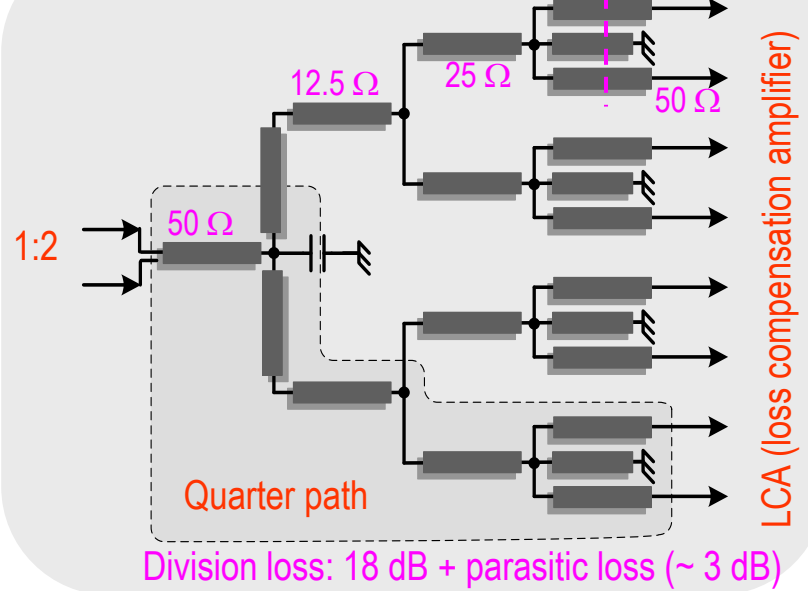

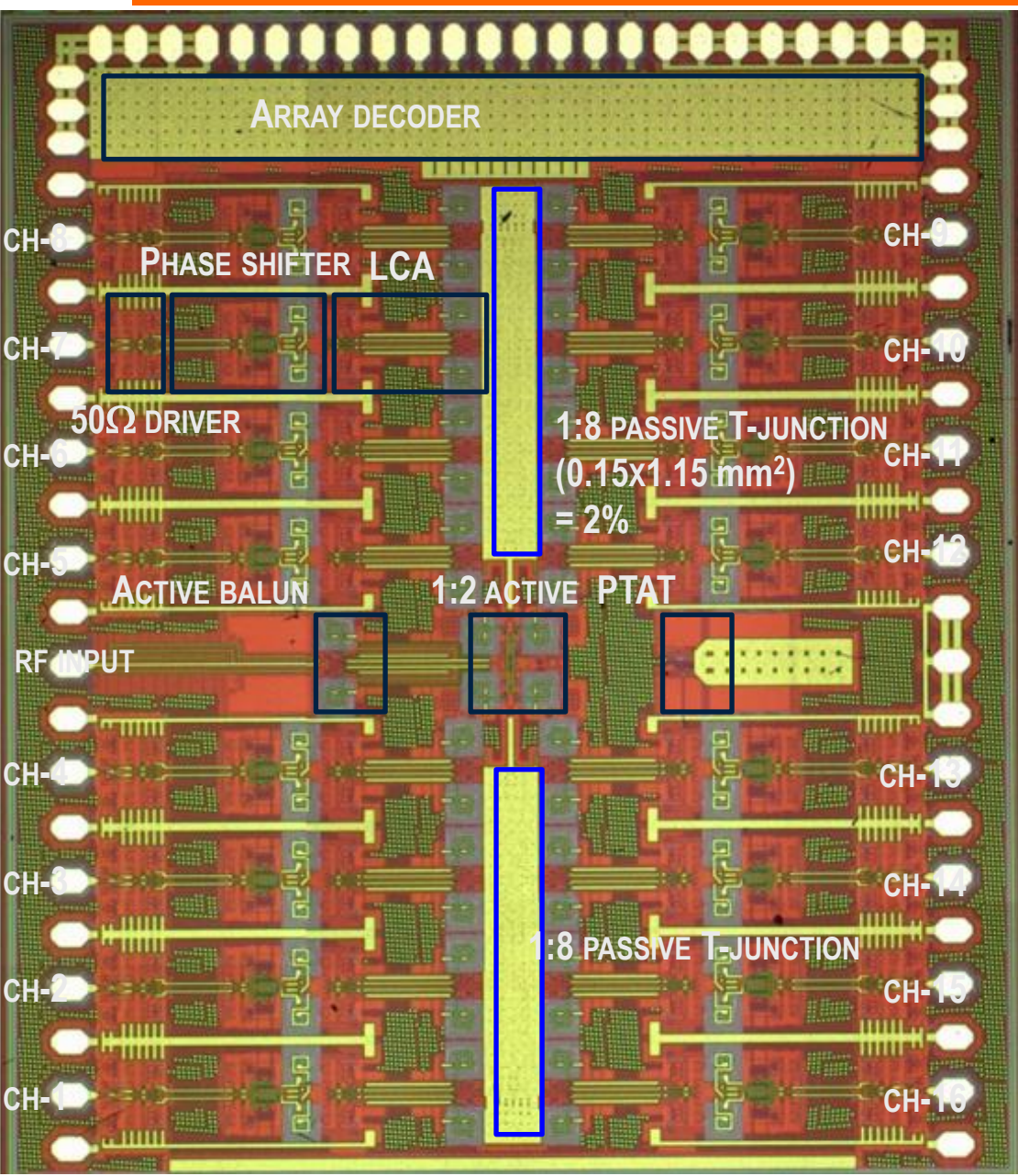16-ELEMENT mm-WAVE PHASED-ARRAY TX (44 GHz, COAXIAL T-LINE)




SHIELDED BROADSIDE-COUPLED DIFF-T-LINE

 


- Perfectly shielded (no coupling btw T-lines)
- Allow compact integration of many diff T-lines

ODD-MODE E-FIELDS

 

EVEN-MODE E-FIELDS

 

- $W=3\text{ }\mu\text{m}$: odd-mode impedance= $50\text{ }\Omega$ (HFSS sim)
- Most fields ($> 95\%$) are confined btw diff-T lines
- Measured loss: 3 dB / 0.5 mm @45 GHz


16-ELEMENT mm-WAVE PHASED-ARRAY Tx (44 GHz, MEASUREMENT)

PARAMETER	RESULTS
Technology	0.18- μ m SiGe BiCMOS (Jazz SiGe120, 1P6M)
Supply voltage	5 V (analog), 3.3 V (digital)
Current consumption	I_{bias} =720 mA (44 mA per channel)
Frequency band	Q-band (3-dB BW: 40-45.5 GHz)
Phase resolution	4-bit (accuracy > 5-bit)
Input return loss	< -10 dB @ 36.6-50 GHz
Output return loss	< -10 dB @ 37.6-50 GHz
Power gain (ave)	12.5 dB @ 42.5 GHz
Maximum output power	-2.5 \pm 1.5 dBm @ 42.5 GHz
Phase error (RMS)	< 8.8° @ 30-50 GHz
Gain error (RMS)	< 1.3 dB @ 30-50 GHz
Output P_{1dB}	-5 \pm 1.5 dBm @ 42.5 GHz
Phase mismatch (RMS)	< 7° @ 30-50 GHz (between all channels)
Amp. mismatch (RMS)	< 1.8 dB @ 30-50 GHz (between all channels)
Isolation (CH-to-CH)	< -30 dB @ 30-50 GHz
Array factor directivity	12 dB (16-element)
Chip area	2.6 x3.2 mm ²

SINGLE CHANNEL

16-ARRAY

 BEAM PATTERN BASED ON MEASURED S-PARAMETERS
(16 S-PARA X 16 CHANNELS= 256 S-PARA)




ASSUMPTION


- Isotropic radiator, uniform array spacing, $d=\lambda/2$
- Ideal 45°-scan: $127.3^\circ (= 360^\circ \times d/\lambda \times \sin 45^\circ)$

CONCLUSIONS

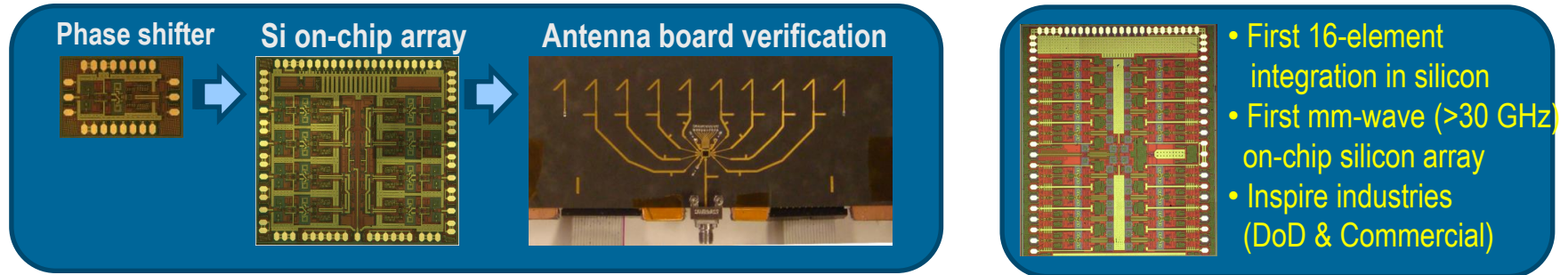- Provide a low-cost phased array solution for RF and mm-wave defense & commercial applications
- First implementation of *All-RF (RF-scanning)* Si phased array IC including system-level demonstration



 
- Successful technology transfers to DoD industries (Boeing, Lockheed Martin, Raytheon, Teledyne, NG)



- Designs can be extended for high data-rate wireless systems at mm-wave frequencies (60 GHz wireless comm., > 100 GHz high data rate mm-wave comm. ...)
- SiBeam, IBM, MTK, Intel ... all use now the *All-RF* based phased array architecture.


BACK-UP SLIDES

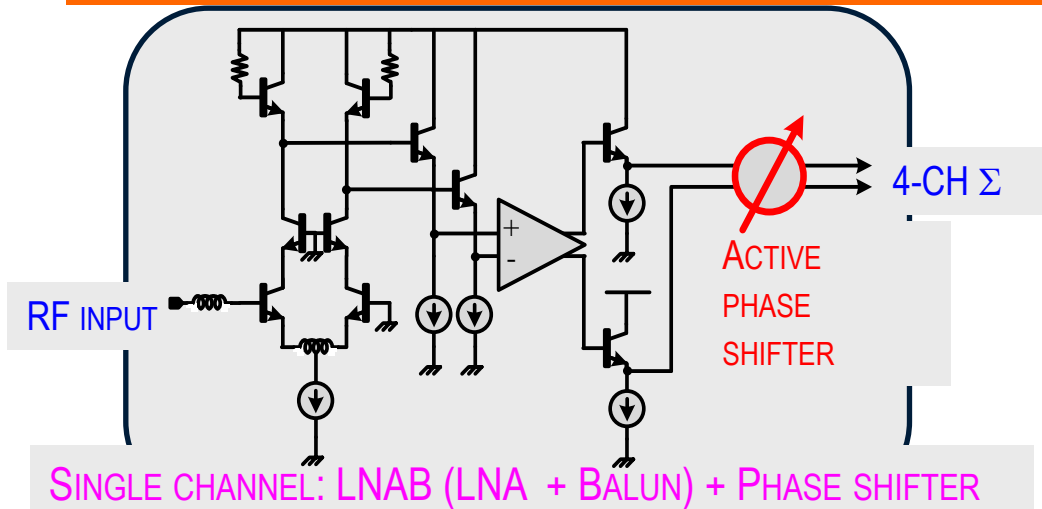8-ELEMENT PHASED-ARRAY (12 GHz, SCHEMATICS)




- Emitter-coupled diff-pair
- Single-to-differential conversion
- L-C input matching
- 2nd-stage diff amp: CMRR

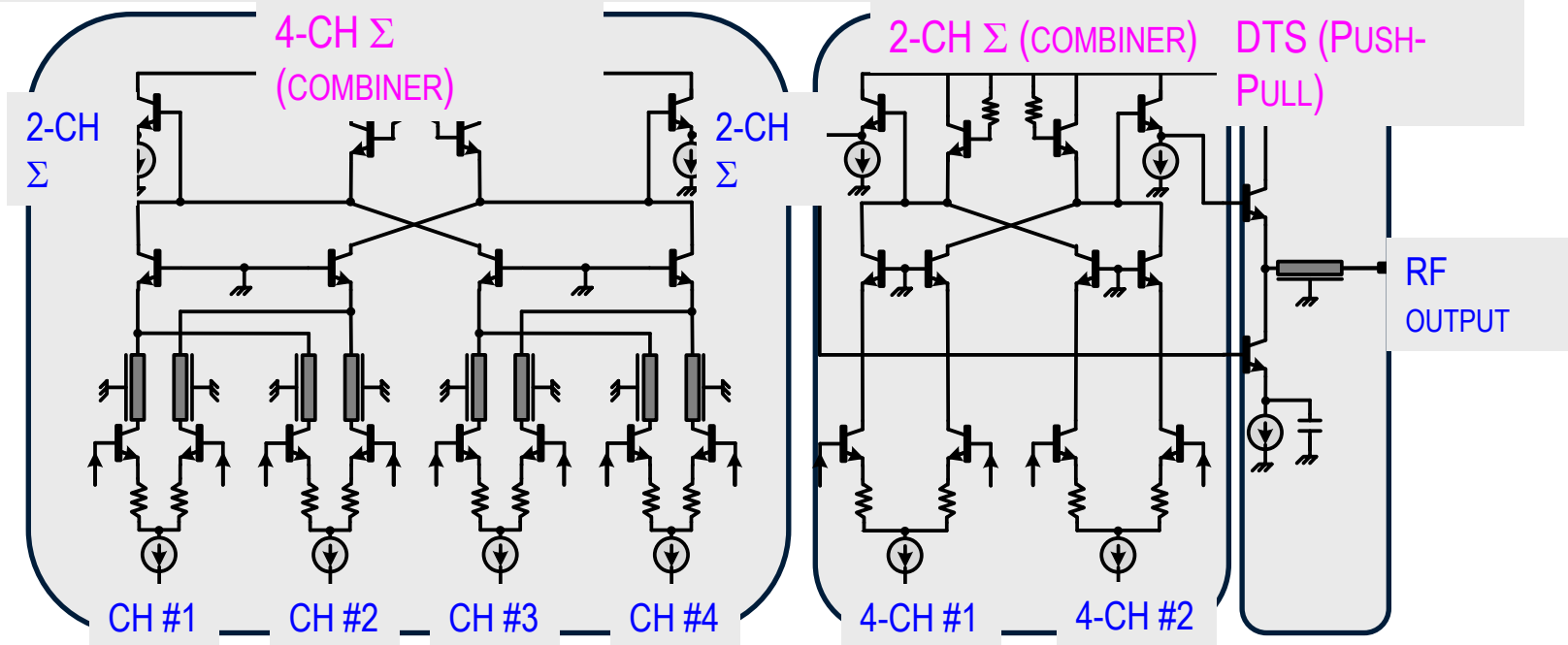
- Signal - Σ in current domain
- Binary fashion signal - Σ
- Wideband signal- Σ
- NMOS-based push-pull



 8-ELEMENT PHASED-ARRAY (12 GHz, CH-TO-CH COUPLING)



 
SIGNAL ERROR DUE TO COUPLING
(@ 12 GHz, GAIN=20 dB)




- Coupling causes amplitude & phase errors which could be serious in silicon
- Measured errors are negligible due to high isolation layout, e.g. metallic barrier

4-ELEMENT mm-WAVE PHASED-ARRAY RX (44 GHz, ARCH & CHIP PHOTO)

PHASED-ARRAY RX BLOCK DIAGRAM

 


CHIP PHOTOGRAPH

 


SiGe BiCMOS ($f_T=150$ GHz), Area=1.4x1.7 mm²

4-ELEMENT mm-WAVE PHASED-ARRAY RX (44 GHz, WILKINSON COUPLER)

WILKINSON COUPLER MEASUREMENTS

 


CHIP PHOTOGRAPH

 

SiGe BiCMOS ($f_T=150$ GHz), Area=1.4x1.7 mm²



4-ELEMENT mm-WAVE PHASED-ARRAY RX (44 GHz, MEASUREMENT)

PARAMETER	RESULTS
Technology	0.18-μm SiGe BiCMOS (Jazz SiGe120, 1P6M)
Supply voltage	5 V (analog), 3.3 V (digital)
Current consumption	I _{bias} =118 mA (29 mA per channel)
Frequency band	Q-band (3-dB BW: 32.3-44 GHz)
Phase resolution	4-bit (accuracy > 5-bit)
Input return loss	< -10 dB @ 40-50 GHz
Output return loss	< -10 dB @ 40-50 GHz
Power gain (ave)	10.4 dB @ 38.5 GHz
NF	12.4 dB @ 38.5 GHz
Phase error (RMS)	< 8.7° @ 30-50 GHz
Gain error (RMS)	< 1.2 dB @ 30-50 GHz
IP3	-13.8±1.5 dBm @ 38.5 GHz
Phase mismatch (RMS)	< 2° @ 30-50 GHz (between all channels)
Amp. mismatch (RMS)	< 0.4 dB @ 30-50 GHz (between all channels)
Isolation (CH-to-CH)	< -35 dB @ 30-50 GHz
Array factor directivity	6 dB (4-element)
Chip area	1.4 x1.7 mm ²

 


Ref: K.-J. Koh *et al*, "A Q-Band Four-Element Phased-Array Front-End Receiver with Integrated Wilkinson Power Combiners in 0.18-μm SiGe BiCMOS Technology", IEEE Trans. On MTT, Sept 2008

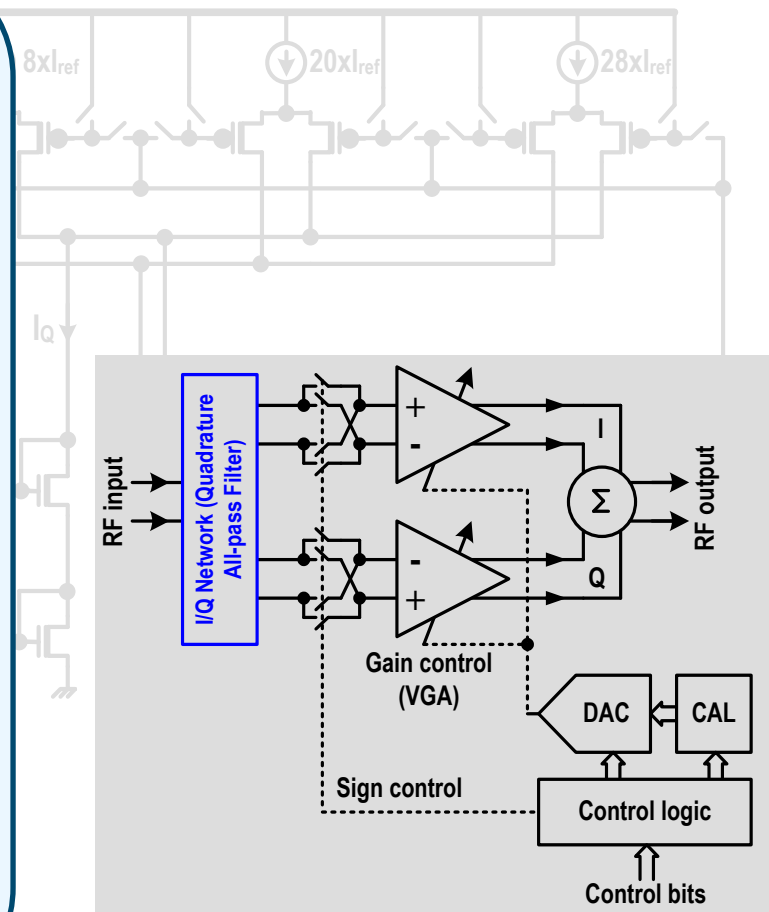 ACTIVE PHASE SHIFTER - I/Q NETWORK (LOSSLESS)



SOME REMARKS ON I/Q NETWORK

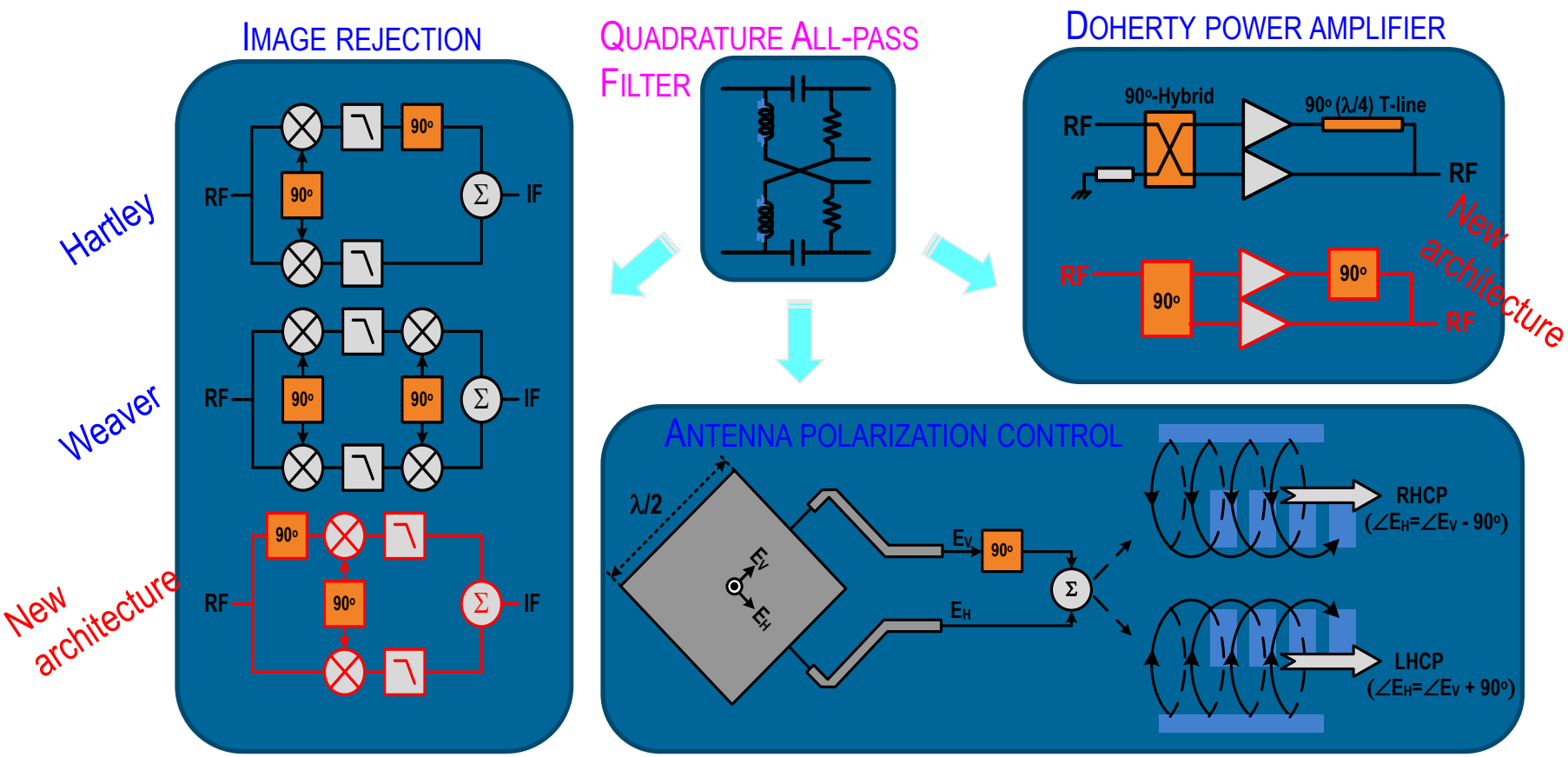
- I/Q network is an indispensable block for comm. system, but rarely used at RF signal path due to loss
- Lossless I/Q network, QAF (3dB gain, 3dB NF, All-Pass), enables many new system configurations




- Versatile and promising building block for future RF & mm-wave phased arrays and comm. systems

0.13- μm CMOS ACTIVE PHASE SHIFTERS

X-BAND (6-18 GHz) DESIGN

 

KU-BAND (15-26 GHz) DESIGN

 


CMOS implementations with same active phase shifter architectures

Phase shifter core size: 0.3 x 0.4 mm² (smallest one published)

Ref: K.-J. Koh et al, "0.13- μm CMOS phase shifters for X-, Ku-, and K-Band Phased Arrays", IEEE JSSC, Nov. 2007

- First realization of CMOS active phase shifters (4-bit resolution)
- Supported by Intel "UC Discovery Project" (2006-2007)
- Presented at Intel project review meeting & RFIC 2007



ACTIVE PHASE SHIFTER – MEASUREMENTS

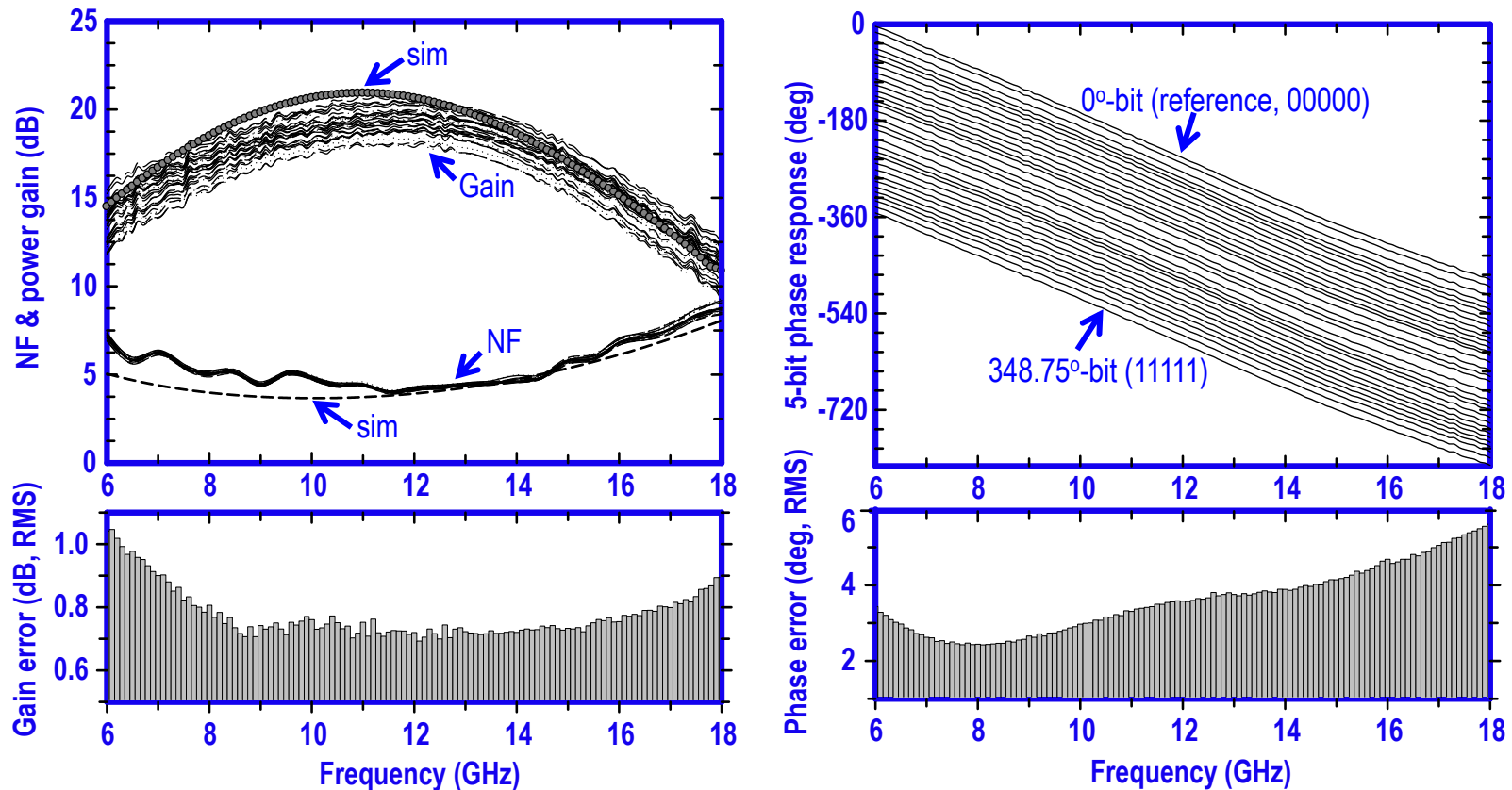

- Gain: 16.5 - 19.5 dB @7.5-15.2 GHz
- Gain error: ≤ 1.1 dB (RMS) @6-18 GHz
- NF: 4 - 5.7 dB @7.5-15.2 GHz
- Phase error: $< 5.6^\circ$ (RMS) @6-18 GHz
- S11 < -10 dB @11-15.5 GHz
- S22 < -10 dB @6-18 GHz


The active phase shifter achieves 6-bit accuracy at 6-18 GHz ($\Delta=360^\circ/2^6=5.625^\circ$)

 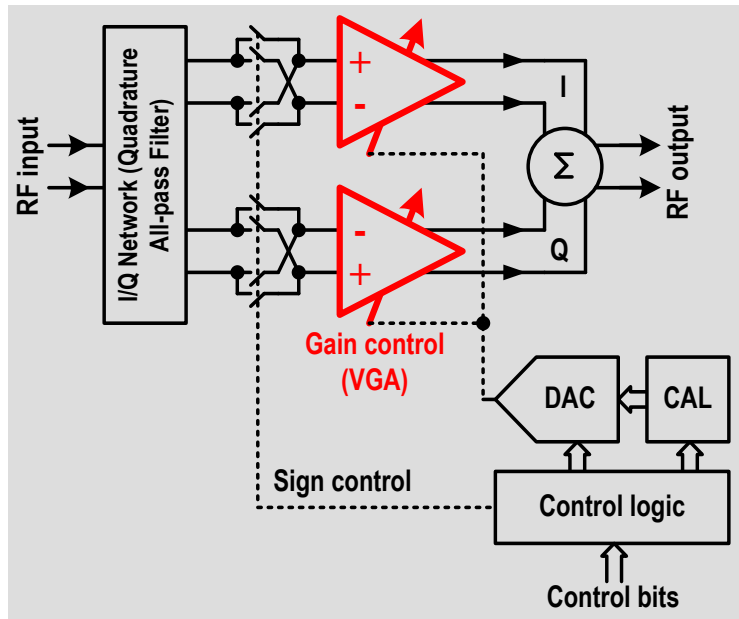ACTIVE PHASE SHIFTER – TEMPERATURE MEASUREMENTS




- I & Q paths are biased with a reference PTAT circuit
- RMS phase error < 6° @ 25°-100° C
- RMS gain error < 0.8 dB @ 25°-100° C
- I & Q amplifiers track each other vs. PVT, resulting in low sensitivity to PVT

ANGLED-DIPOLE ANTENNA DESIGN @12 GHz

 




0.5 λ_0 @ 12 GHz

 

MEASUREMENT


- $S_{11} < -10$ dB @ 10.5-14 GHz
- 102° HPBW
- 3 dB antenna gain
- Coupling < -17 dB
- Can be used +/- 60° scan with 4dB drop in element factor

   Ref: Y. A. Atesal, B. Cetinoneri, K.-J. Koh, G. M. Rebeiz, "X/Ku-Band 8-Element Phased Arrays Based on Single Silicon Chips", 2010 IMS, May 2020





$S_{11} < -10$ dB @ 10-14 GHz $S_{22} < -10$ dB @ 8.5-13.5 GHz

 8-ELEMENT PHASED-ARRAY (6-18 GHz, BOARD MEASUREMENT)






S11 < -10 dB @ 10-14 GHz

  

S22 < -10 dB @ 8.5-13.5 GHz


3-D PACKAGE SIMULATION (1)

   

Modeled using HFSS
Coupling between adjacent ports < -17 dB


3-D PACKAGE SIMULATION (2)

 Coupling between adjacent ports is reduced to < -25 dB




Ground trace extension
between signal lines




Left open (after 0.75 mm)

 

 Shorted to the bottom gnd (after 0.75 mm)






ACTIVE COMBINER V.S. PASSIVE COMBINER

 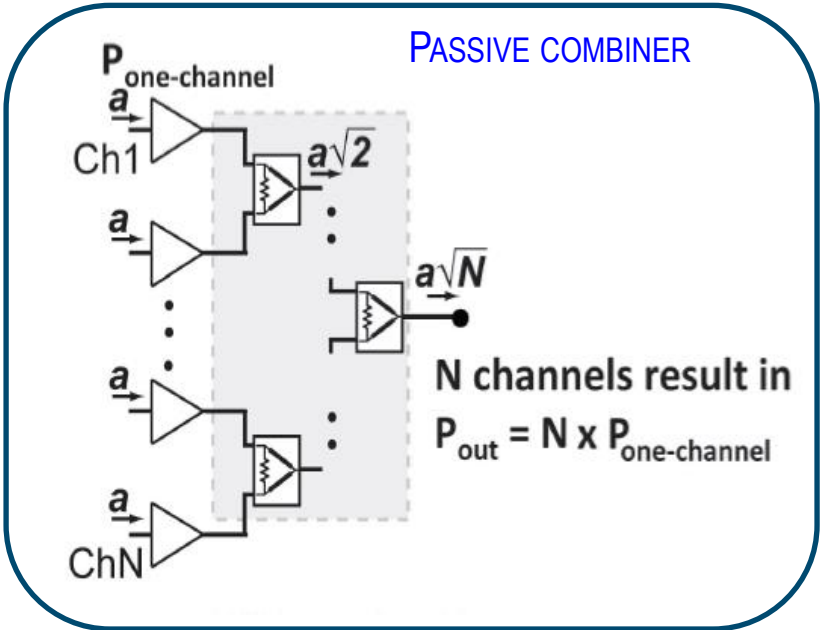
 


  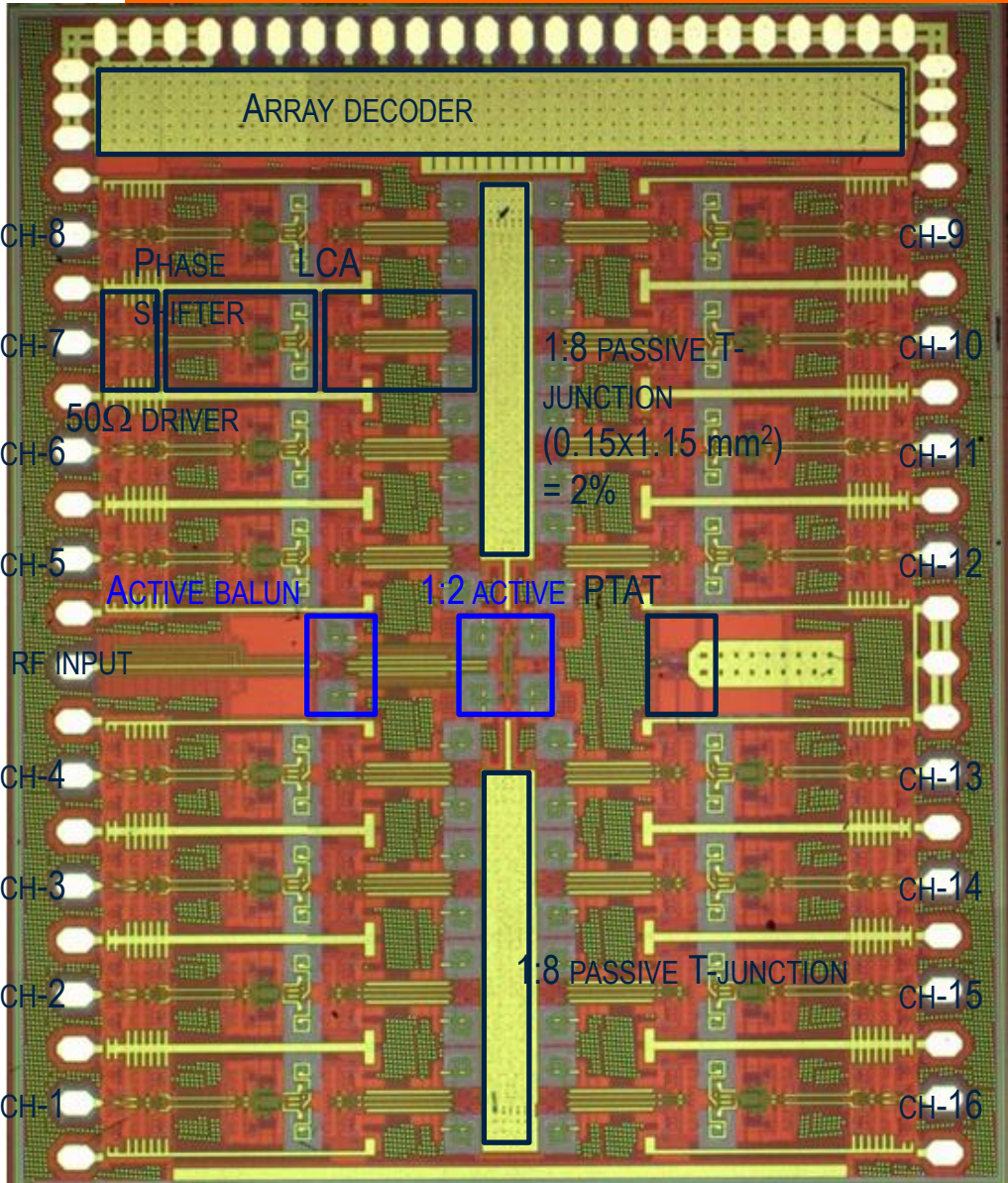- 20-21 dB channel gain
- 18 dB array gain ($\propto N^2$)
- ~ 3 dB antenna gain
- 0.7 dB loss due to connector
- ~40 dB overall measured gain


16-ELEMENT mm-WAVE PHASED-ARRAY Tx (44 GHZ, SCHEMATIC)



  16-ELEMENT mm-WAVE PHASED-ARRAY Tx (44 GHz, 1:8 T-JUNCTION)




SHIELDED BROADSIDE-COUPLED DIFF-T-LINE

 


- Perfectly shielded (no coupling btw T-lines)
- Allow compact integration of many diff T-lines


1:8 TEE-JUNCTION DIVIDER

 

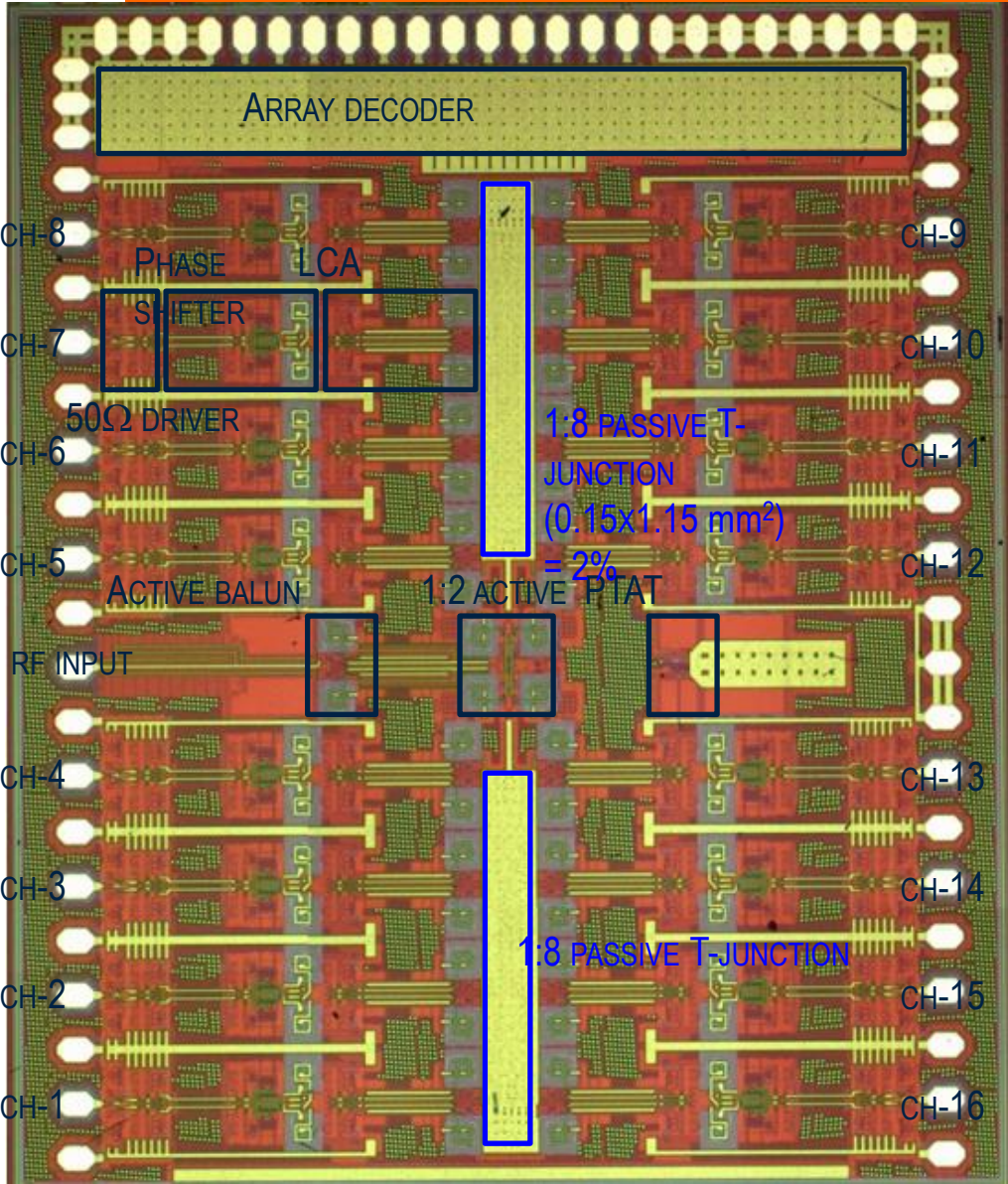16-ELEMENT mm-WAVE PHASED-ARRAY Tx (44 GHz, COAXIAL T-LINE)




SHIELDED BROADSIDE-COUPLED DIFF-T-LINE

 


- Perfectly shielded (no coupling btw T-lines)
- Allow compact integration of many diff T-lines

ODD-MODE E-FIELDS

 


EVEN-MODE E-FIELDS

 


- $W=3\text{ }\mu\text{m}$: odd-mode impedance= $50\text{ }\Omega$ (HFSS sim)
- Most fields (> 95%) are confined btw diff-T lines
- Measured loss: 3 dB / 0.5 mm @45 GHz

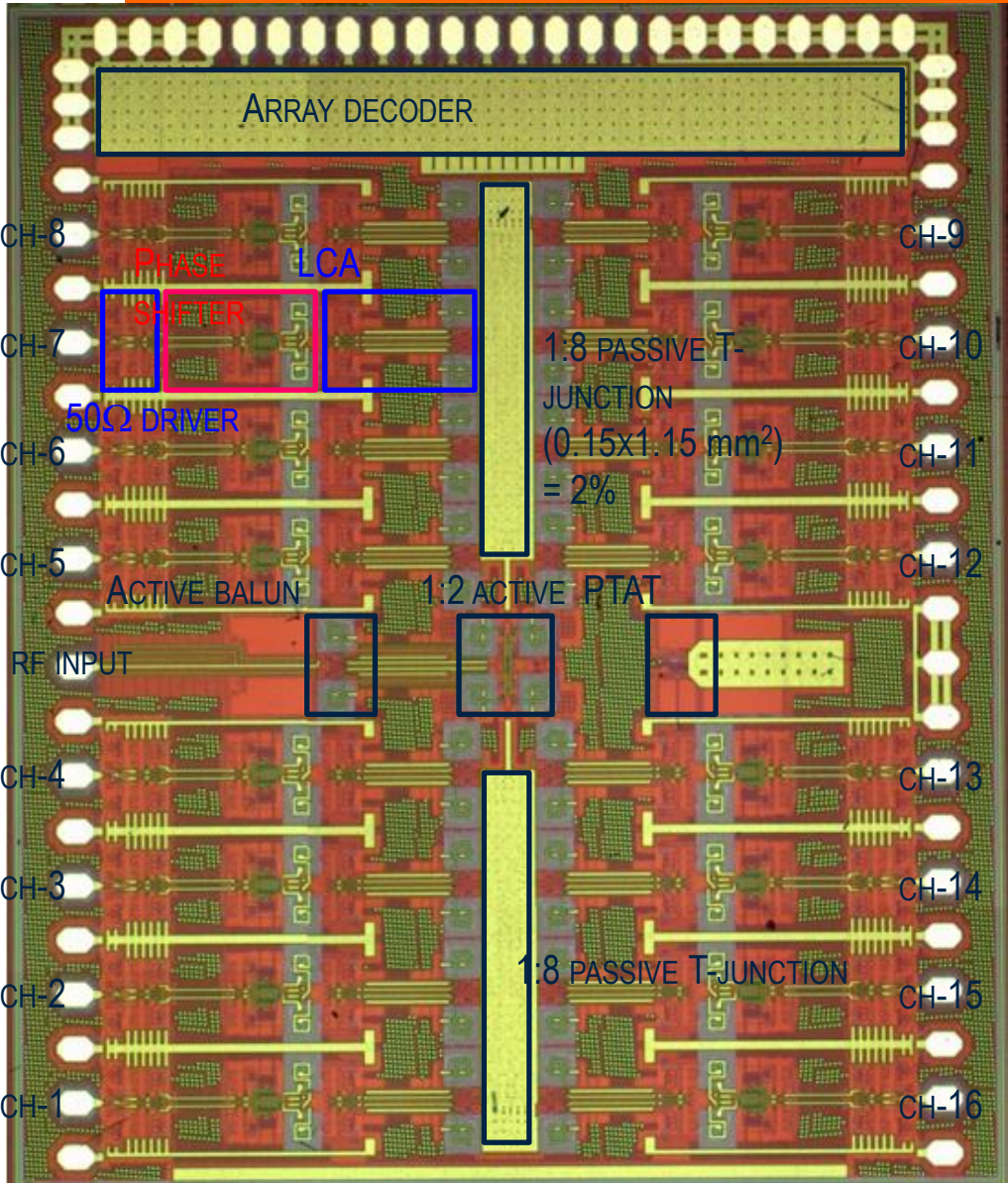
16-ELEMENT mm-WAVE PHASED-ARRAY Tx (44 GHZ, SCHEMATIC)






LOSS COMPENSATION AMP (LCA)

 

50Ω DRIVER

 

   
16-ELEMENT mm-WAVE PHASED-ARRAY TX (44 GHz, MEASUREMENT)




- Power gain: 12.5 dB @42.5 GHz
- RMS gain variation < 1.3 dB @30-50 GHz
- 3-dB BW: 40-45.6 GHz
- $S_{11} < -10$ dB @36.6-50 GHz
- $S_{22} < -10$ dB @37.6-50 GHz
- RMS phase error < 8.8° @40-50 GHz
- P_{sat} : -2.5 ± 1.5 dBm (for all phase states) @42.5 GHz
- OP_{1dB} : -5 ± 1.5 dBm @42.5 GHz

16-ELEMENT mm-WAVE PHASED-ARRAY Tx (CHIP-SET TREND)

EVOLUTION OF PHASED ARRAY CHIP-SET

 


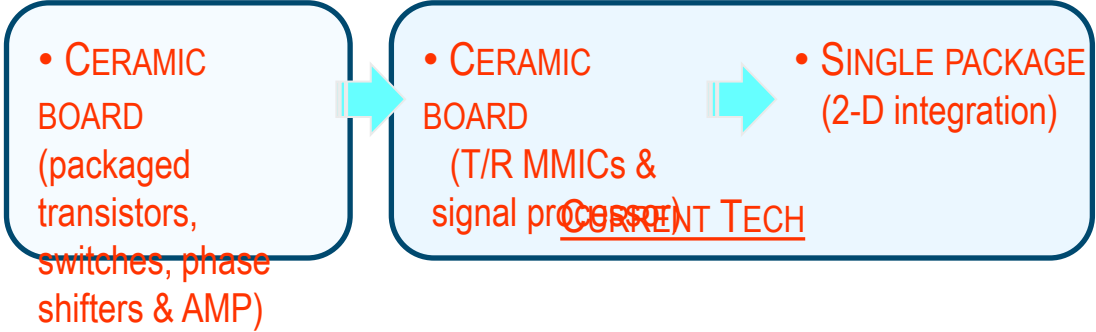Ref: 2007 Multi-function phased-array RADAR Conference





16-ELEMENT mm-WAVE PHASED-ARRAY TX (LARGE ARRAY, 3-D INTEGRATION)

EVOLUTION OF PHASED ARRAY CHIP-SET

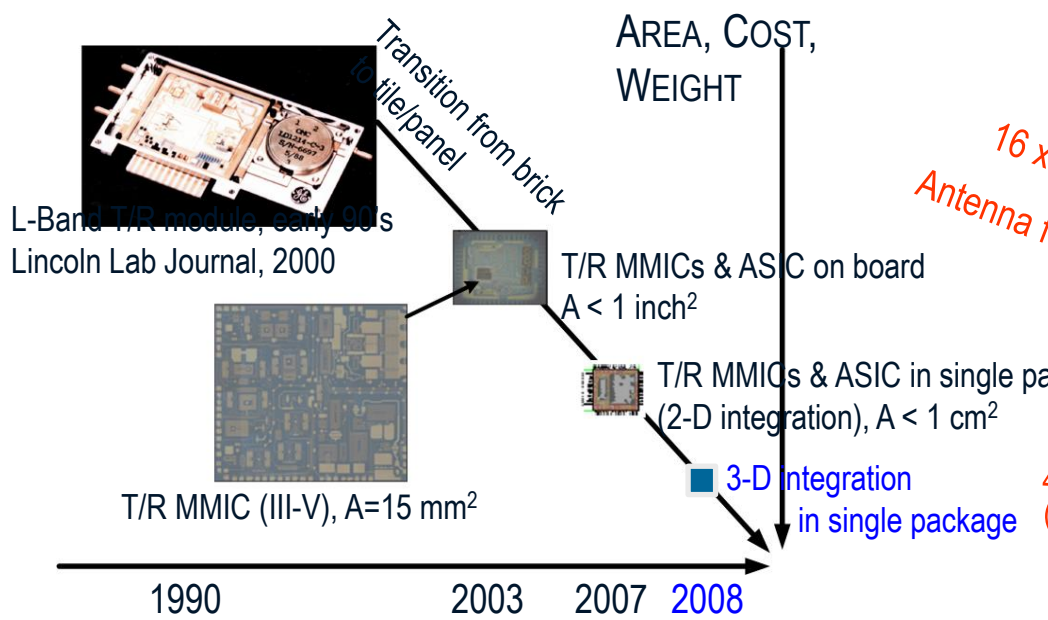

Ref: 2007 Multi-function phased-array RADAR Conference


MULTI-LAYER 3-D INTEGRATION

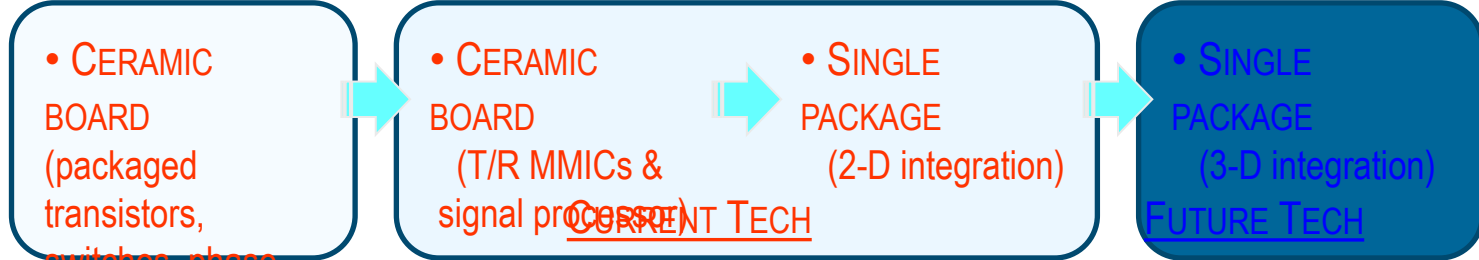 


TYPICAL PASSIVE PHASE SHIFTERS (TOPOLOGIES)

T-LINE APPROACHES


1 Switched T-lines

 

2 90° branch-line hybrid coupler

 


3 Periodic loaded line

 


LUMPED PASSIVE APPROACHES


1 Lumped synthetic T-lines

 

2 Lumped hybrid coupler

 


3 PF / HPF approach

 



ISSUES: Chip area, Loss, Nonlinear control

SAMPLING @ TIME-DOMAIN

 


SAMPLE & HOLD (ADC)

 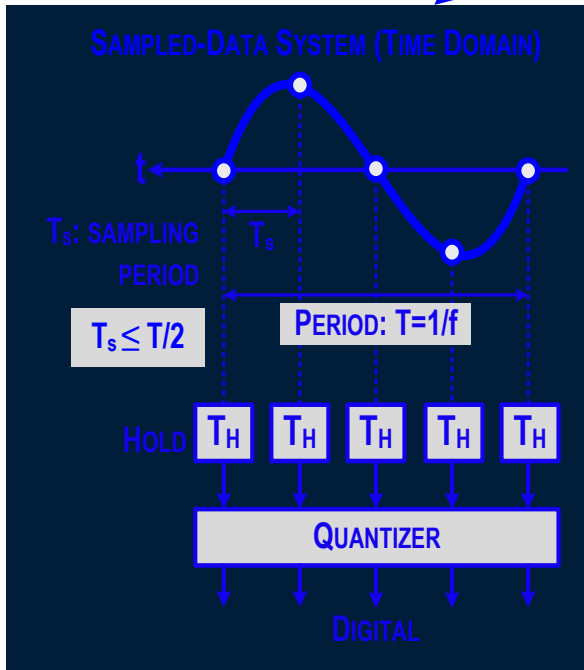- Time-domain sampling
- $T_s < \text{Nyquist rate}$
 ↳ Aliasing
- Need hold time, T_H , to quantize





SAMPLING @ SPACE-DOMAIN

 

SAMPLE & HOLD (ADC)

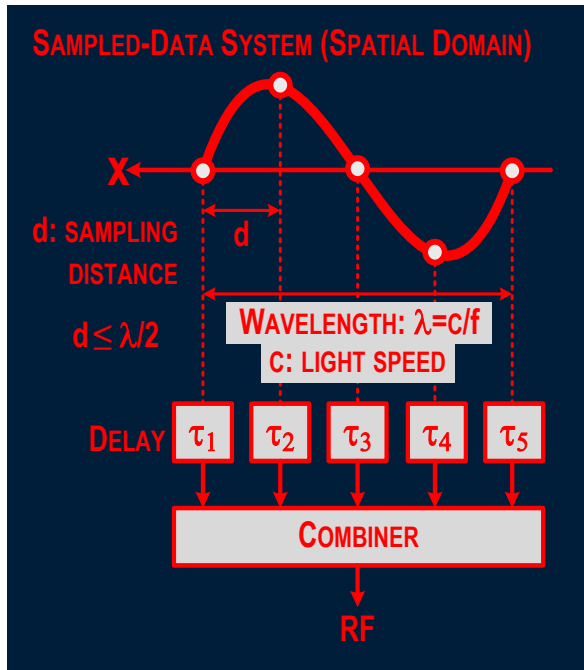 - Time-domain sampling
- $T_s < \text{Nyquist rate}$
 ↳ Aliasing
- Need hold time, T_H , to quantize



PHASED-ARRAY (MULTI-ANTENNA)

- Space-domain sampling
- $d < \text{Nyquist distance}$
 ↳ Aliasing ("Grating lobe")
- Need τ to in-phase ("Select")
 or to out-of-phase ("Reject")


TIME

$$\omega = \frac{2\pi}{T}$$


SPACE

$$k = \frac{2\pi}{\lambda}$$

 2-ANTENNA ARRAY (2-POINT SAMPLING, INTUITIVE)




 - FOR THE SAME WAVE-FRONT
(incident angle: 30°),
- A arrives first to ANT ①
 - B travels X_d more to arrive ANT ②




PHASE DIFFERENCE BTW ① & ②
 
$$\phi_d = \underbrace{\frac{\lambda}{2} \times \sin 30^\circ \times \frac{1}{c} \times 2\pi f}_{\text{Arrival time difference}} \times \underbrace{\lambda/4}_{\text{Distance } (X_d)}$$
$$= \pi \times \sin 30^\circ = 90^\circ$$




PHASED ARRAY V.S. MIMO (1)


PHASED ARRAY

 



MIMO

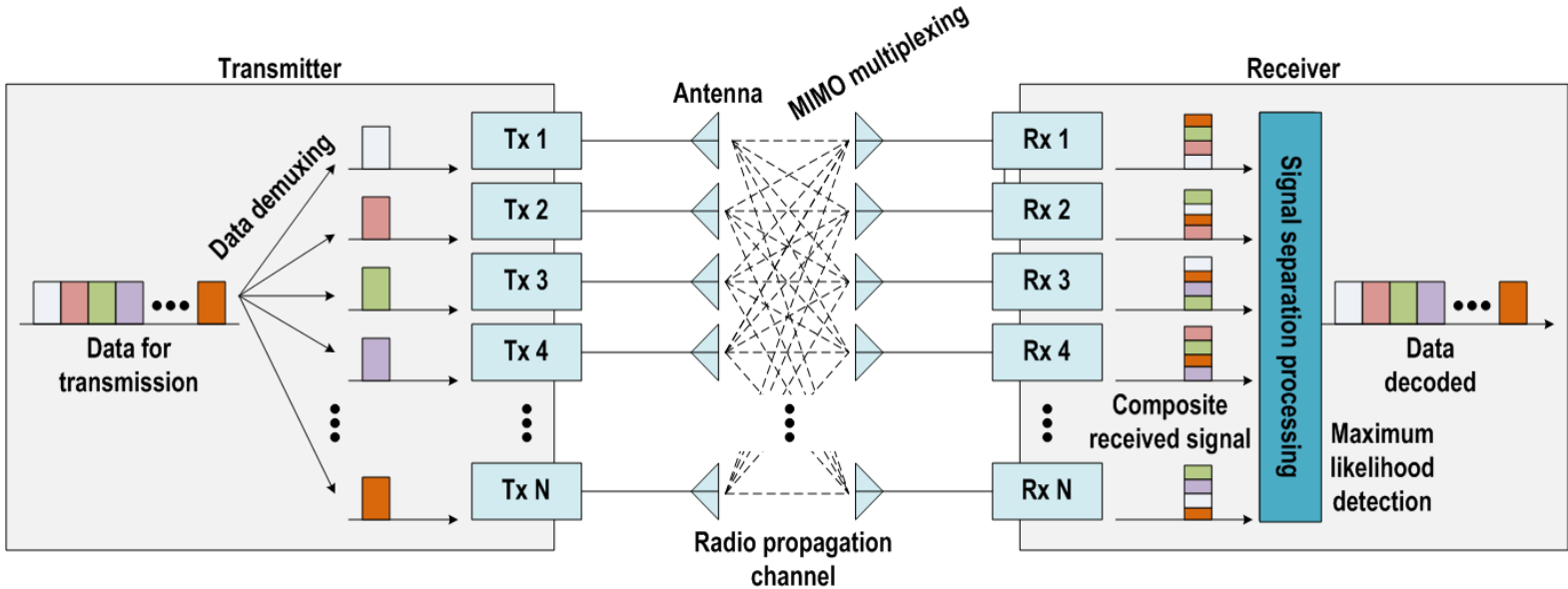


PHASED ARRAY V.S. MIMO (2)

 

 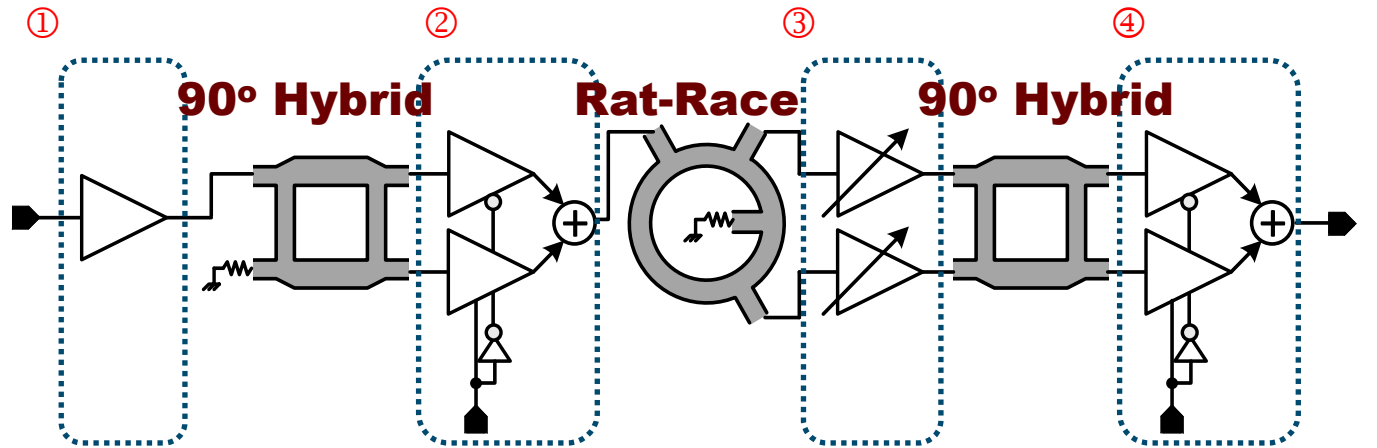
Vector-Summing Phase Shifter (90° hybrid coupler)



①: LNA

 



 
② & ④: Switch Amplifier
(functioning as an active
switch)



③: VGA

-
- The operating principle of an active phase shifter is to vary the amplitudes of two orthogonally-phased input signals to get the desired phase at the output.

   Vector-Summing Phase Shifter (Quadrature all-pass filters)



- Exactly the same I/Q phase performance as the 2-stage polyphase filter
- 6 dB larger voltage gain than the 2-stage polyphase filter

Phased Arrays versus Timed Arrays

